



## → Tag Chip Technologies

Prof. Hao Min  
Auto-ID Labs at Fudan University, China

Jan. 23, 2006



# Outlines



- User requirements
- Performance enhancements
- Some new technologies being developed



# User Requirements



- **Long read range**
- **100% read coverage**
- **Similar read performance in the worldwide frequency range 860-960MHz**
- **Security and authentication**



# Improve the Read Range




- **Lower the power consumption of tag chips**
  - Improve the conversion efficiency of rectifier
    - Bootstrapped circuits
    - Low V<sub>t</sub> using Schottky diode
  - Sub-threshold digital circuits
    - V<sub>dd</sub> = 0.5V
    - Dynamic adjust of communication speed based on received power
  - Adiabatic circuits
    - Energy recycling
  - Conventional low power circuit design technologies


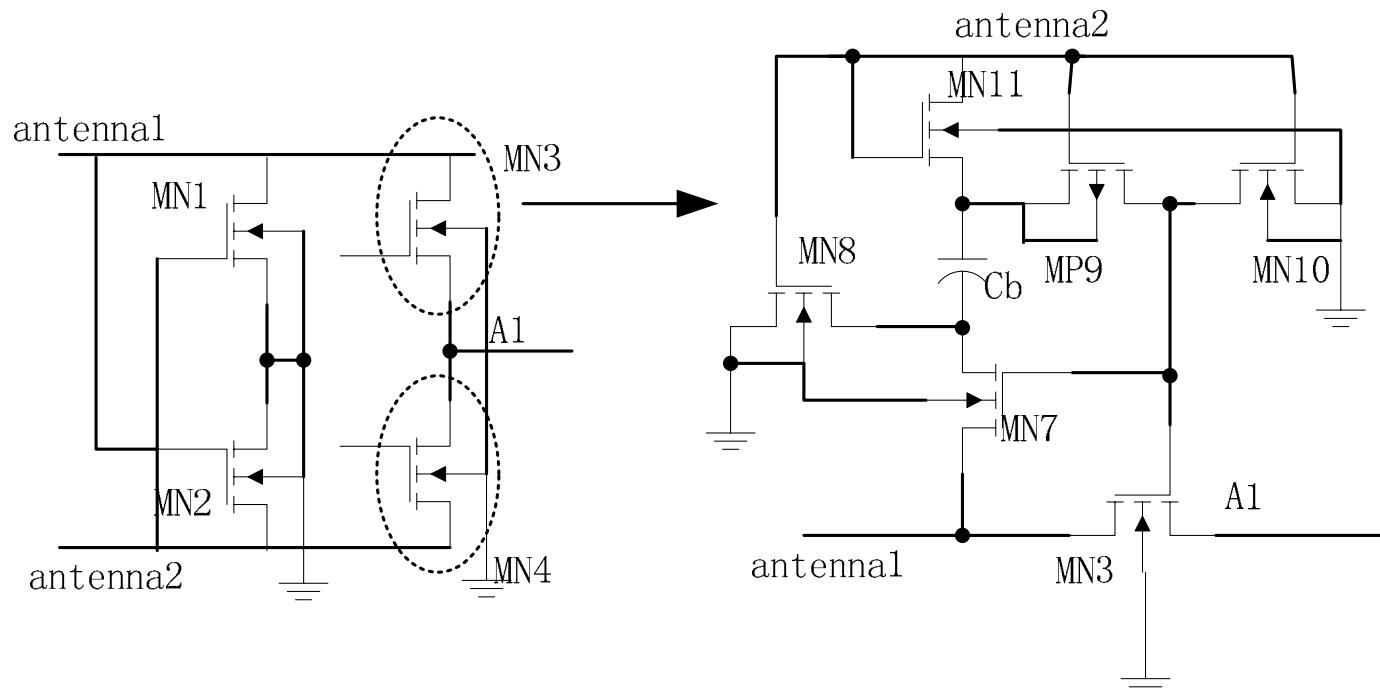
# Bootstrapped Rectifier



- Improve the rectify efficiency by 30-100%
- Suitable for HF tag






# Adiabatic Circuits for RFID




- 50% power drop is expected

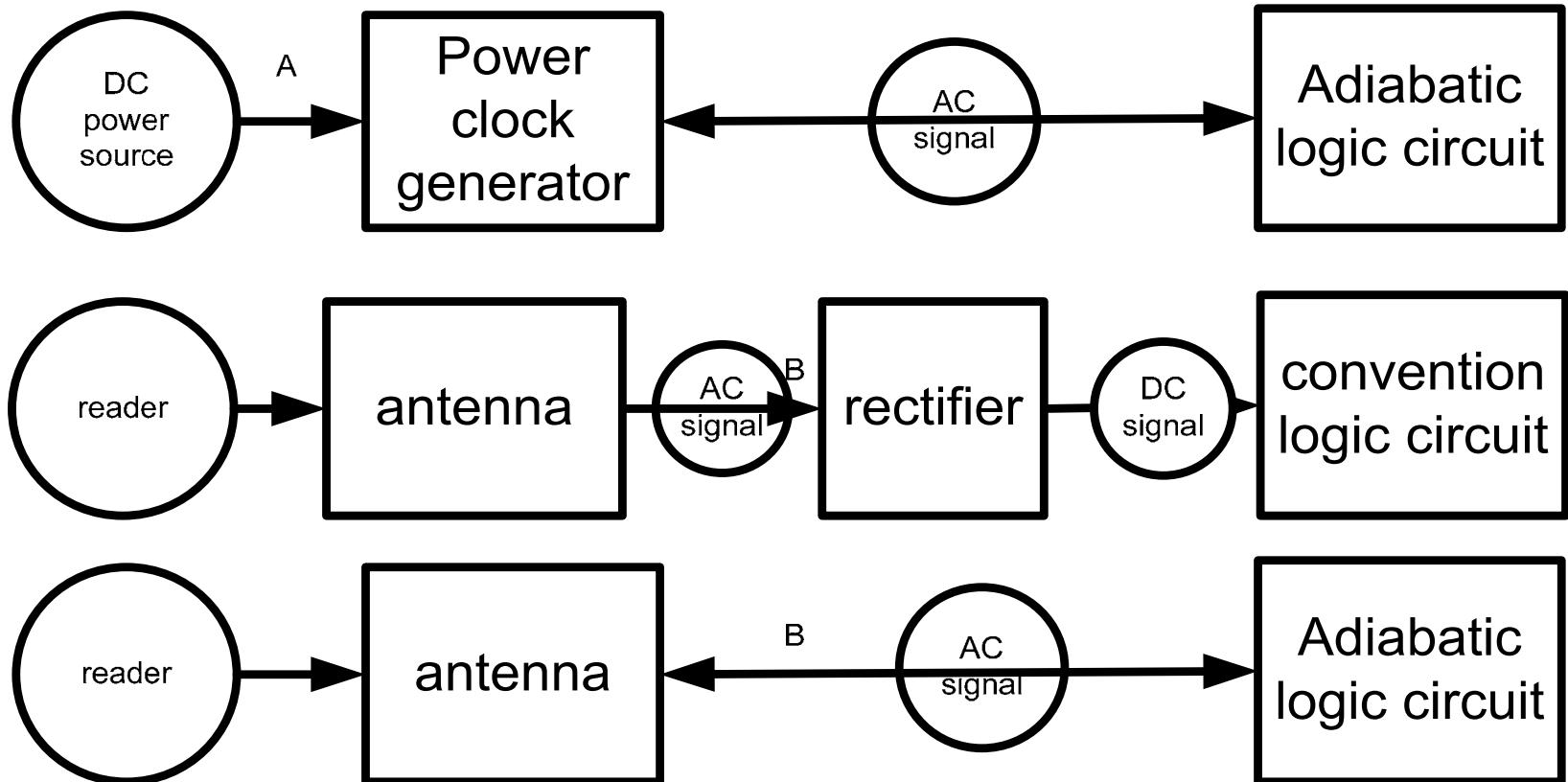



# Sub-threshold Circuits

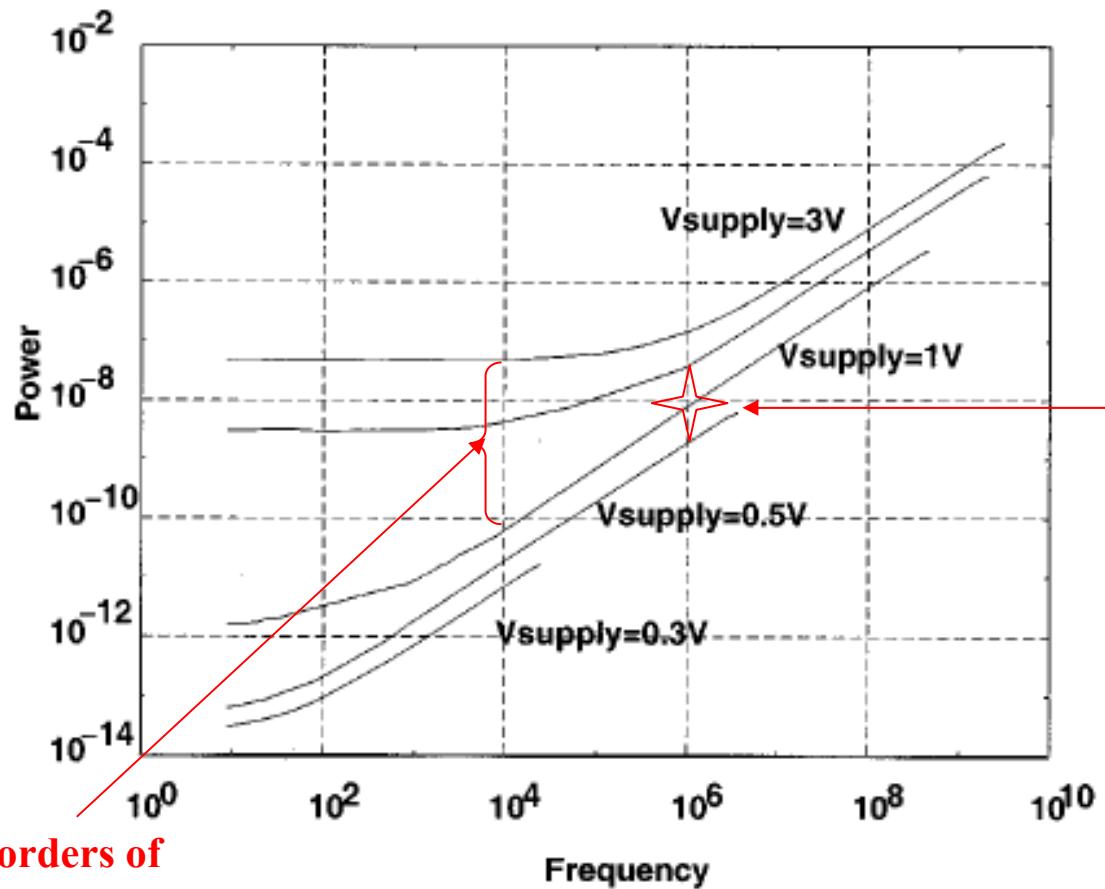


- Frequency=1Mhz
- VDD=1V
- Power=10nA


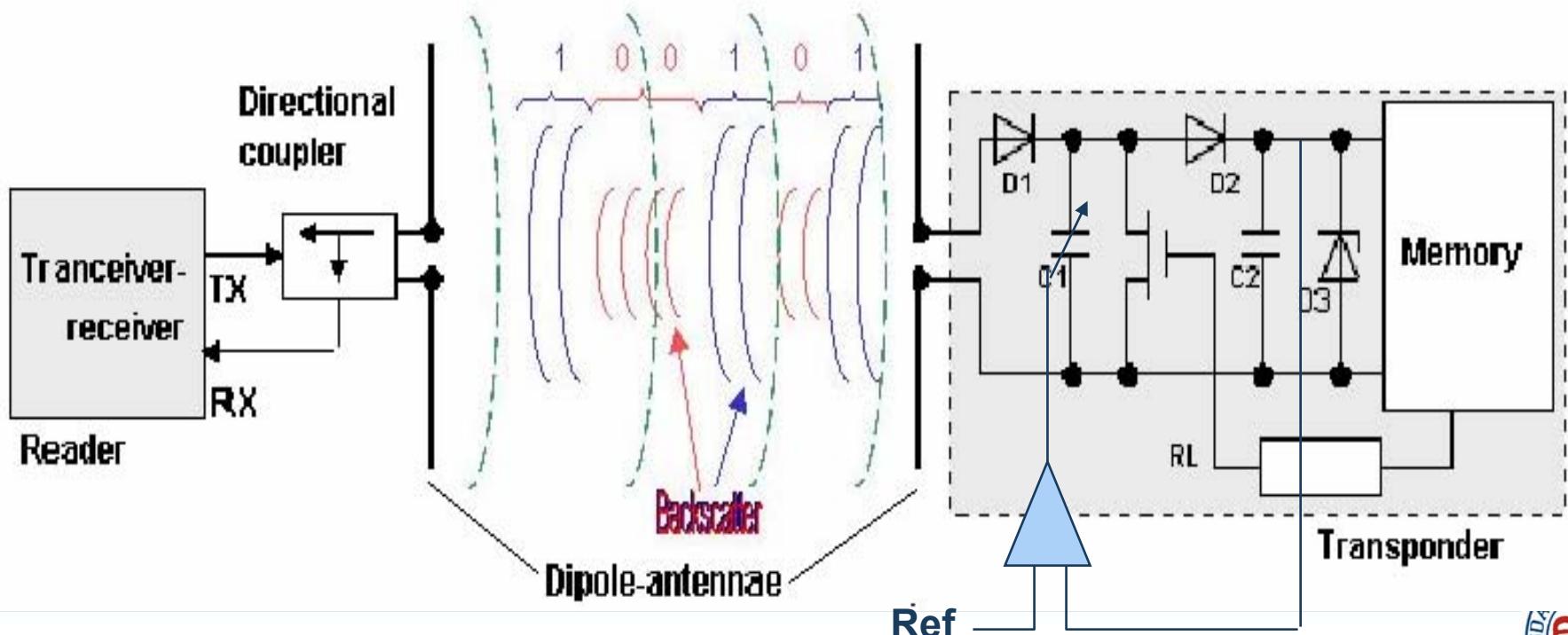
# Improve the Read Coverage



- **Dynamic antenna matching circuits**
  - Improve the mask effect of closer tags
  - Protect tags from being burned






# Worldwide frequency



- Adaptive tuning circuits

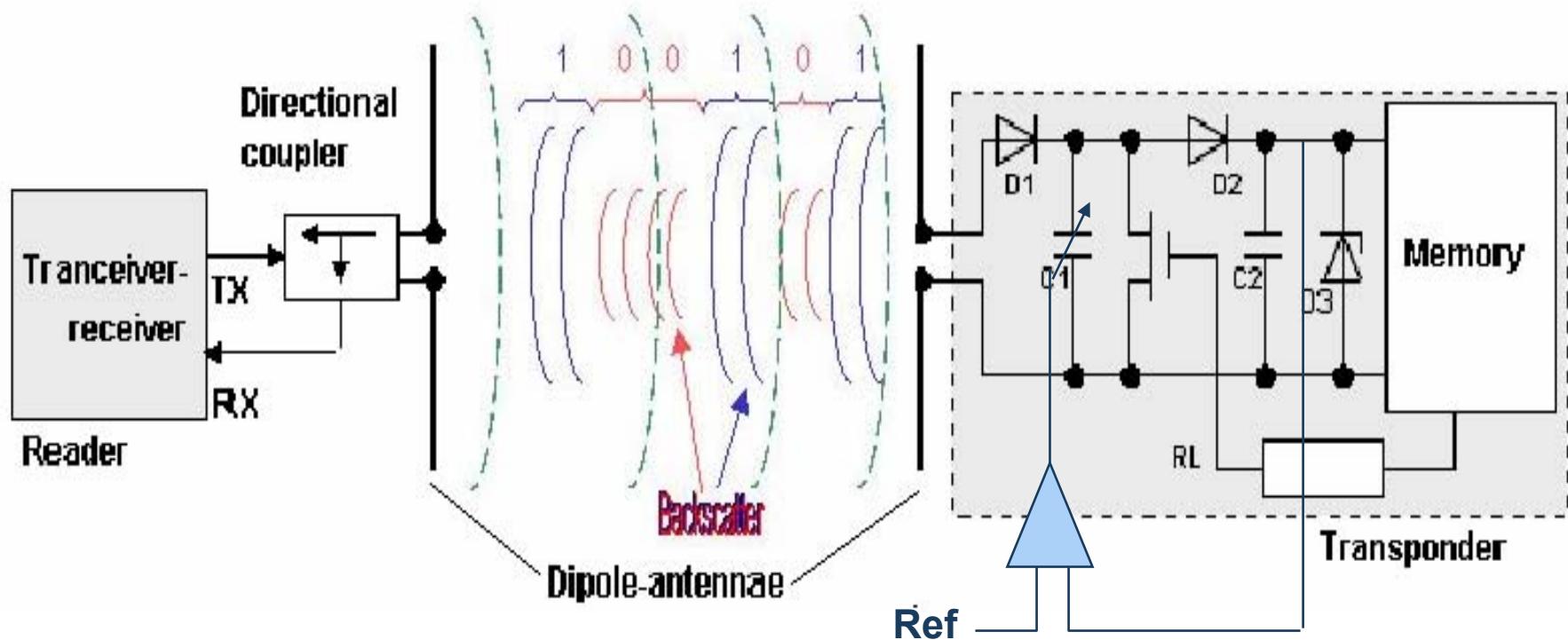




# Security and Authentication



- **Two way authentication**
- **Encrypted communication between tags and readers**
- **Light crypto engine**
  - Low cost
  - Low power
  - Adequate security between tags and readers
- **Shared random number generator (share with anti-collision)**



# Authentication Flow Based on C1G2

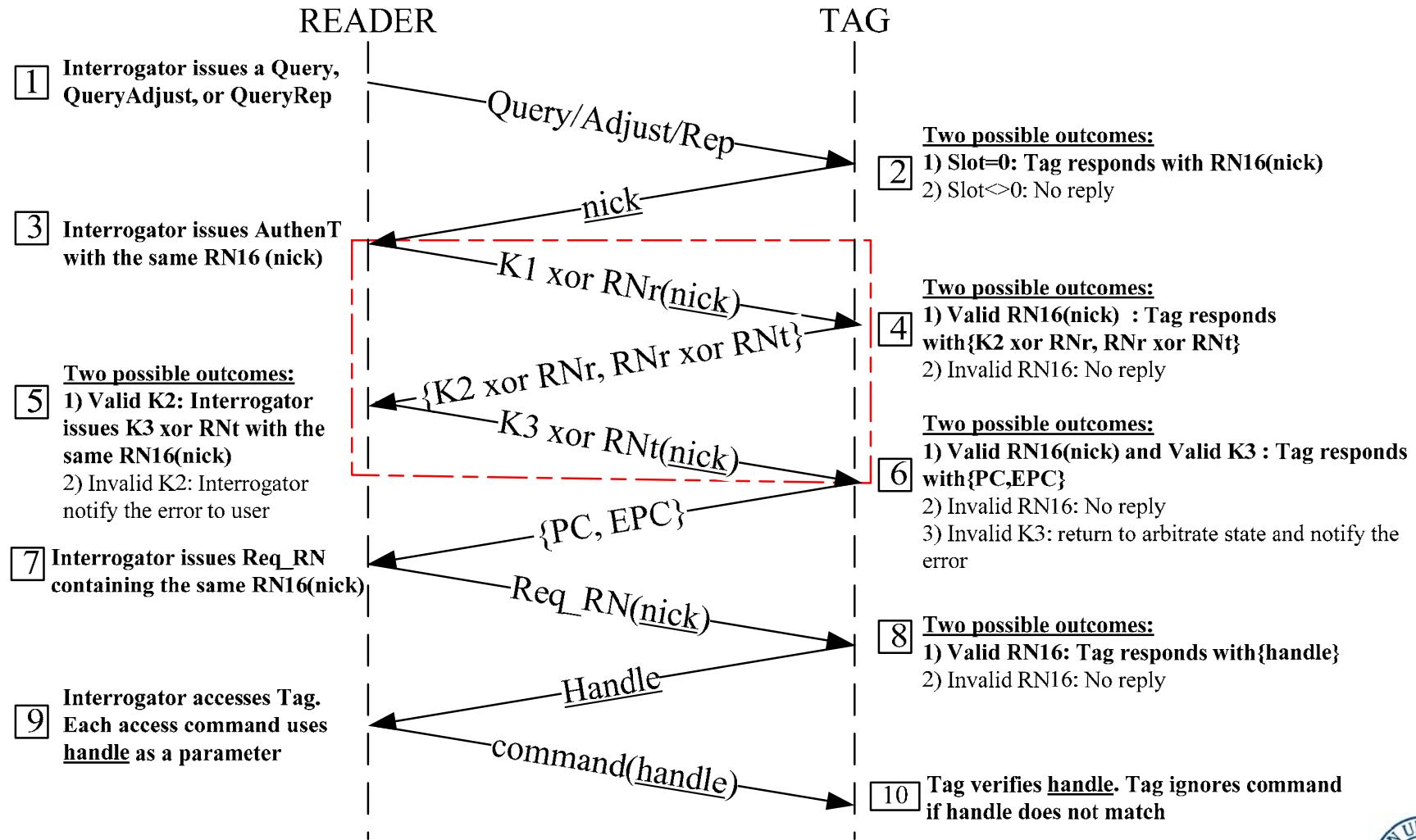



# Q & A



<http://www.autoidcenter.cn>

