

## Part II Problems and Solutions

**Problem 1:** [Series RLC circuits; amplitude and phase] Open the Mathlet Series RLC Circuit. Here we will focus entirely on the current response, so it will be clearer if the check boxes labelled  $V_R$ ,  $V_L$ ,  $V_C$ , are left unchecked. But click twice on the  $I$  box, to make a green curve appear in the graphing window, representing the current through any point in the circuit as a function of time.

The Mathlet uses the International System of Units, SI, formerly known as the mks (meter-kilogram-second) system. The equation

$$L\ddot{I} + R\dot{I} + (1/C)I = \dot{V}$$

is correct when:

the resistance  $R$  is measured in ohms,  $\Omega$ ,

the inductance  $L$  is measured in H, henries,

the capacitance  $C$  is measured in farads, F,

the voltage  $V$  is measured in volts, also denoted  $V$ ,

the current  $I$  is measured in amperes, A.

The slider displays millihenries, mH ( $1 \text{ mH} = 10^{-3} \text{ H}$ ) and microfarads,  $\mu\text{F}$  ( $1 \mu\text{F} = 10^{-6} \text{ F}$ ), and milliseconds, ms ( $1 \text{ ms} = 10^{-3} \text{ sec}$ ).

The Mathlet studies a sinusoidal input signal  $V(t) = V_0 \sin(\omega t)$ . Play around with the various sliders and watch the effect on the (blue) voltage curve and the (green) current curve.

(a) By experimenting, identify a few values of the system parameters  $R$ ,  $L$ ,  $C$ ,  $V_0$ ,  $\omega$ , for which the current and the voltage are perfectly in phase. For example, if  $L = 500 \text{ mH}$  and  $\omega = 200 \text{ radians/second}$ , what values of  $R$ ,  $C$ , and  $V_0$  put  $I$  in phase with  $V$ ?

(b) Now calculate the relationship between the system parameters which leads to  $I$  and  $V$  being in phase. Do your experiments align with your calculations?

(c) Set  $R = 100 \Omega$ ,  $L = 1000 \text{ mH}$ ,  $C = 100 \mu\text{F}$ ,  $V_0 = 500 \text{ V}$ . Vary  $\omega$  and watch the action. For what value of  $\omega$  is the amplitude of  $I(t)$  maximal? What is that amplitude (in amps)? What is the phase lag between the input signal,  $V_0 \sin(\omega t)$ , and the system response,  $I(t)$ , for that value of  $\omega$ ?

(d) Verify the three observations made in (c) computationally. You should be able to do this for general values of  $R$ ,  $L$ ,  $C$ ,  $V_0$ .

**Solution:** (a) It seems that  $C$  must be close to  $50 \mu\text{F}$ . The values of  $V_0$  and  $R$  don't seem to matter.

**(b)** Here is one of several ways to do this problem. We are looking at

$$L\ddot{I} + R\dot{I} + (1/C)I = V_0\omega \cos(\omega t).$$

To understand its sinusoidal solution, make the complex replacement

$$L\ddot{z} + R\dot{z} + (1/C)z = V_0\omega e^{i\omega t},$$

so that  $I_p = \text{Re}(z_p)$ . By the ERF, the exponential solution is  $z_p = \frac{V_0\omega e^{i\omega t}}{p(i\omega)}$ . To be in phase with  $\sin(\omega t)$ , the real part of this must be a positive multiple of  $\sin(\omega t)$ . This occurs precisely when the real part of  $p(i\omega)$  is zero.  $\text{Re } p(i\omega) = (1/C) - L\omega^2$ , so the relation is  $1/C = L\omega^2$ .

To check, when  $L = 500 \text{ mH} = .5 \text{ H}$  and  $\omega = 200 \text{ rad/sec}$ , the system response is in phase when  $C = 1/ (.5 \times (200)^2) = 50 \times 10^{-6} \text{ F} = 50 \mu\text{F}$ .

**(c)** It seems that the maximal system response amplitude  $I_r$  occurs when  $\omega = 100 \text{ rad/sec}$ , and that it is about 5 amps. Then the solution is in phase with the input voltage.

**(d)** In **(b)** we saw that the solution is the real part of  $z_p = \frac{V_0\omega e^{i\omega t}}{p(i\omega)}$ . The amplitude of this sinusoid is  $\left| \frac{V_0\omega}{p(i\omega)} \right|$ , which is maximal when its reciprocal  $\left| \frac{(1/C - L\omega^2) + Ri\omega}{V_0\omega} \right| = \left| \left( \frac{1}{C\omega} - L\omega \right) + Ri \right|$  is minimal. The imaginary part here is constant, so as  $\omega$  varies the complex number moves along the horizontal straight line with imaginary part  $R$ . The point on that line with minimal magnitude is  $Ri$ , which occurs when the real part is zero:  $1/C\omega = L\omega$ , or  $\omega_r = 1/\sqrt{LC}$ . The amplitude is then  $I_r = g(\omega_r)V_0 = V_0/R$ . It depends only on  $V_0$  and  $R$ , not on  $L$  or  $C$ ! Finally, this is the same as the condition for phase lag zero, so the phase lag at  $\omega = \omega_r$  is zero.

With the given values  $R = 100 \Omega$ ,  $L = 1 \text{ H}$ ,  $C = 10^{-4} \text{ F}$ ,  $\omega_r = 100 \text{ rad/sec}$ , as observed. When  $V_0 = 500 \text{ V}$  and  $R = 100 \Omega$ ,  $I_r = 5 \text{ Amps}$ , as observed.

### **Problem 2:** *AM Radio Tuning and LRC Circuits*

*An LRC circuit can be modeled using the same DE as in the previous problem. Specifically,*

$$LI'' + RI' + \frac{1}{C}I = E'.$$

*Where  $I$  = current in amps,  $L$  = inductance in henries,  $R$  = resistance in ohms,  $C$  = capacitance in farads and  $E$  = input EMF in volts. Often the important output is the voltage drop  $V_R$  across the resistor. Ohm's law tells us  $V_R = RI$ . This gives us the DE*

$$LV_R'' + RV_R' + \frac{1}{C}V_R = RE'.$$

- (a) Assume  $E = E_0 \cos(\omega t)$  and solve the DE for  $V_R$  in phase-amplitude form.
- (b) Open the 'LRC Filter Applet'. This applet models an LRC circuit with input voltage a superposition of sine waves. Play with the applet –be sure to learn how to vary  $\omega_1$  and  $\omega_2$  by dragging the dots on the amplitude plot.

Describe what happens to the amplitude response plot as  $L$ ,  $R$  and  $C$  are varied.

- (c) An LRC circuit can be used as part of a simple AM radio tuner. In an AM radio broadcast the signal is given by  $a \cos(\omega t)$  where  $\omega$  is the 'carrier' frequency (between 530 and 1600 khz). To really carry information the amplitude  $a$  must vary –this is the amplitude modulation– but, we will ignore this right here.

The range of values for this simple variable capacitor AM radio tuner is  $L \approx .5$  microhenries,  $R$  is the resistance in the wire (very small) and  $C$  is between .02 and .2 microfarads. To keep things simple we will use different ranges however the idea is the same.

In the LRC Filter applet set  $\omega_1 = 1$  and  $\omega_2 = 4$  (set them as close as you can on your system). Set the input amplitudes  $a$  and  $b$  to 1. Find settings for  $L$ ,  $R$  and  $C$  so that the output filters out the  $\omega_2$  part of the signal i.e. the output looks (a lot) like a sine wave of frequency  $\omega_1$ . Give your values for  $L$ ,  $R$  and  $C$ .

How does the quality of the filter change as you vary  $R$ ?

- (d) An antenna on a radio picks up electromagnetic signals from all frequencies. It responds by outputting a signal consisting of voltages at each of these frequencies. This signal is used as input to a tuner circuit.

Using the applet, set  $L = 1$ ,  $R = .5$ . Now, vary  $C$  and then explain why a variable capacitor circuit could be used as an AM radio tuner.

- (e) Show that the natural frequency (undamped, unforced resonant frequency) of the system is  $\omega_0 = 1/\sqrt{LC}$ . Show that even with damping, i.e.,  $R > 0$ ,  $\omega_0$  is always the practical resonant frequency. (Hint: this can be done without calculus by writing  $A(\omega)$  in the proper way.)

**Solution:** (a) Here is the answer with very little comment. (Note we complexify the input before taking the derivative.)

For simplicity write  $V$  for  $V_R$ .

Complex DE:  $L\tilde{V}'' + R\tilde{V}' + \frac{1}{C}\tilde{V} = (RE_0e^{i\omega t})' = i\omega RE_0e^{i\omega t}$ ,  $V = \text{Re}(\tilde{V})$ .

Char. polynomial:  $P(i\omega) = \frac{1}{C} - L\omega^2 + Ri\omega$ .

Note:  $|P(i\omega)| = \frac{\sqrt{(1 - LC\omega^2)^2 + (RC\omega)^2}}{C},$

$$\frac{i}{P(i\omega)} = \frac{C}{(1 - LC\omega^2)^2 + (RC\omega)^2} (RC\omega + i(1 - LC\omega^2)).$$

Exp. Input Thm:  $\tilde{V}_p = \frac{iR\omega E_0}{P(i\omega)} e^{i\omega t}, \quad V_p = \text{Re}(\tilde{V}_p).$

Amplitude-Phase Form:  $V_p = A \cos(\omega t - \phi)$ , where

$$A = \left| \frac{iR\omega E_0}{P(i\omega)} \right| = \frac{RC\omega E_0}{\sqrt{(1 - LC\omega^2)^2 + (RC\omega)^2}} \Rightarrow A = \frac{E_0}{\sqrt{\left(\frac{1 - LC\omega^2}{RC\omega}\right)^2 + 1}},$$

$$\phi = -\text{Arg} \left( \frac{iR\omega E_0}{P(i\omega)} \right) = -\text{Arg} \left( \frac{i}{P(i\omega)} \right) = -\tan^{-1} \left( \frac{1 - LC\omega^2}{RC\omega} \right),$$

where, since the complex number  $RC\omega + i(1 - LC\omega^2)$  is in the 1st or 4th quadrants,  $\phi$  is between  $-\pi/2$  and  $\pi/2$ .

**(b)** Except for the fact that  $C$  corresponds to  $1/k$  we get the same answer as the previous problems.

As  $L$  increases the amplitude peak moves to the left and the graph gets a little spikier.

As  $R$  decreases the peak doesn't move and the amplitude graph gets spikier.

As  $C$  increases the peak moves to the left.

**(c)** One possibility is  $L = 3, C = .33, R = .4$ . In any case,  $LC = 1$ . The smaller  $R$  is the less of the  $\omega_2$  frequency signal gets through. In general, the smaller the value of  $R$  the smaller the pass-band of the filter.

**(d)** As  $C$  varies the spike in the amplitude graph moves. Thus changing the frequency that can pass through the filter.

**(e)** Without damping or forcing the DE is  $LI'' + \frac{1}{C}I = 0 \Rightarrow I'' + \frac{1}{LC}I = 0 \Rightarrow$  resonant frequency is  $\omega_0 = 1/\sqrt{LC}$ .

The boxed formula for  $A$  in part (a) shows that  $A$  is maximized when the term under the square root is minimized. This happens when the term in parentheses is 0, i.e. when  $LC\omega^2 - 1 = 0 \Leftrightarrow \omega = 1/\sqrt{LC} = \omega_0$ .

MIT OpenCourseWare  
<http://ocw.mit.edu>

18.03SC Differential Equations  
Fall 2011

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.