

Summary from previous lecture

- Laplace transform

$$\mathcal{L}[f(t)] \equiv F(s) = \int_{0^-}^{+\infty} f(t)e^{-st} dt.$$



$$\mathcal{L}[\dot{f}(t)] = sF(s) - f(0^-).$$

$$\mathcal{L}[u(t)] \equiv U(s) = \frac{1}{s}.$$

$$\mathcal{L}\left[\int_{0^-}^t f(\xi) d\xi\right] = \frac{F(s)}{s}.$$


$$\mathcal{L}[e^{-at}] = \frac{1}{s+a}.$$

- Transfer functions and impedances

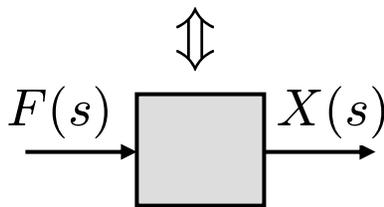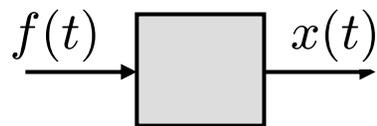

$$\text{TF}(s) = \frac{X(s)}{F(s)}$$

$$Z(s) = \frac{F(s)}{X(s)}$$

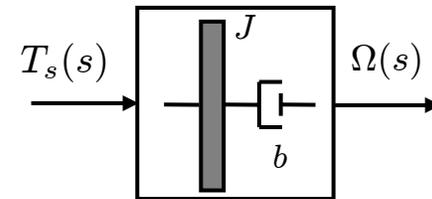

$$\text{TF}(s) := \frac{\Omega(s)}{T_s(s)} = \frac{1}{Js + b}.$$

$$Z_J = Js; \quad Z_b = b; \quad \text{TF}(s) = \frac{1}{Z_J + Z_b}$$

Goals for today

- Dynamical variables in electrical systems:
 - charge,
 - current,
 - voltage.
- Electrical elements:
 - resistors,
 - capacitors,
 - inductors,
 - amplifiers.
- Transfer Functions of electrical systems (networks)
- **Next lecture (Friday):**
 - DC motor (electro-mechanical element) model
 - DC motor Transfer Function

Electrical dynamical variables: charge, current, voltage

charge q


Coulomb [Cb]

charge flow \equiv current $i(t)$


Ampère [A] = [Cb]/[sec]

voltage (*aka* potential) $v(t)$

Volt [V]

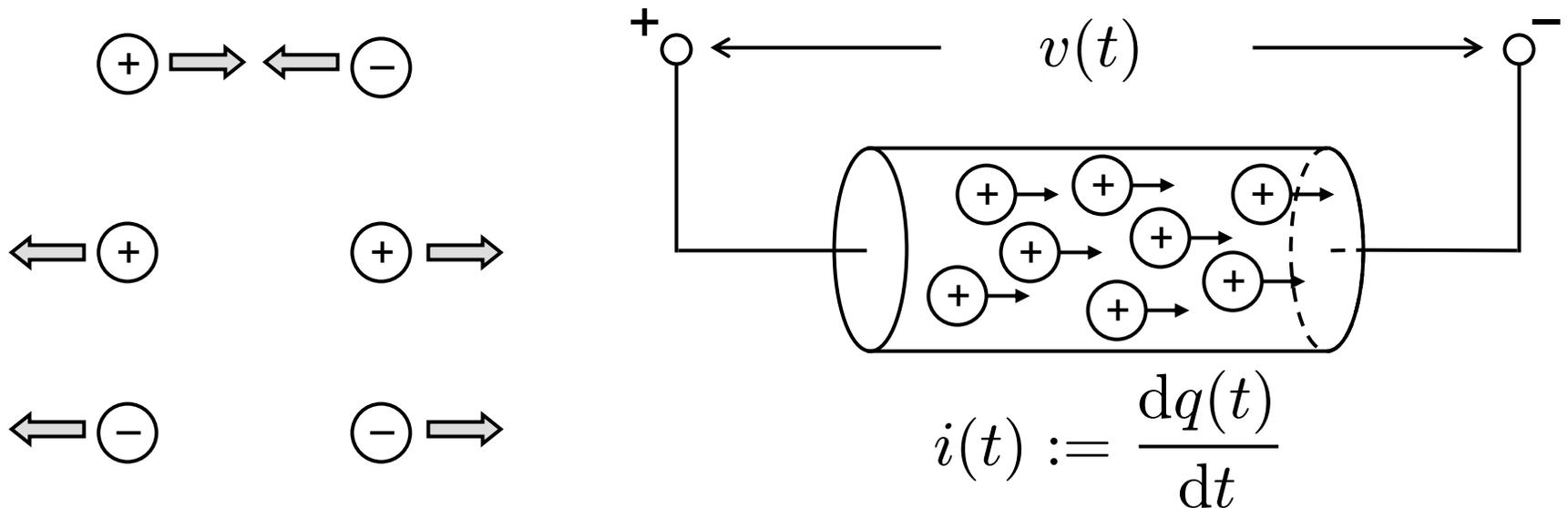

Electrical resistance

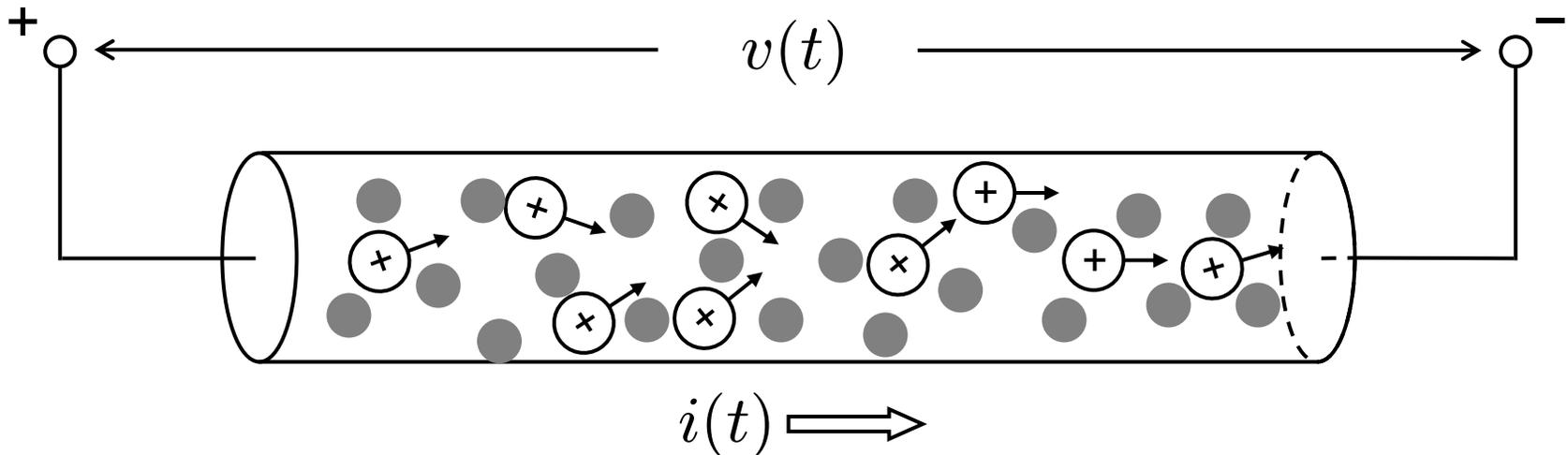


- Collisions between the mobile charges and the material fabric (ions, generally disordered) lead to energy dissipation (loss). As result, energy must be expended to generate current along the resistor; i.e., the current flow requires application of potential across the resistor

$$v(t) = Ri(t) \Rightarrow V(s) = RI(s) \Rightarrow \frac{V(s)}{I(s)} = R \equiv Z_R$$


- The quantity $Z_R=R$ is called the resistance (unit: Ohms, or Ω)
- The quantity $G_R=1/R$ is called the conductance (unit: Mhos or Ω^{-1})

Capacitance

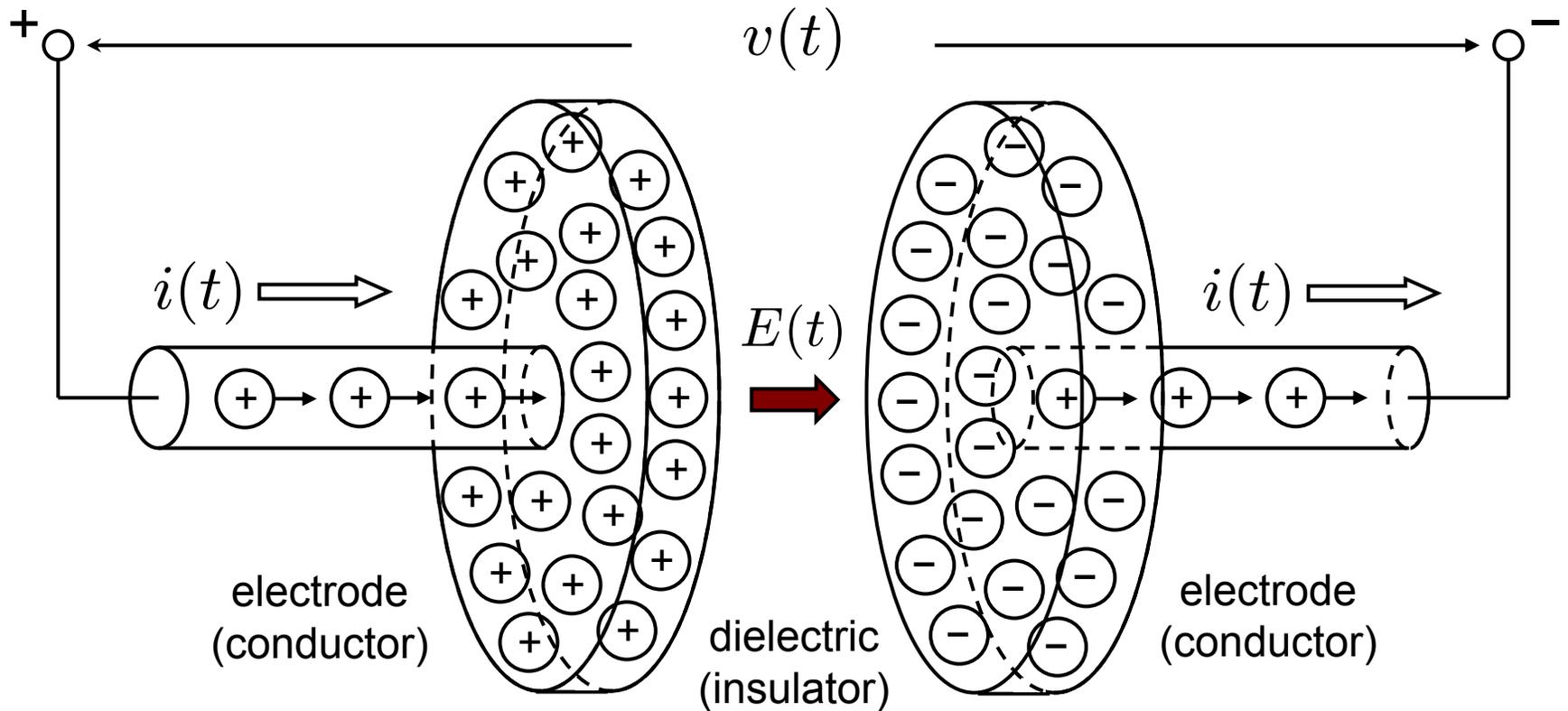


- Since similar charges repel, the potential v is necessary to prevent the charges from flowing away from the electrodes (discharge)
- Each change in potential $v(t+\Delta t)=v(t)+\Delta v$ results in change of the energy stored in the capacitor, in the form of charges moving to/away from the electrodes (\leftrightarrow change in electric field)

Capacitance

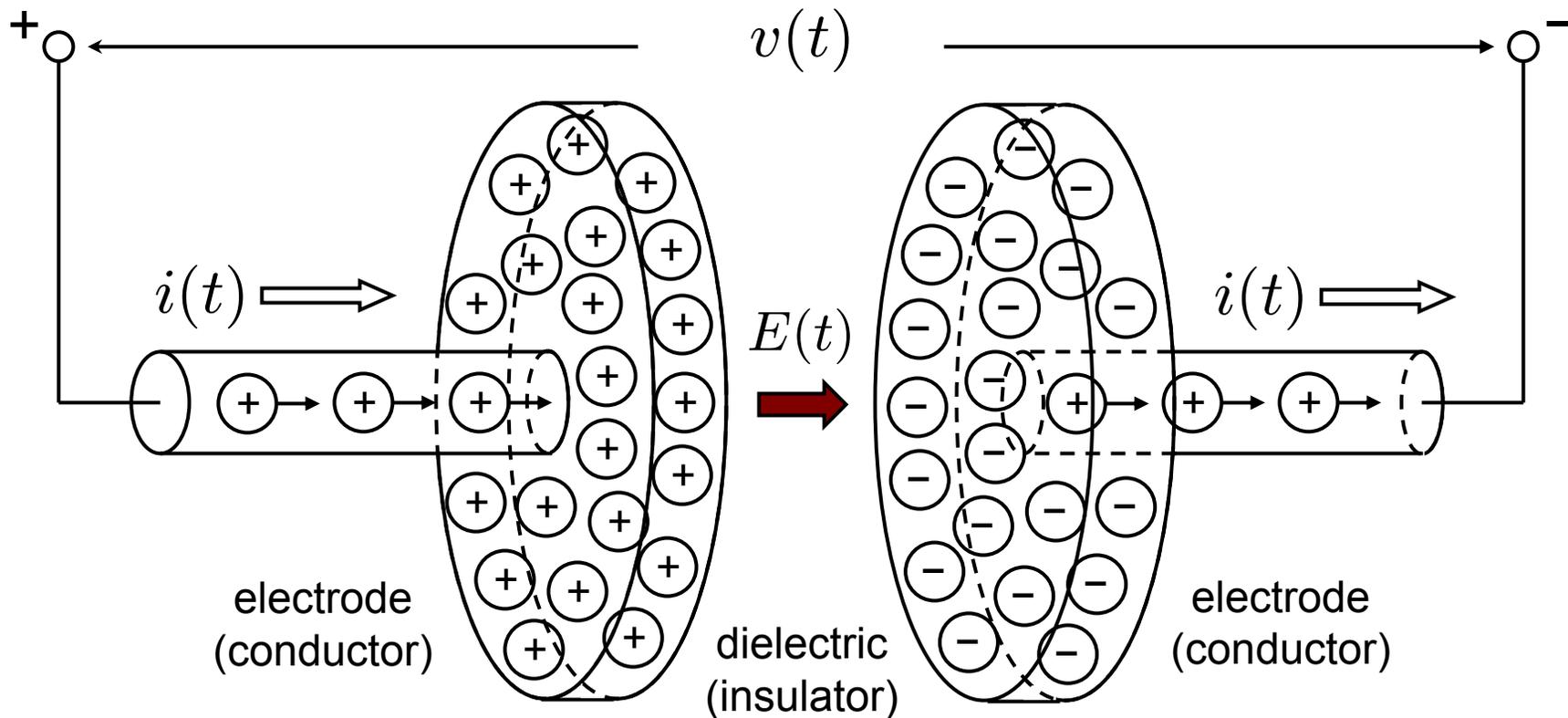

- Capacitance C : $q(t) = Cv(t) \Rightarrow \frac{dq(t)}{dt} \equiv i(t) = C \frac{dv(t)}{dt}$
- in Laplace domain: $I(s) = CsV(s) \Rightarrow \frac{V(s)}{I(s)} \equiv Z_C(s) = \frac{1}{Cs}$

Inductance

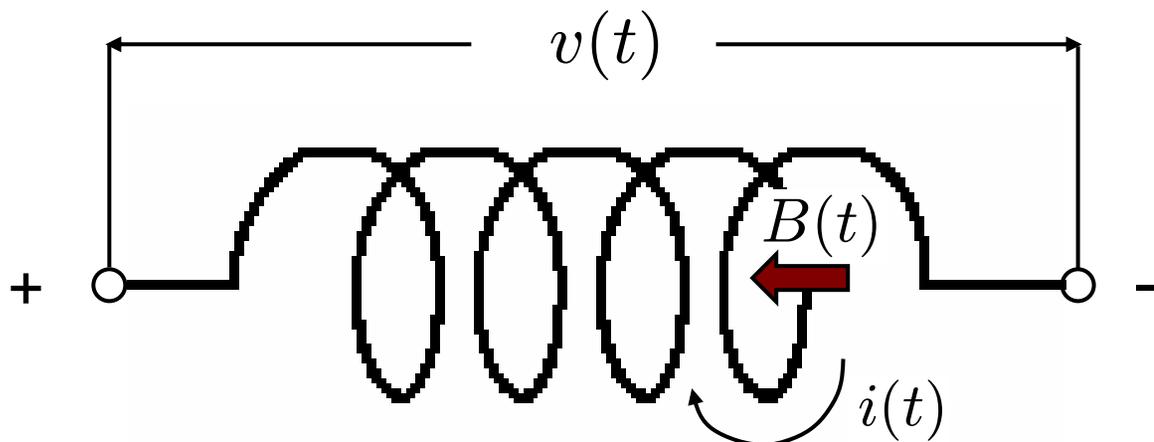

- Current flow i around a loop results in magnetic field B pointing normal to the loop plane. The magnetic field counteracts changes in current; therefore, to effect a change in current $i(t+\Delta t)=i(t)+\Delta i$ a potential v must be applied (*i.e.*, energy expended)

- Inductance L :
$$v(t) = L \frac{di(t)}{dt}$$


- in Laplace domain:
$$V(s) = LsI(s) \Rightarrow \frac{V(s)}{I(s)} \equiv Z_L(s) = Ls$$

Summary: passive electrical elements; Sources


Table removed due to copyright restrictions.

Please see: Table 2.3 in Nise, Norman S. *Control Systems Engineering*. 4th ed. Hoboken, NJ: John Wiley, 2004.

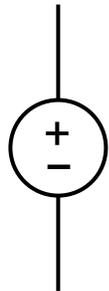Electrical inputs: voltage source, current source




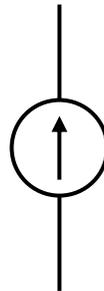Voltage source:
 $v(t)$ independent
of current through.




Current source:
 $i(t)$ independent
of voltage across.

Ground:
potential reference

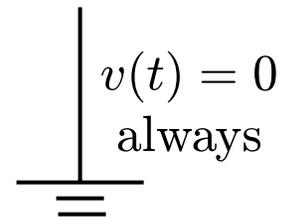

Combining electrical elements: networks


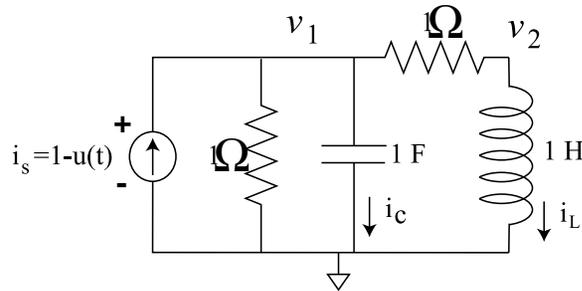


Courtesy of Prof. David Trumper. Used with permission.




Network analysis relies on two physical principles

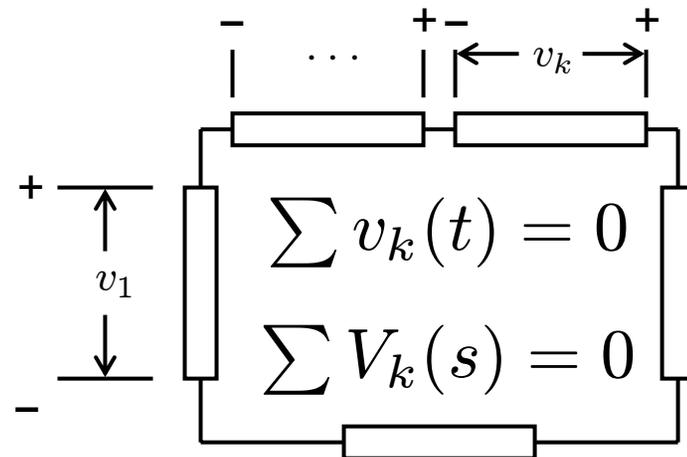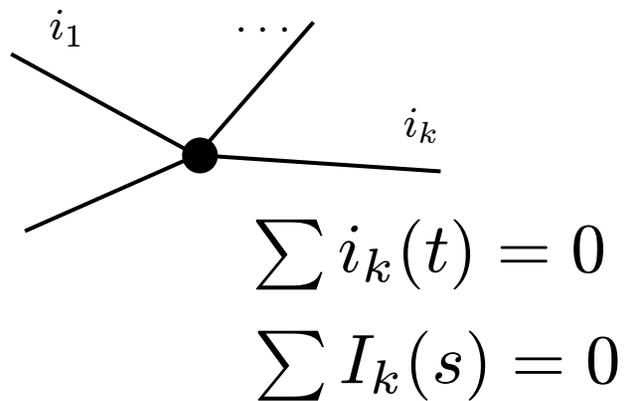- Kirchhoff Current Law (KCL)
 - charge conservation
- Kirchhoff Voltage Law (KVL)
 - energy conservation



Impedances in series and in parallel

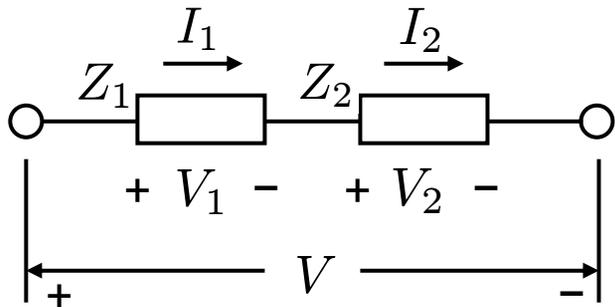

Impedances **in series**

$$\text{KCL: } I_1 = I_2 \equiv I.$$



$$\text{KVL: } V = V_1 + V_2.$$

From definition of impedances:

$$Z_1 = \frac{V_1}{I_1}; \quad Z_2 = \frac{V_2}{I_2}.$$

Therefore, equivalent circuit has
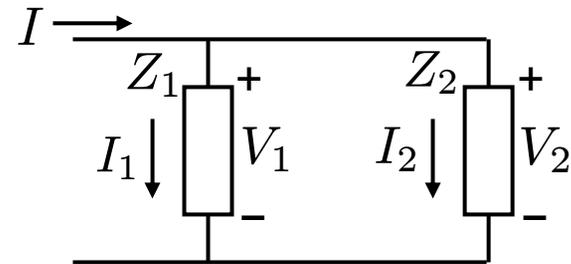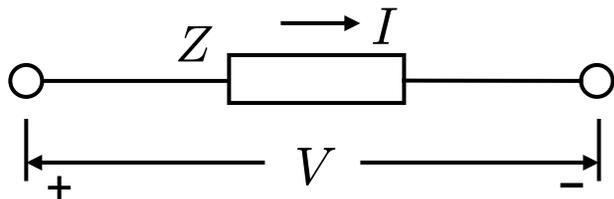
$$Z = Z_1 + Z_2 \left(\Leftrightarrow \frac{1}{G} = \frac{1}{G_1} + \frac{1}{G_2} \right)$$



Impedances **in parallel**

$$\text{KCL: } I = I_1 + I_2.$$


$$\text{KVL: } V_1 + V_2 \equiv V.$$

From definition of impedances:


$$Z_1 = \frac{V_1}{I_1}; \quad Z_2 = \frac{V_2}{I_2}.$$

Therefore, equivalent circuit has

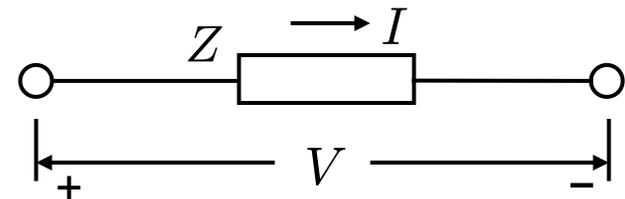
$$\frac{1}{Z} = \frac{1}{Z_1} + \frac{1}{Z_2} \left(\Leftrightarrow G = G_1 + G_2 \right)$$



The voltage divider

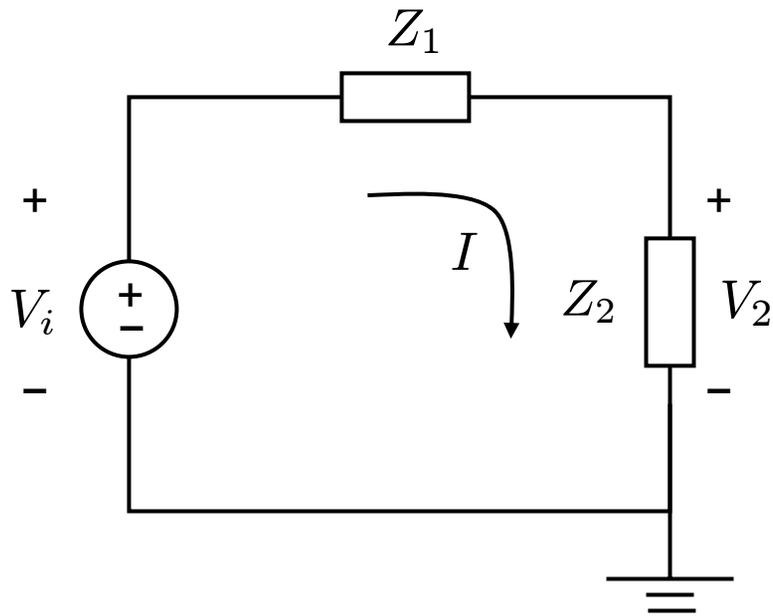

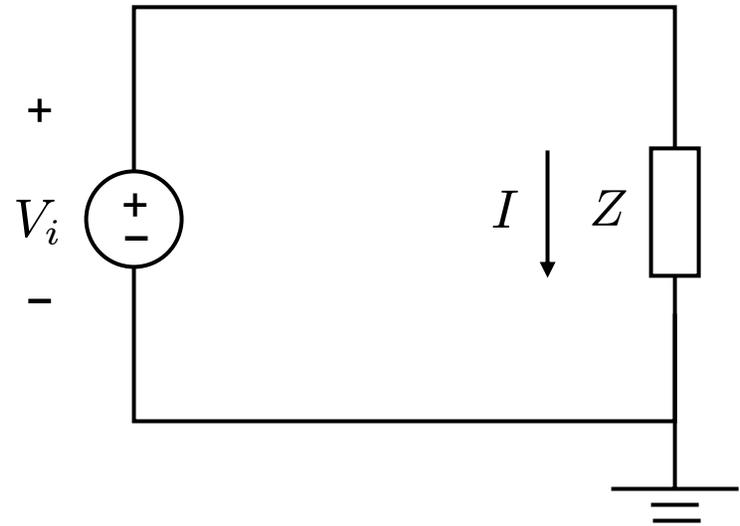Equivalent circuit for computing the current I .



Since the two impedances are in series, they combine to an equivalent impedance

$$Z = Z_1 + Z_2.$$


The current flowing through the combined impedance is

$$I = \frac{V}{Z}.$$


Therefore, the voltage drop across Z_2 is

$$V_2 = Z_2 I = Z_2 \frac{V}{Z} \Rightarrow \frac{V_2}{V_i} = \frac{Z_2}{Z_1 + Z_2}.$$


Block diagram & Transfer Function

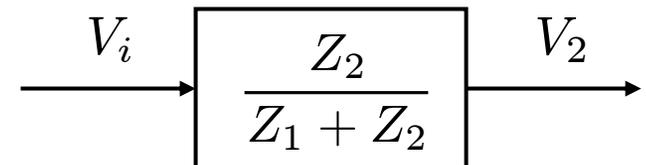

Example: the RC circuit

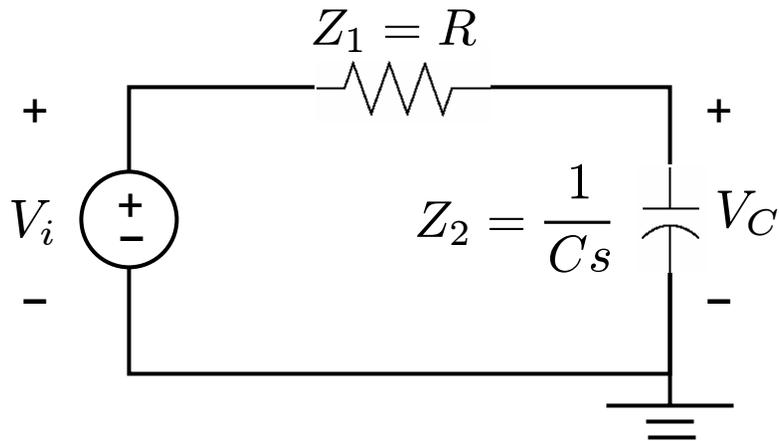

Block diagram & Transfer Function

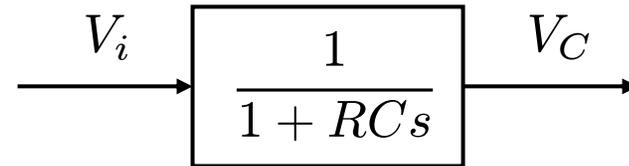


We recognize the voltage divider configuration, with the voltage across the capacitor as output. The transfer function is obtained as

$$\text{TF}(s) = \frac{V_C(s)}{V_i(s)} = \frac{1/Cs}{R + 1/Cs} = \frac{1}{1 + RCs} = \frac{1}{1 + \tau s},$$

where $\tau \equiv RC$. Further, we note the similarity to the transfer function of the rotational mechanical system consisting of a motor, inertia J and viscous friction coefficient b that we saw in Lecture 3. [The transfer function was $1/b(1 + \tau s)$, *i.e.* identical within a multiplicative constant, and the time constant τ was defined as J/b .] We can use the analogy to establish properties of the RC system without re-deriving them: e.g., the response to a step input $V_i = V_0 u(t)$ (step response) is


$$V_C(t) = V_0 \left(1 - e^{-t/\tau}\right) u(t), \quad \text{where now } \tau = RC.$$

Interpretation of the *RC* step response

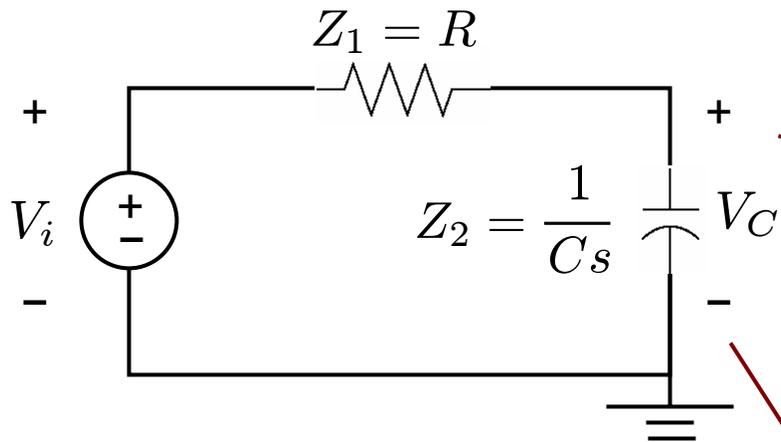


$$V_C(t) = V_0 (1 - e^{-t/\tau}) u(t), \quad \tau = RC.$$
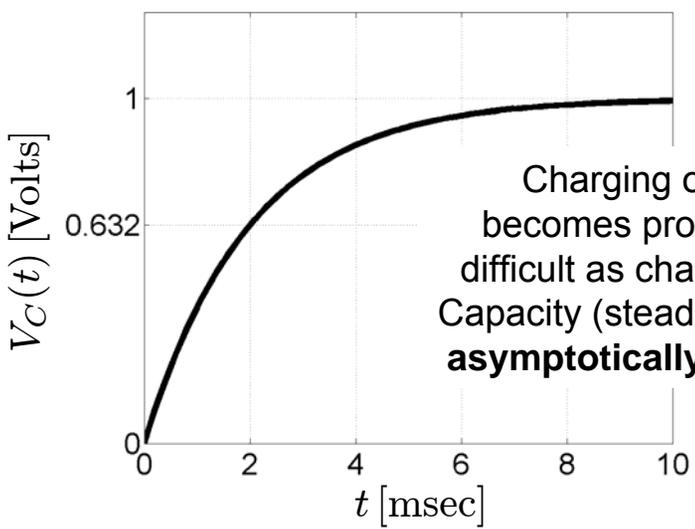
$$V_0 = 1 \text{ Volt} \quad R = 2k\Omega \quad C = 1\mu F$$



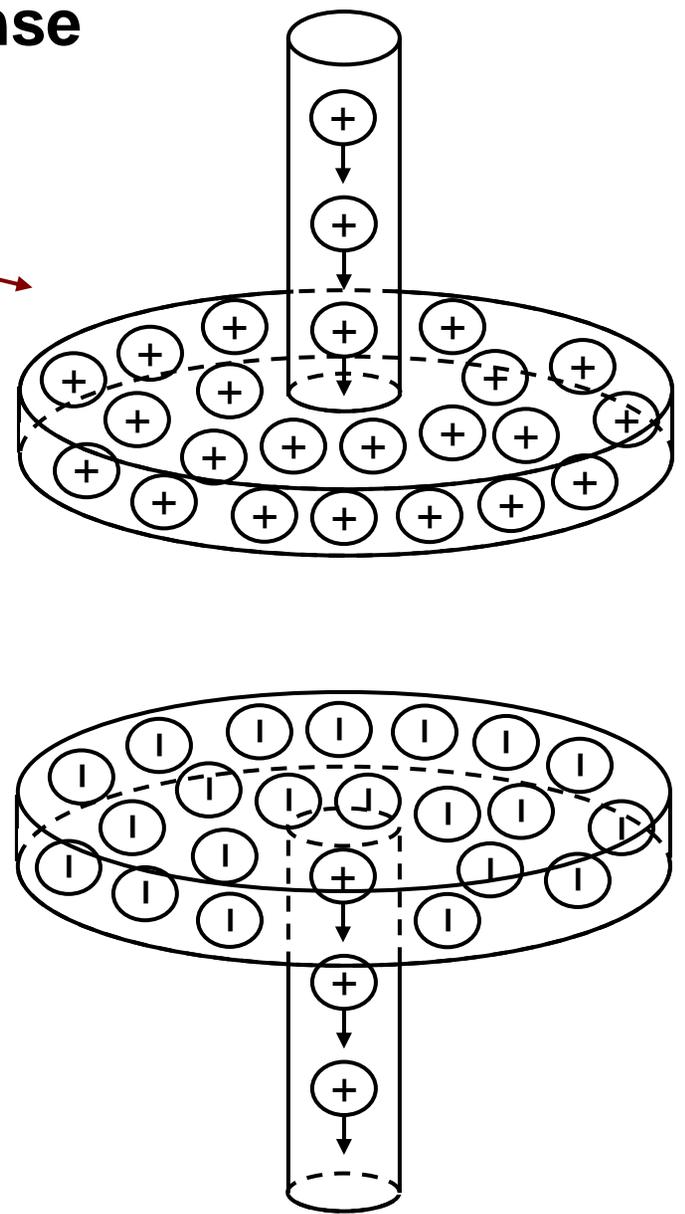Charging of a capacitor:
 becomes progressively more
 difficult as charges accumulate.
 Capacity (steady-state) is reached
asymptotically ($V_C \rightarrow V_0$ as $t \rightarrow \infty$)



Example: RLC circuit with voltage source

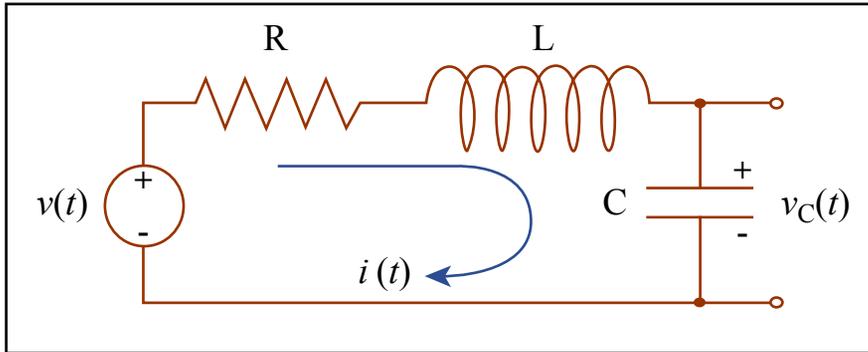


Figure by MIT OpenCourseWare.

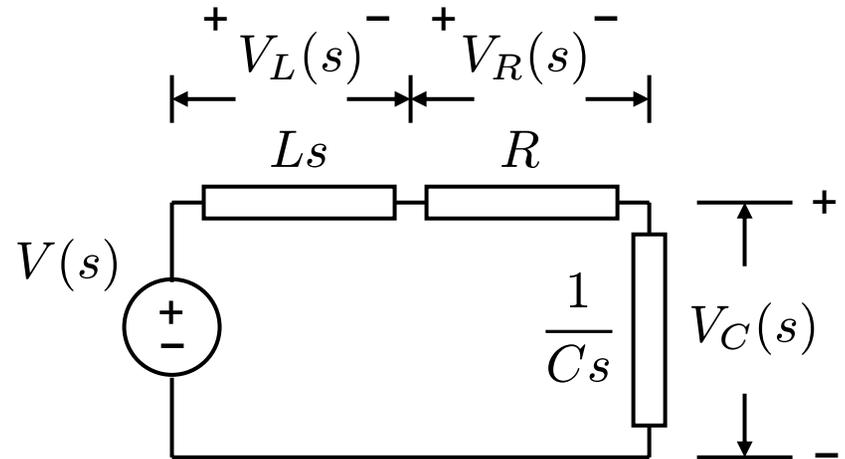


Figure 2.3

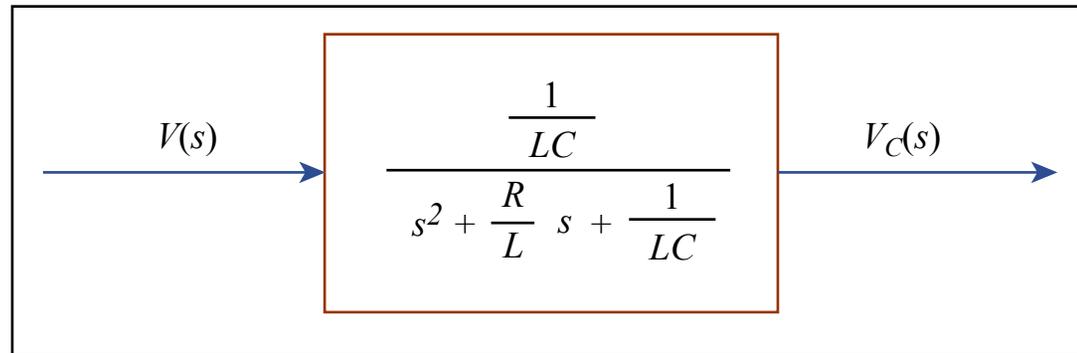


Figure 2.4

Figure by MIT OpenCourseWare.

Example: two-loop network

Images removed due to copyright restrictions.

Please see: Fig. 2.6 and 2.7 in Nise, Norman S. *Control Systems Engineering*. 4th ed. Hoboken, NJ: John Wiley, 2004.

The operational amplifier (op-amp)

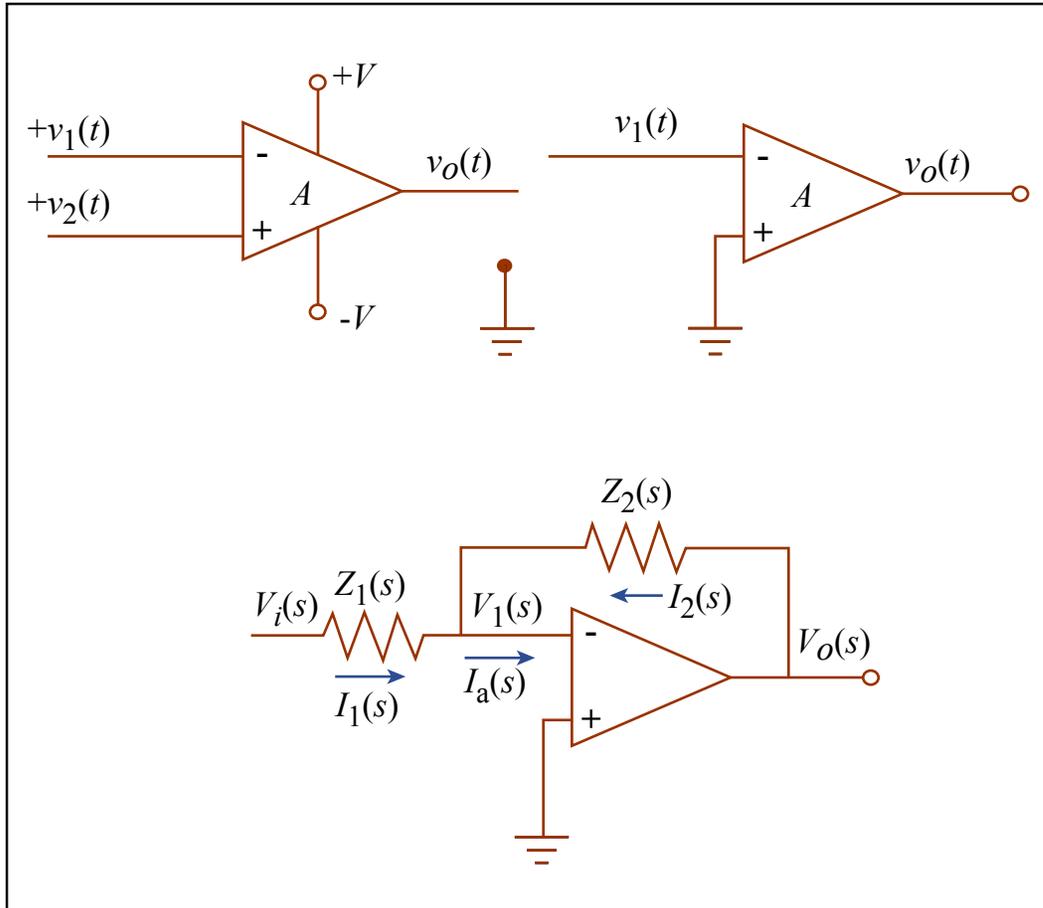


Figure 2.10

Figure by MIT OpenCourseWare.

(a) Generally, $v_o = A(v_2 - v_1)$, where A is the amplifier **gain**.

(b) When v_2 is grounded, as is often the case in practice, then $v_o = -Av_1$. (Inverting amplifier.)

(c) Often, A is large enough that we can approximate $A \rightarrow \infty$.

Rather than connecting the input directly, the op-amp should then instead be used in the **feedback** configuration of Fig. (c).

We have:

$$V_1 = 0; \quad I_a = 0$$

(because V_o must remain finite) therefore

$$I_1 + I_2 = 0;$$

$$V_i - V_1 = V_i = I_1 Z_1;$$

$$V_o - V_1 = V_o = I_2 Z_2.$$

Combining, we obtain

$$\frac{V_o(s)}{V_i(s)} = -\frac{Z_2(s)}{Z_1(s)}.$$