

Goals for today

- The operational amplifier
 - input-output relationships
 - feedback configuration
- More about zeros
 - zero on the right-half plane: non-minimum phase response
 - Zero-pole cancellation
- Next week
 - Block diagram operations
 - Analysis of a simple feedback system

The operational amplifier (op-amp)

(a) Generally, $v_o = A(v_2 - v_1)$, where A is the amplifier **gain**.

(b) When v_2 is grounded, as is often the case in practice, then $v_o = -Av_1$. (Inverting amplifier.)

(c) Often, A is large enough that we can approximate $A \rightarrow \infty$.

Rather than connecting the input directly, the op-amp should then instead be used in the **feedback** configuration of Fig. (c).

We have:

$$V_1 = 0; \quad I_a = 0$$

(because V_o must remain finite) therefore

$$I_1 + I_2 = 0;$$

$$V_i - V_1 = V_i = I_1 Z_1;$$

$$V_o - V_1 = V_o = I_2 Z_2.$$

Combining, we obtain

$$\frac{V_o(s)}{V_i(s)} = -\frac{Z_2(s)}{Z_1(s)}.$$

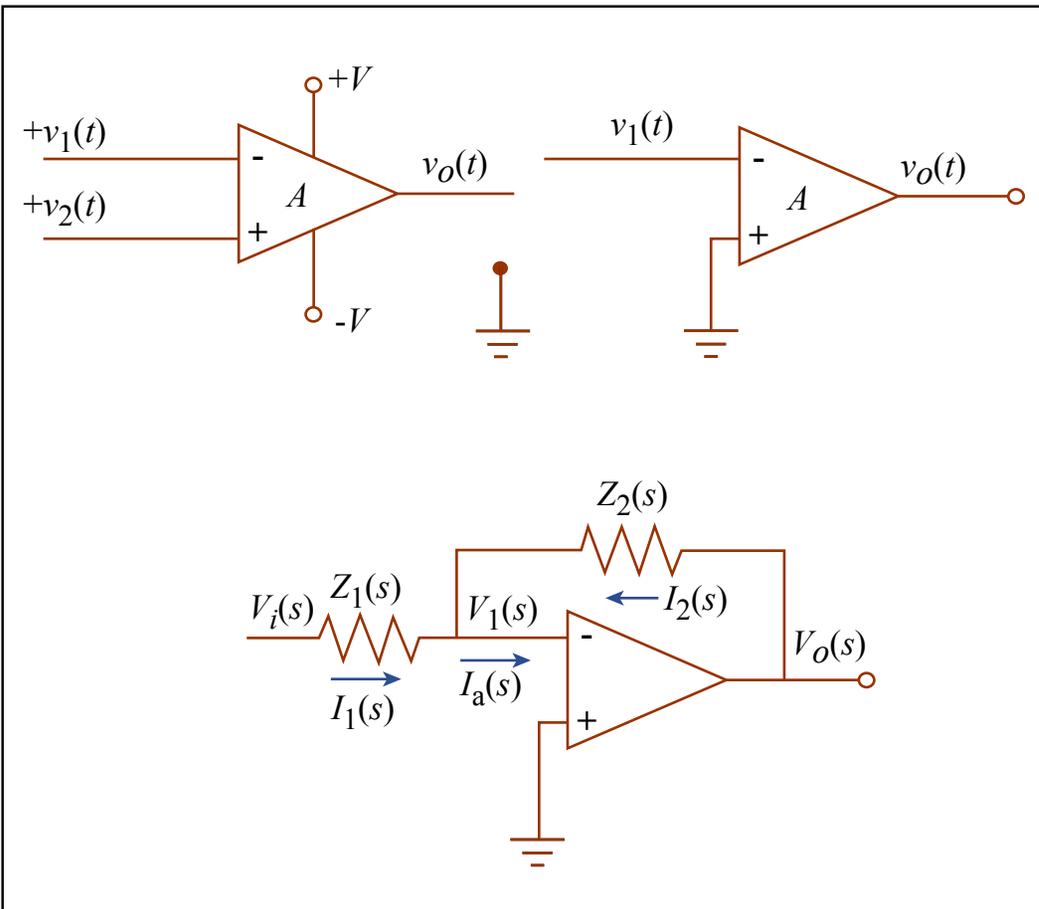


Figure by MIT OpenCourseWare.

Figure 2.10
(see also Lecture 04 – page 16)

Example: PID controller

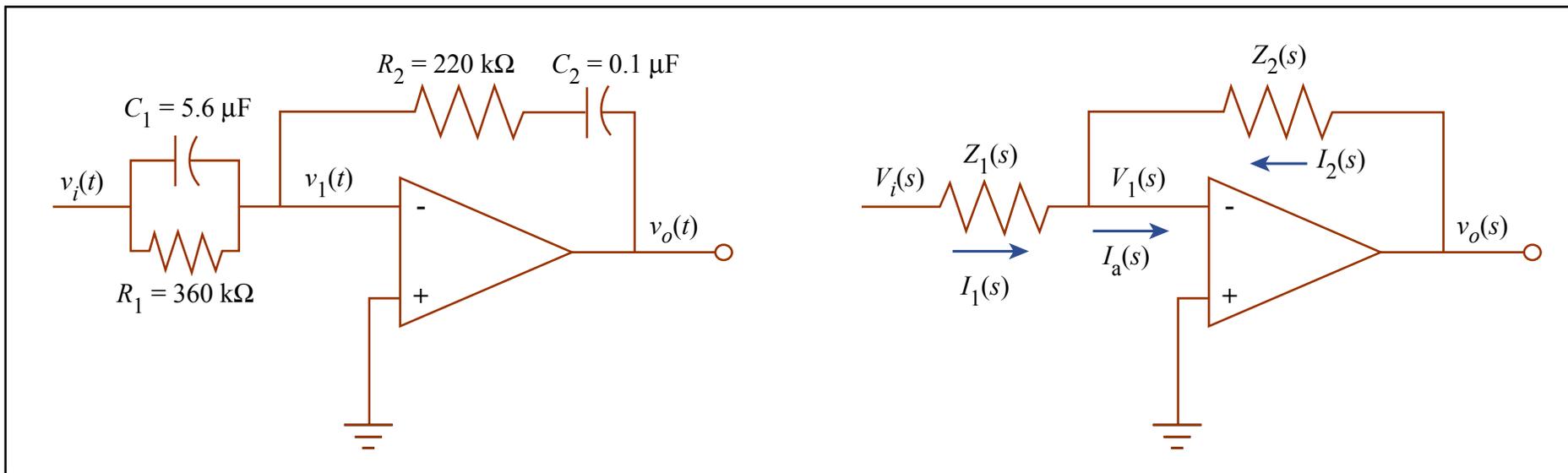


Figure by MIT OpenCourseWare.

Figure 2.11

Figure 2.10

Equivalent impedances:

(R_1 , C_1 connected in parallel)

$$\frac{1}{Z_1(s)} = \frac{1}{R_1} + C_1 s \Rightarrow Z_1(s) = \frac{R_1}{1 + R_1 C_1 s} = \frac{360 \times 10^3}{1 + 2.016s};$$

(R_2 , C_2 connected in series)

$$Z_2(s) = R_2 + \frac{1}{C_2 s} = 220 \times 10^3 + \frac{1}{10^{-7} s}.$$

⇒ Transfer Function:

$$\frac{V_o(s)}{V_i(s)} = -1.232 \frac{s^2 + 45.95s + 22.55}{s}.$$

Example: *all-pass filter*


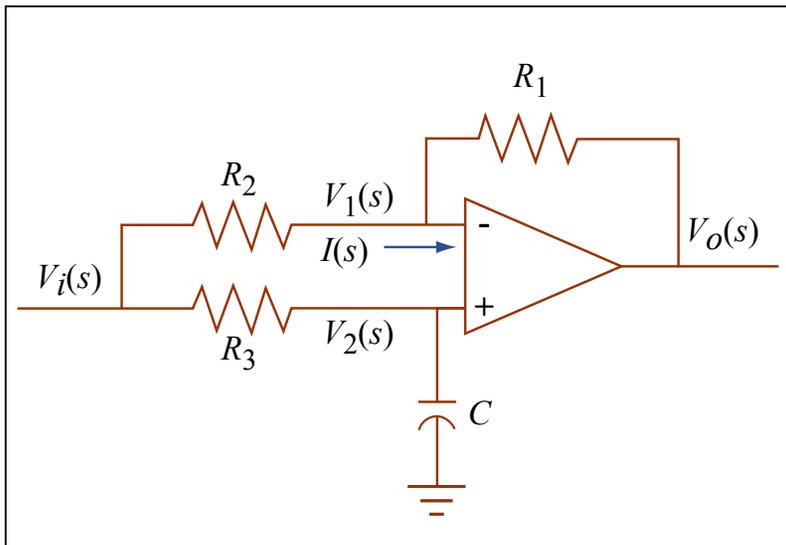


Figure by MIT OpenCourseWare.

Transfer function:
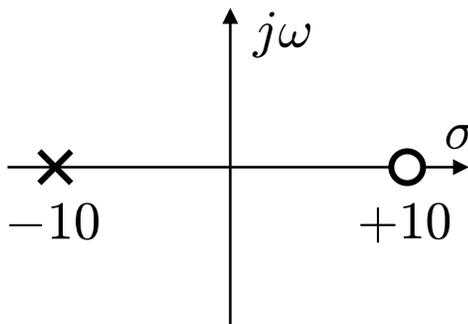
$$\frac{V_o(s)}{V_i(s)} = -\frac{R_1}{R_2} \frac{s - \frac{R_2}{R_1 R_3 C}}{s + \frac{1}{R_3 C}}$$



Substituting $R_1 = R_2$, $R_3 = 100\text{k}\Omega$, $C = 1\mu\text{F}$,

$$\frac{V_o(s)}{V_i(s)} = -\frac{s - 10}{s + 10} \quad \text{zero in the r.h.p.}$$

Step response without zero:

$$C_o(s) = -\frac{1}{s(s+10)} = -\frac{1/10}{s} + \frac{1/10}{s+10}$$

$$c_0(t) = -\frac{1}{10} (1 - e^{-10t}) u(t).$$

Images removed due to copyright restrictions.
Please see Fig. 4.28 in Nise, Norman S. *Control Systems Engineering*.
4th ed. Hoboken, NJ: John Wiley, 2004.

Step response:

$$\begin{aligned} C(s) &= -\frac{s - 10}{s(s + 10)} \\ &= \frac{1}{s} - \frac{2}{s + 10} \Rightarrow \\ c(t) &= (1 - 2e^{-10t}) u(t). \end{aligned}$$

Non-minimum phase system

Nonminimum-phase response

Consider a system without a zero, whose step response is $C_o(s)$ and recall that the effect of the zero is $C(s) = (s + a)C_o(s) = sC_o(s) + aC_o(s)$.

In the time domain, $c(t) = \dot{c}_o(t) + ac_o(t)$. Therefore, the system response with the zero is the sum of the derivative of the original response plus the original response amplified by a gain equal to a (“proportional term.”)

If $a < 0$ and the derivative term $\dot{c}_o(t = 0)$ is larger than the proportional term $ac_o(t = 0)$, then the response will initially follow the derivative term in the *opposite direction* of the proportional term.

Images removed due to copyright restrictions.

Please see: Fig. 4.26 in Nise, Norman S. *Control Systems Engineering*. 4th ed. Hoboken, NJ: John Wiley, 2004.

Zero-pole cancellation

Compare the step responses

$$C_1(s) = \frac{26.25(s + 4)}{s(s + 3.5)(s + 5)(s + 6)}$$

$$C_2(s) = \frac{26.25(s + 4)}{s(s + 4.01)(s + 5)(s + 6)}$$


Partial fraction expansion yields

$$C_1(s) = \frac{1}{s} - \frac{3.5}{s + 5} + \frac{3.5}{s + 6} - \frac{1}{s + 3.5}$$


$$C_2(s) = \frac{0.87}{s} - \frac{5.3}{s + 5} + \frac{4.4}{s + 6} - \frac{0.033}{s + 4.01}$$

non-negligible

negligible

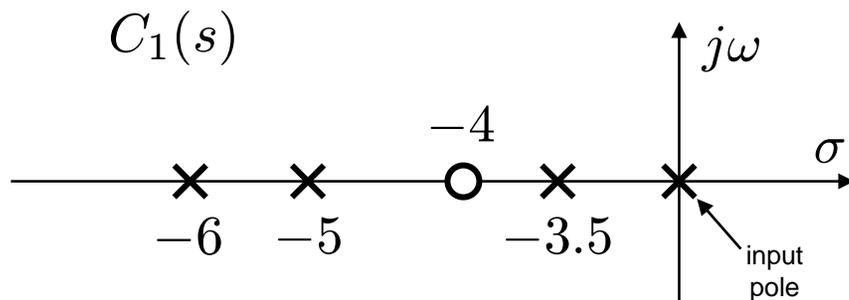

zero-pole cancellation does not occur

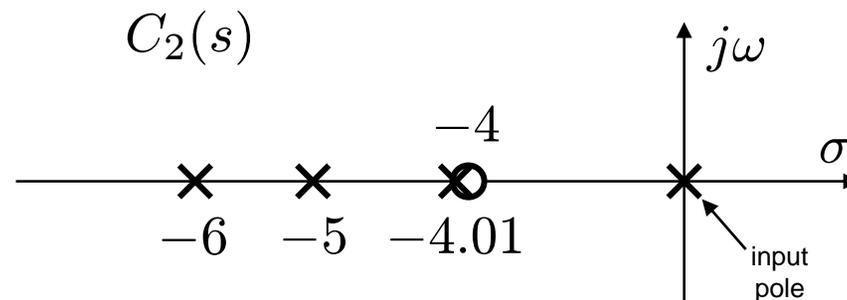

zero-pole cancellation occurs