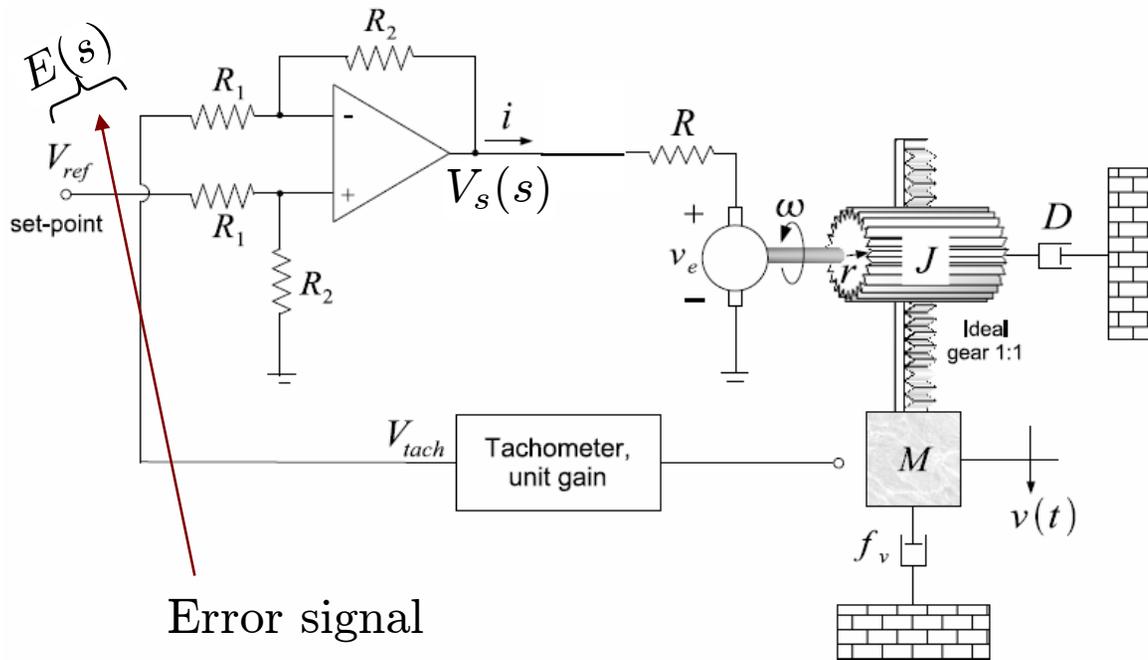


# This week's goals

- **Today**
  - Physical realization of compensators
- **Wednesday**
  - Proportional-Derivative compensator
  - Lead/Lag compensators
- **Friday**
  - Introduction to state space

# Differential amplifier as proportional controller



Controller gain


$$K = \frac{R_2}{R_1}$$

Recall the differential amplifier input-output relation


$$\begin{aligned} V_s(s) &= \frac{R_2}{R_1} (V_{ref}(s) - V(s)) \\ &= \frac{R_2}{R_1} E(s). \end{aligned}$$

Error signal

$$E(s) = V_{ref}(s) - V(s)$$

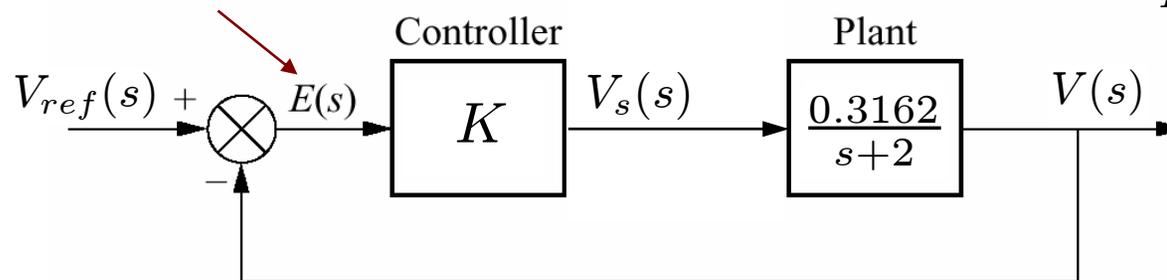
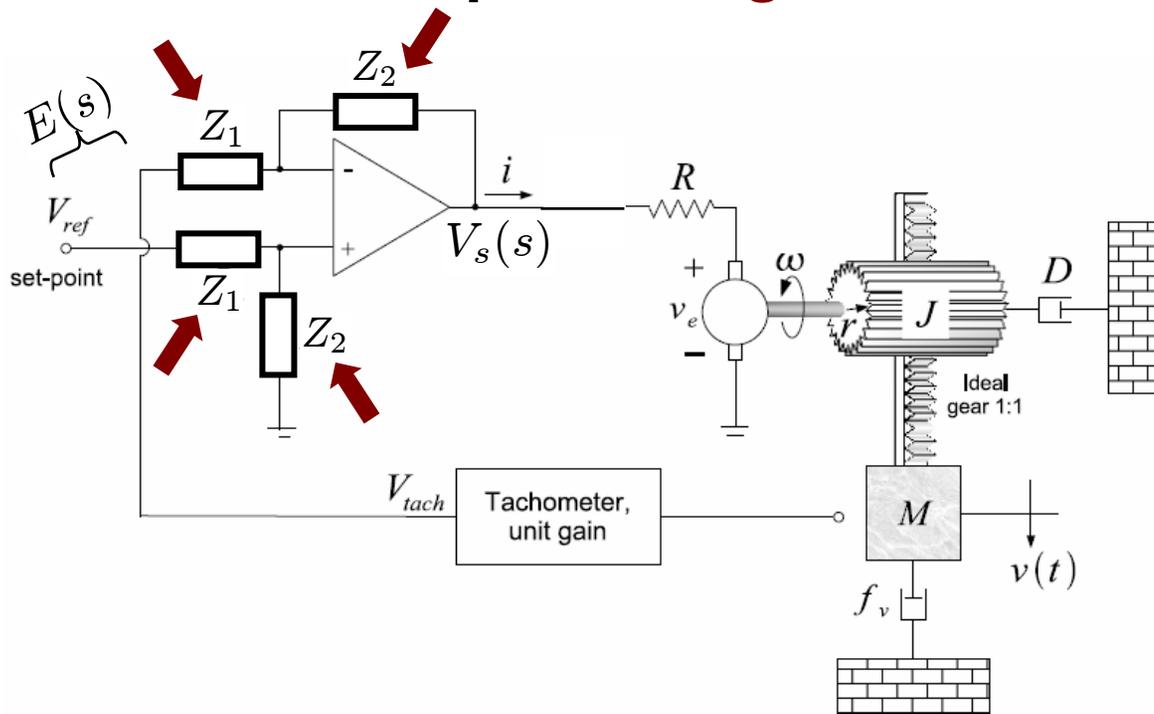
# Differential amplifier as *generic* controller





Input-output relation of differential amplifier with general impedances

$$V_s(s) = \frac{Z_2(s)}{Z_1(s)} (V_{ref}(s) - V(s))$$



$$= \frac{Z_2(s)}{Z_1(s)} E(s).$$

Controller transfer function

$$G_c(s) = \frac{Z_2(s)}{Z_1(s)}$$

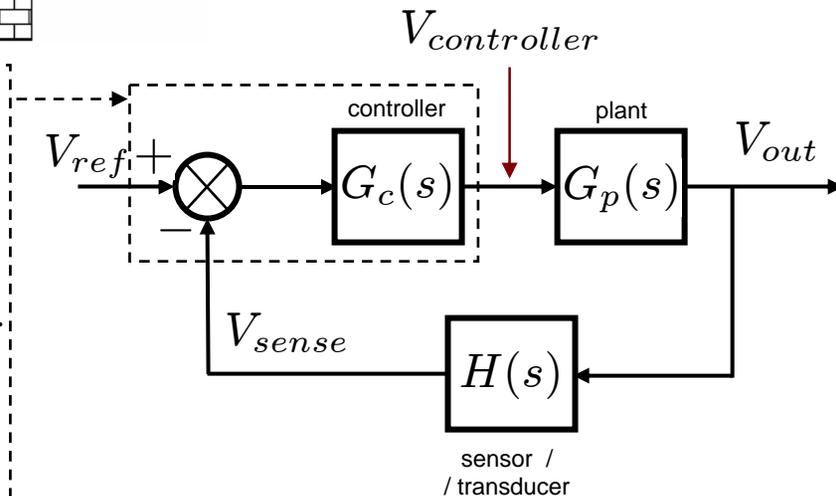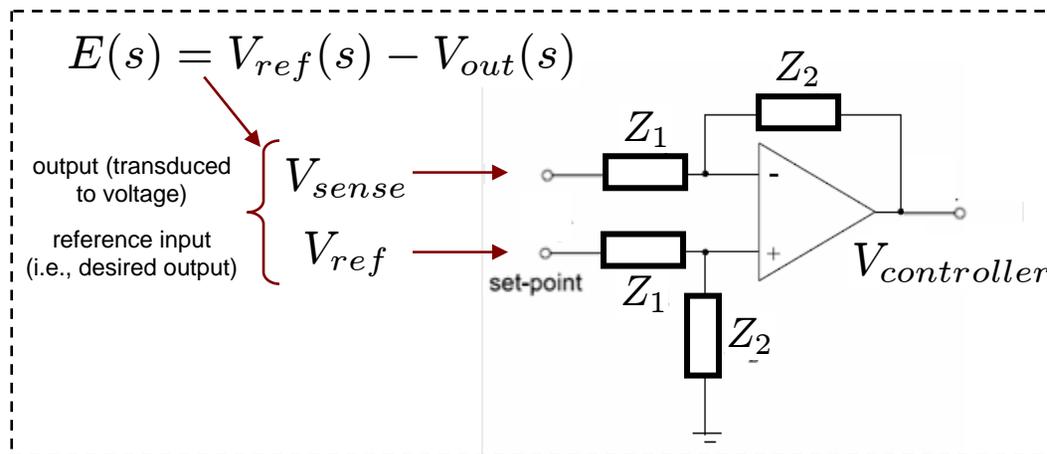

# Example 1: Ideal integral controller

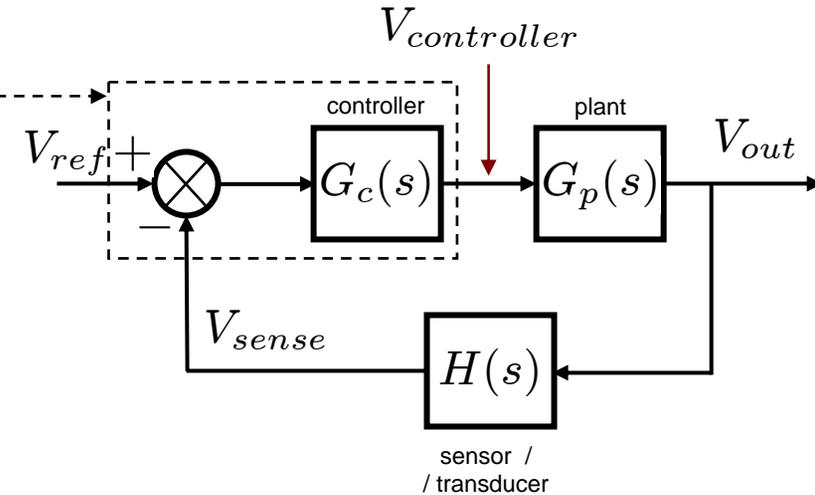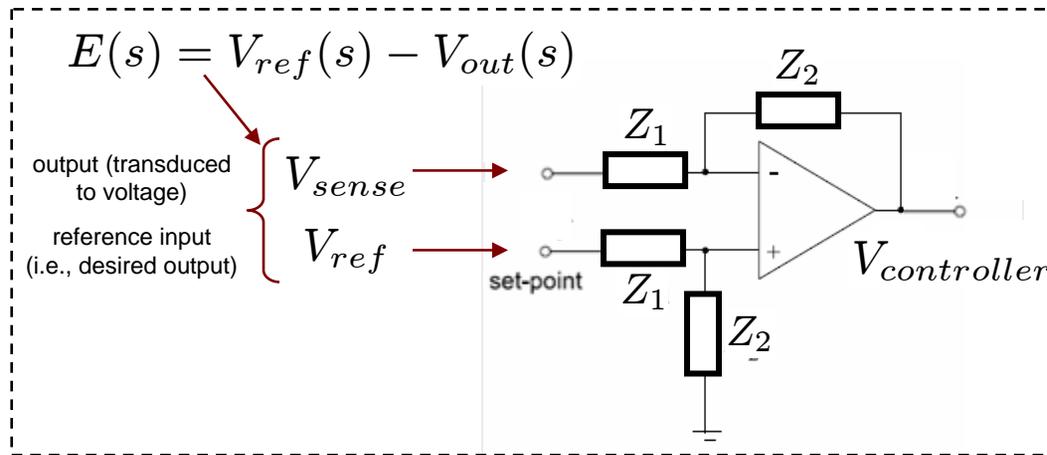





$$\boxed{Z_1} = R$$

$$\boxed{Z_2} = C$$

Controller transfer function

$$G_c(s) = \frac{Z_2(s)}{Z_1(s)} = \frac{1/(Cs)}{R} = \frac{1/(RC)}{s}$$
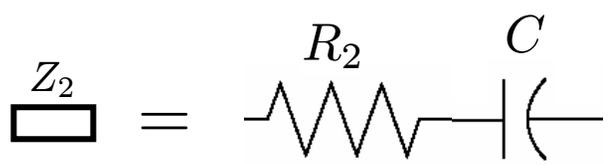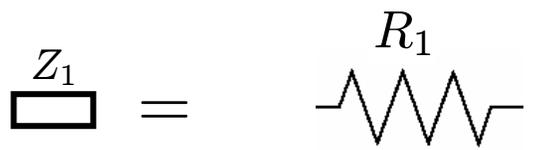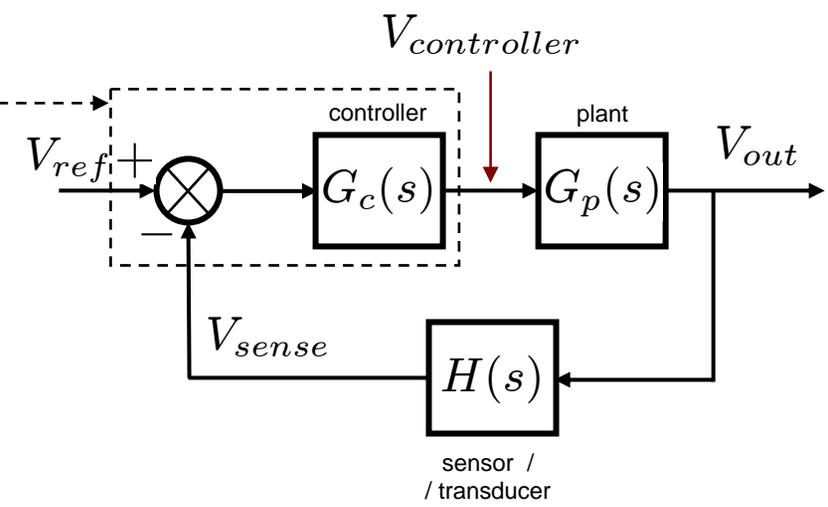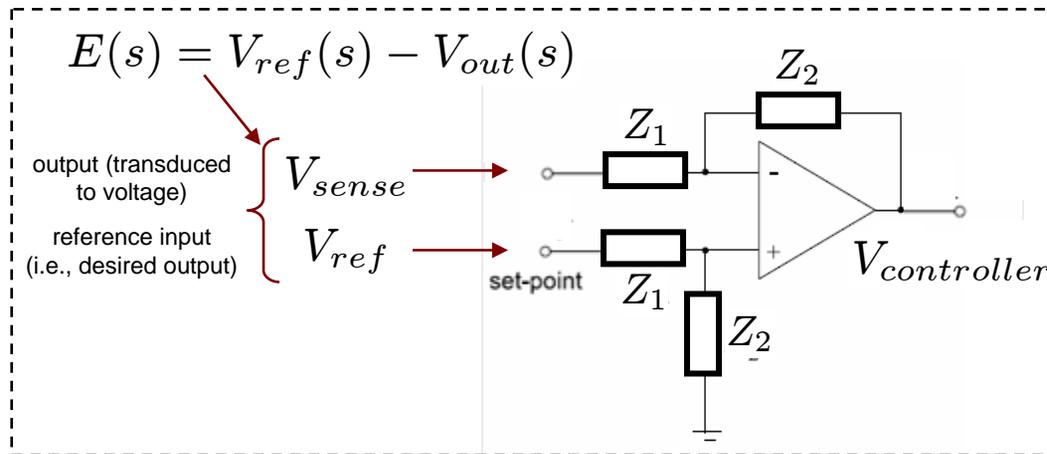
# Example 2: Proportional-integral controller







Controller transfer function

$$G_c(s) = \frac{Z_2(s)}{Z_1(s)} = \frac{R_2 + 1/(Cs)}{R_1} = \frac{R_2 s + 1/(R_2 C)}{R_1 s}$$

$$= K_p \frac{s + z}{s}, \quad \text{where } K_p = \frac{R_2}{R_1}, \quad z = \frac{1}{R_2 C}$$

$$= K_p + \frac{K_i}{s}, \quad \text{where } K_i = \frac{1}{R_1 C}$$
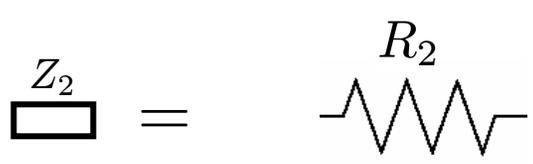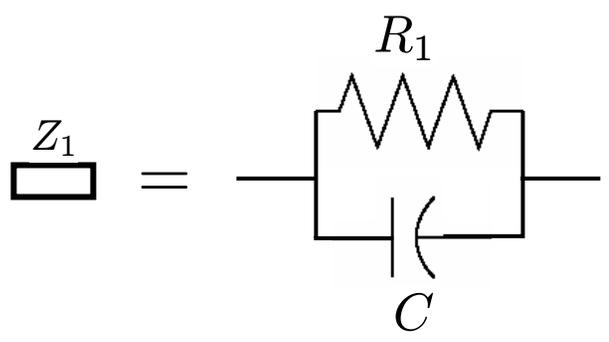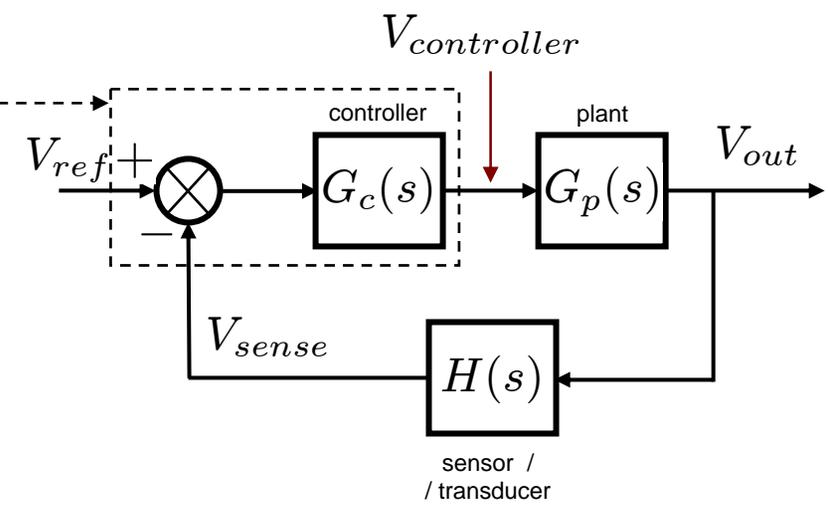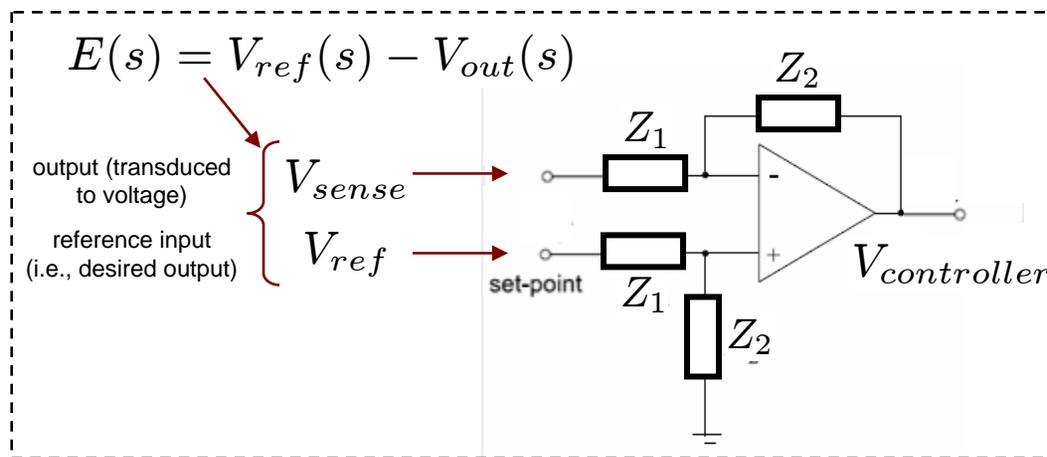
# Example 3: Proportional-derivative controller



Controller transfer function

$$G_c(s) = \frac{Z_2(s)}{Z_1(s)} = \frac{R_2}{R_1 / (1 + R_1 C s)} = \frac{R_2}{R_1} + R_2 C s$$

$$= K_p + K_d s, \quad \text{where } K_p = \frac{R_2}{R_1}, \quad K_d = R_2 C.$$