
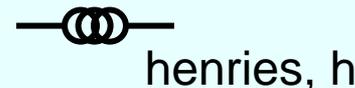
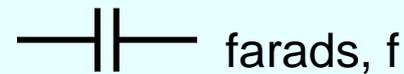


Electronics Essentials for 2.017

Reviewing Basics


- *Kirchoff's Voltage rule*: voltages V at a node are the same.
- *Kirchoff's Current rule*: sum of currents i flowing into and out of a node is zero.
- *Analogy*: Voltage is like fluid pressure, current is like fluid volumetric flow rate. The wire is like a pipe.
- Resistor R : $V = IR$,
 - Dissipation: Resistive Power $P = I^2R = V^2/R$
 - Analogy: viscous losses in pipe flow
- Capacitor C : $i = C dV/dt$
 - Analogy: a hydraulic accumulator
- Inductor H : $V = L di/dt$
 - Analogy: inertia of water in a pipe

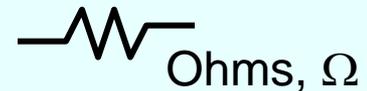

The Op-Amp

Two inputs (called inverting and non-inverting); one output.

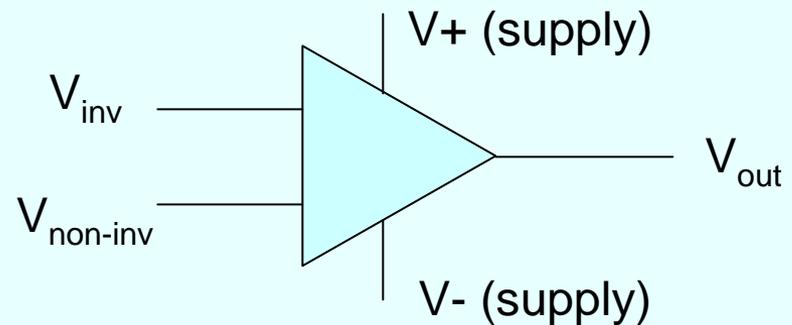The output voltage is a HUGE gain multiplied by the difference between the inputs.




Horiwitz's & Hill's golden rules:

a. The op-amp enforces (in proper use)

$$V_{inv} = V_{non-inv}$$

b. No current flows into the device at either input

Example Op-Amp: Adding a Voltage Bias

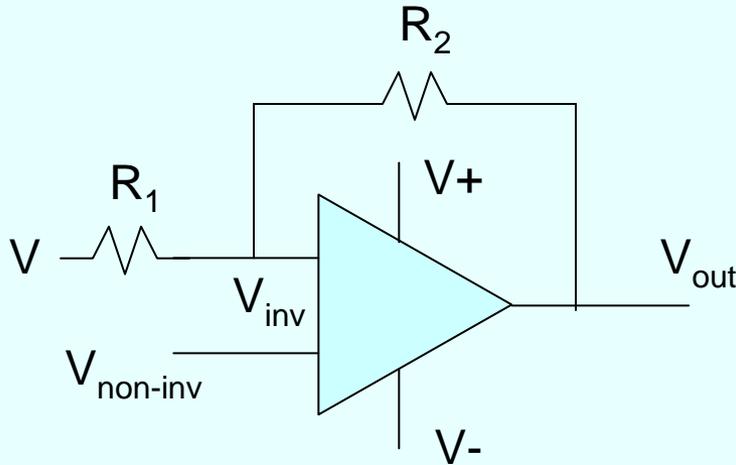

Voltage bias useful for bringing signal levels into the range of sensors.

The op-amp is discussed in detail by Horowitz and Hill, covering integrators, filters, etc.

$$(V - V_{inv})/R_1 = (V_{inv} - V_{out})/R_2 \quad \text{and} \\ V_{inv} = V_{non-inv} \rightarrow$$

$$VR_2 = V_{inv}(R_1 + R_2) - V_{out}R_1 \rightarrow$$

$$V_{out} = V_{non-inv} (R_1 + R_2)/R_1 - VR_2/R_1$$

Letting $R_1 = R_2$, then

$$V_{out} = 2V_{non-inv} - V$$


The circuit inverts the input V and adds on $2V_{non-inv}$

IF V_{non_inv} is ground, then V_{out} is just $-V$. This is just an inverting amplifier.

Serial Communications

- *How to transmit digital information fast and reliably over a few wires?*
- Examples: RS-232, RS-485, etc. refer to pins & wires
- A minimal case of RS-232 (DB25 connector is full case):
 - Asynchronous operation; both sides agree on BAUD rate
 - Three wires: send (TX), receive (RX), ground
 - No error checking! No flow control!

EXAMPLE using CMOS components:

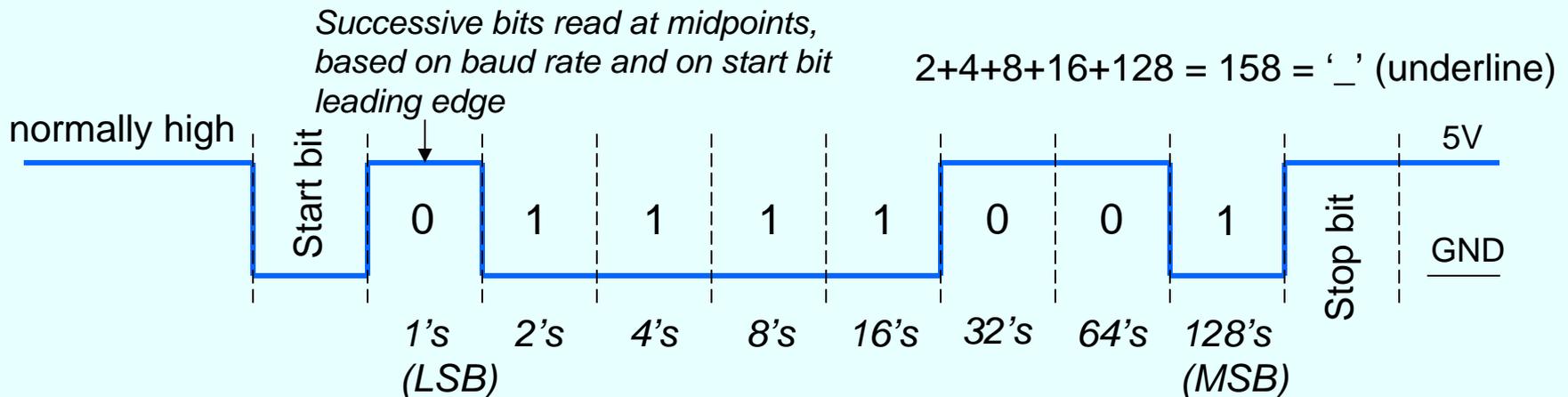

EXAMPLE: A GPS String

- Garmin GPS25 series – Smart embedded device!
- Similar to TT8's interface with you – I/O strings are passed through a serial port
- Reconfigurable through special commands
- Output at 1Hz
- String maintains exactly the same syntax: e.g.,

**\$GPRMC,hhmmss,V,
ddmm.mmmm,N,dddmm.mmmm,E,
000.0,000.0,ddmmyy,000.0,E,N,*XX<CR><LF>**

→ *73 chars appear as one line:*

\$GPRMC,hhmmss,V,ddmm.mmmm,N,dddmm.mmmm,E,000.0,000.0,ddmmyy,000.0,E,N,*XX

Serial devices communicate using characters encoded into bits. This includes upper- and lowercase letters, carriage returns and linefeeds, punctuation, etc. Characters are not numbers! E.g.,

```
char c = '7' ;  
char d[2] = '92' ;  
int n ;
```

The numerical value of **c** is [00110111] (binary) or 55 (decimal).

But because the ASCII characters '0','1','2','3','4','5','6','7','8', and '9' occur in order, making simple conversions is easy:

```
n = c - '0' ;
```


assigns to **n** the actual number 7. The ASCII character that goes with 7 is known as BEL – on many machines this will ring a bell if it is sent to the screen as a character! – **printf(“%c”,n) ;**

How to turn d[2] into a number?

```
n = 10*( d[0] - '0' ) + ( d[1] - '0' ) ;
```

Pulse Width Modulation

- A Regular Waveform

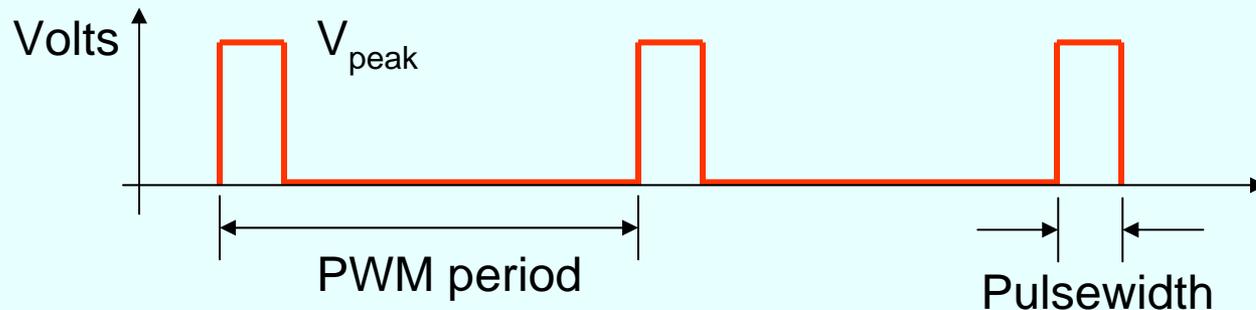


- PWM frequency (Hz) = $1 / \text{PWM period}$
- Duty cycle = $\text{Pulsewidth} / \text{PWM period}$
- PWM frequencies typically range from 100Hz into MHz
- Duty cycles can be used from 0 – 100%, although some systems use much smaller ranges, e.g. 5-10% for hobby remote servos.
- The waveform has two pieces of information: Period and Pulsewidth, although they are usually not changed simultaneously.

Some PWM Uses

- The Allure: very fast, cheap switches and clocks to approximate continuous processes. Also, two-state signal resists noise corruption.
- Sensors: PWM period is naturally related to *rotation or update rate*: Hall effect, anemometers, incremental encoders, tachometers, etc.
- Communication: PWM duty cycle is *continuously variable* → like an D/A and an A/D.
- Actuation: At very high frequencies, physical systems filter out all but the mean; i.e.,

$$V_{\text{effective}} = \text{duty_cycle} * V_{\text{peak}}$$

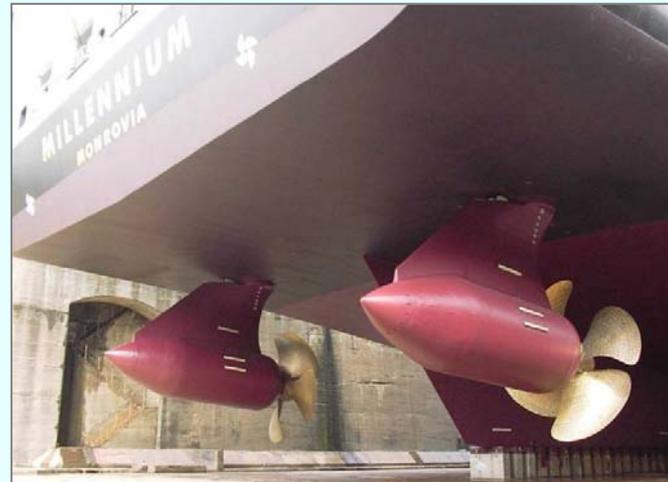
High frequency switching is the dominant mode for powering large motors!



Field Effect Transistor (FET)


- Like a “valve”, that is very easy to open or close. When FET is open, resistance is low (milli-Ohms); when FET is closed, resistance is high (mega-Ohms or higher)

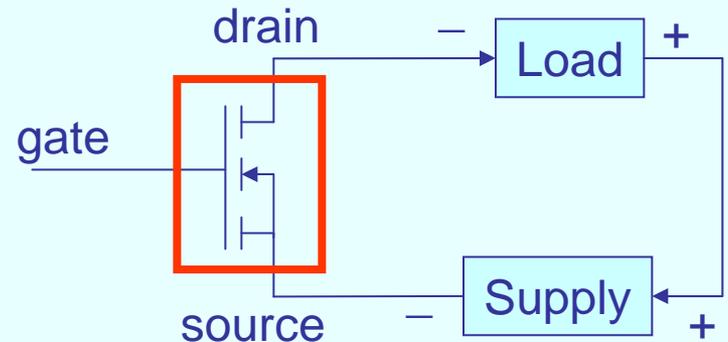- Typically three connections:
 - Gate: the signal; low current
 - Source: power in
 - Drain: power out




- *N*- and *P*-type junctions are common, and involve the polarity of the device. (*N* is shown)
- Extremely sensitive to static discharge! *Handle with care.*
- MOSFET: modern FET's capable of handling higher power levels.


Bipolar Control with a MOSFET H-Bridge

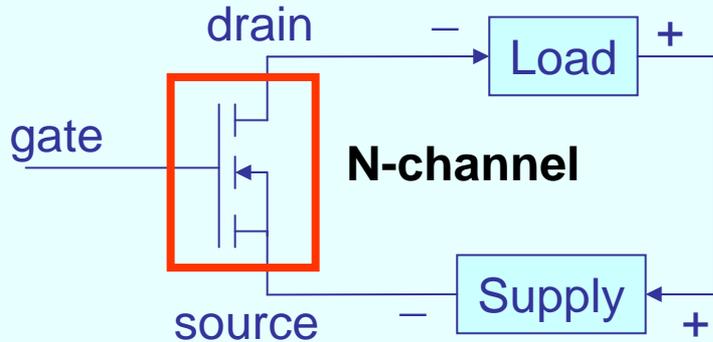

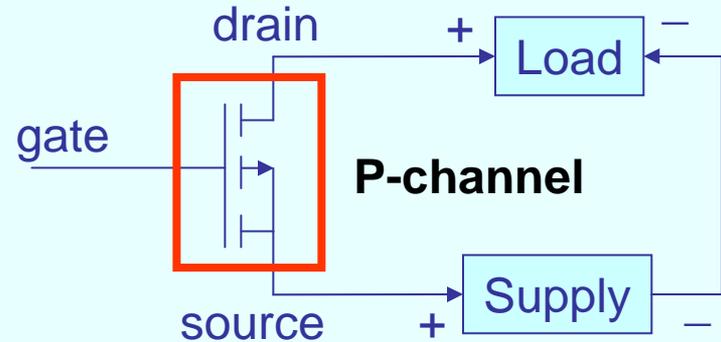
MOSFET turns on when $V_{gate} > V_{source}$



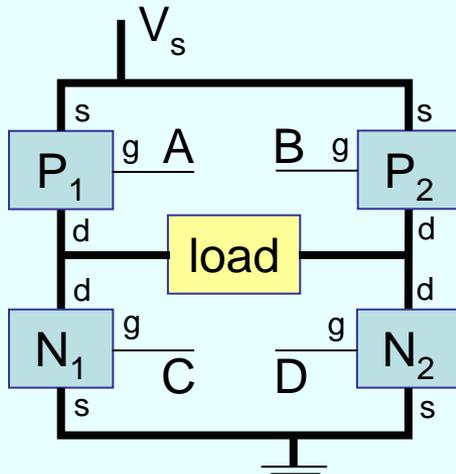
MOSFET turns on when $V_{gate} < V_{source}$



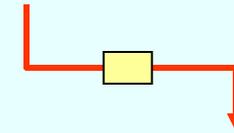To make flow UL to LR,
set A = GND and D = V_s



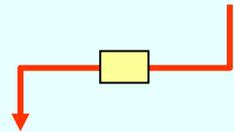To make flow UR to LL,
Set B = GND and C = V_s



*Connect A and B to V_s with pull-up resistors;
Connect C and D to GND with pull-down resistors;
Control all four gates explicitly*

The Basic DC Brush Motor

Torque $\tau \leftrightarrow$ (coils)(flux density)(current i),
or, in a given motor,

$$\tau = k_t * i \quad \text{where } k_t \text{ is the torque constant}$$

But the motion of the coils also induces a
voltage in the coil, the back-EMF:

$$e_b = k_t * \omega \quad (\text{YES, that's the same } k_t!)$$


And the windings have a resistance R :

$$e_R = R * i$$

Summing voltages around the loop,

$$V_{supply} = e_b + e_R$$

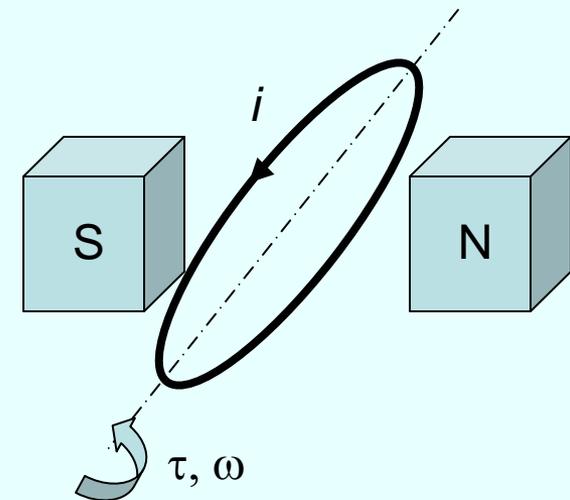Vector relations:
force = current x flux
field = velocity x flux



Properties of the DC Brush Motor

- No-load speed:

$$\tau = 0 \rightarrow i = 0 \rightarrow$$

$$\omega = V / k_t$$

- Zero-speed torque (*BURNS UP MOTOR IF SUSTAINED*):

$$\omega = 0 \rightarrow e_b = 0 \rightarrow i = V / R \rightarrow$$

$$\tau = k_t V / R$$

- Power output:


$$P_{out} = \tau \omega = i e_b \rightarrow$$

$$P_{out} = i (V - Ri)$$

- Efficiency:



$$\eta = P_{out} / P_{in} = \tau \omega / i V \rightarrow$$

$$\eta = 1 - i R / V$$

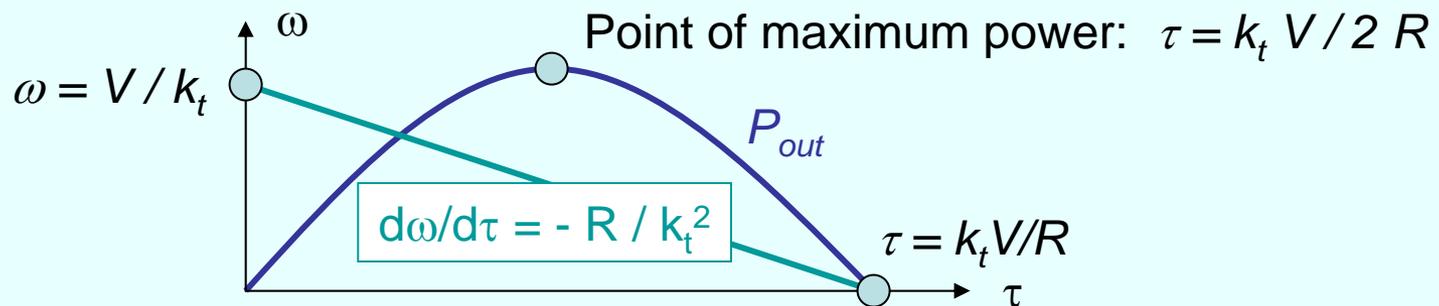

Incremental Encoders for Control

- *What is the position of the motor?*
- Take advantage of cheap, fast counters → make a large number of pulses per revolution, and count them!
- Advantages of the incremental encoder:
 - High resilience to noise because it is a digital signal
 - Counting chip can keep track of multiple motor turns
 - Easy to make – phototransistor, light source, slotted disk
- Two pulse trains required to discern direction: *quadrature*

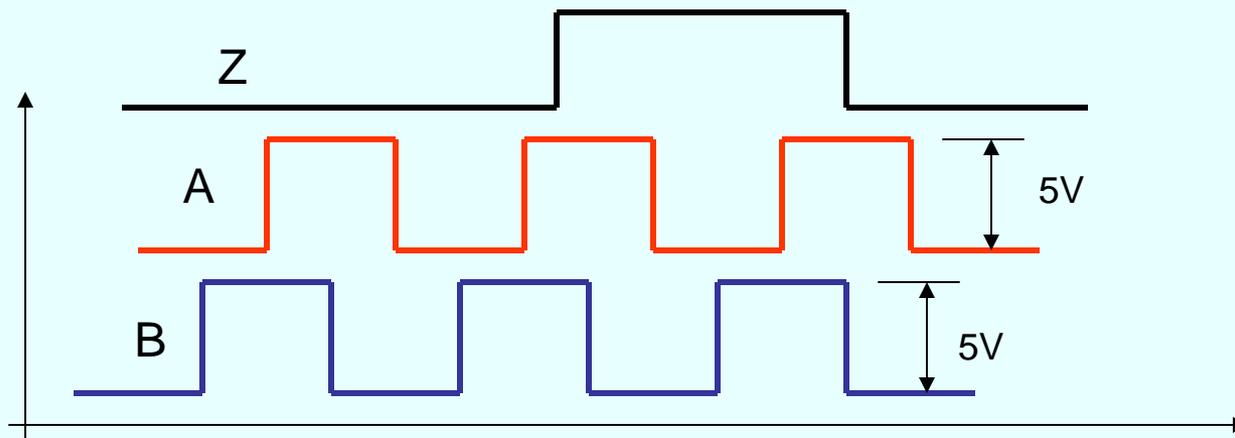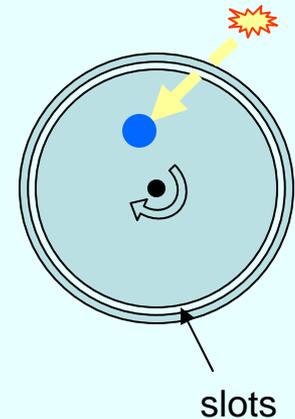


Stepper Motors

Switched coils at fixed positions on the stator attract permanent magnets at fixed positions on the rotor.

Smooth variation of switching leads to half-stepping and micro-stepping

Encoder still recommended!

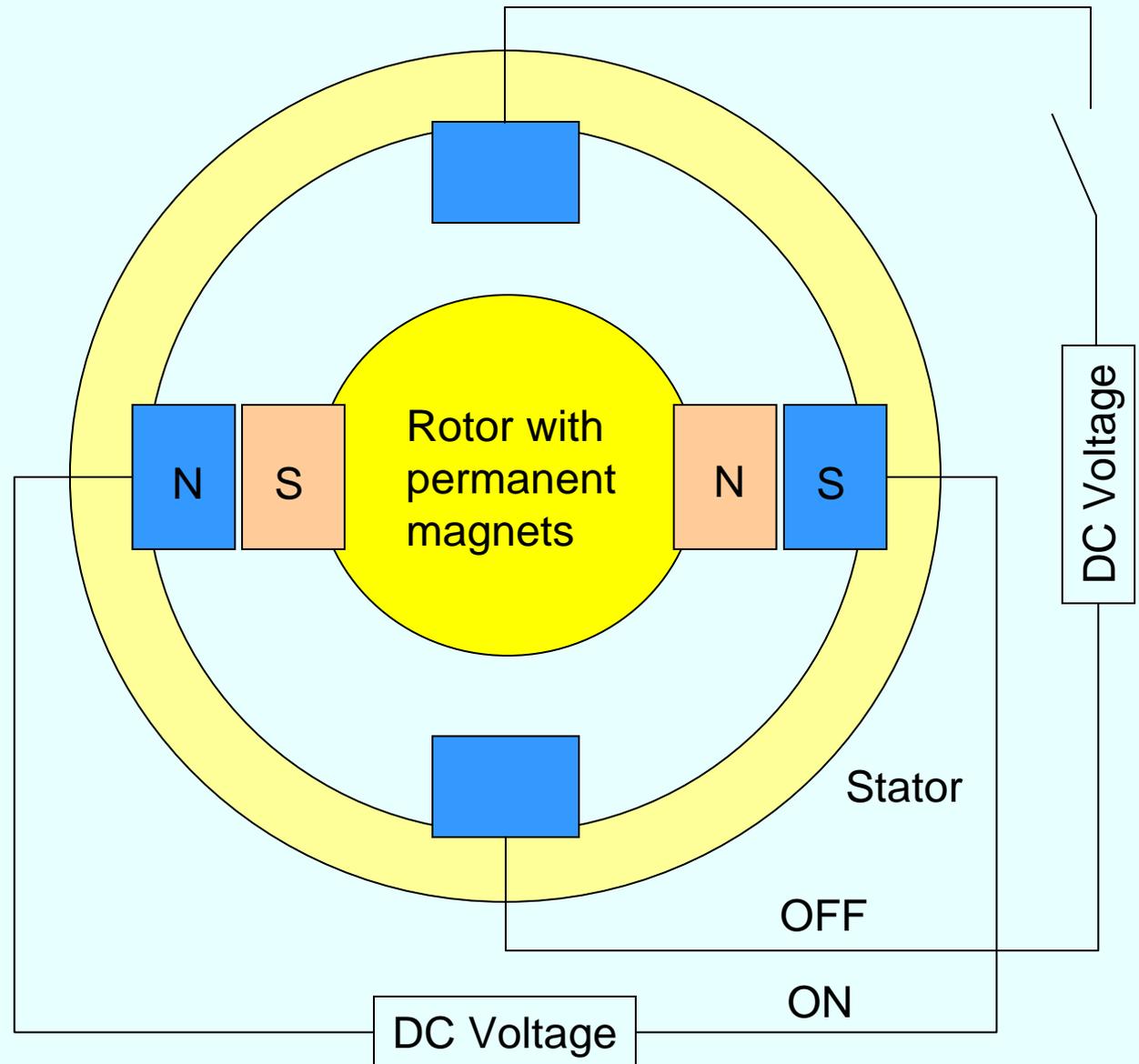

MIT OpenCourseWare
<http://ocw.mit.edu>

2.017J Design of Electromechanical Robotic Systems
Fall 2009

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.