

Toolbox: Electrical Systems Dynamics

Dr. John C. Wright

MIT - PSFC

05 OCT 2010



OUTLINE


- AC and DC power transmission
- Basic electric circuits
- Electricity and the grid

Image removed due to copyright restrictions. Please see "[How Electricity Gets from the Power Station to your Home.](#)" PowerWise Teacher's Center, 2007.




“THE WAR OF THE CURRENTS”

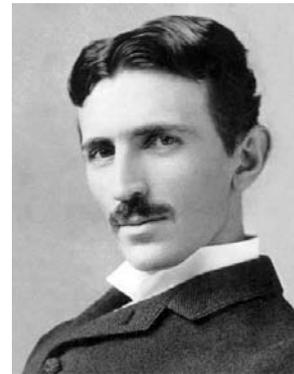- Pros and Cons
 - One kills elephants
 - One has simpler infrastructure
- Why do we have AC and not DC?
- Look at a simple transmission circuit to decide.
- Use Voltage=120 VDC and Power=1.2 GW



Tesla

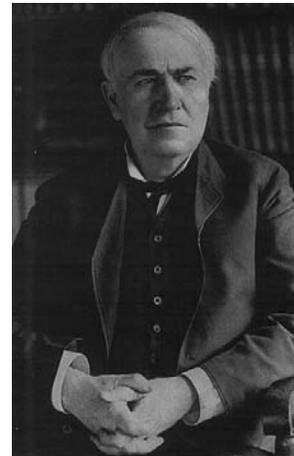


Edison

EFFICIENT TRANSMISSION REQUIRES AC

- Goals of the analysis
 - Find the generator voltage
 - Find the power delivered by the generator
 - Find the power dissipated by the transmission line
 - Find the ratio $P_{\text{Trans}}/P_{\text{Load}}$



A SIMPLE ELECTRIC CIRCUIT

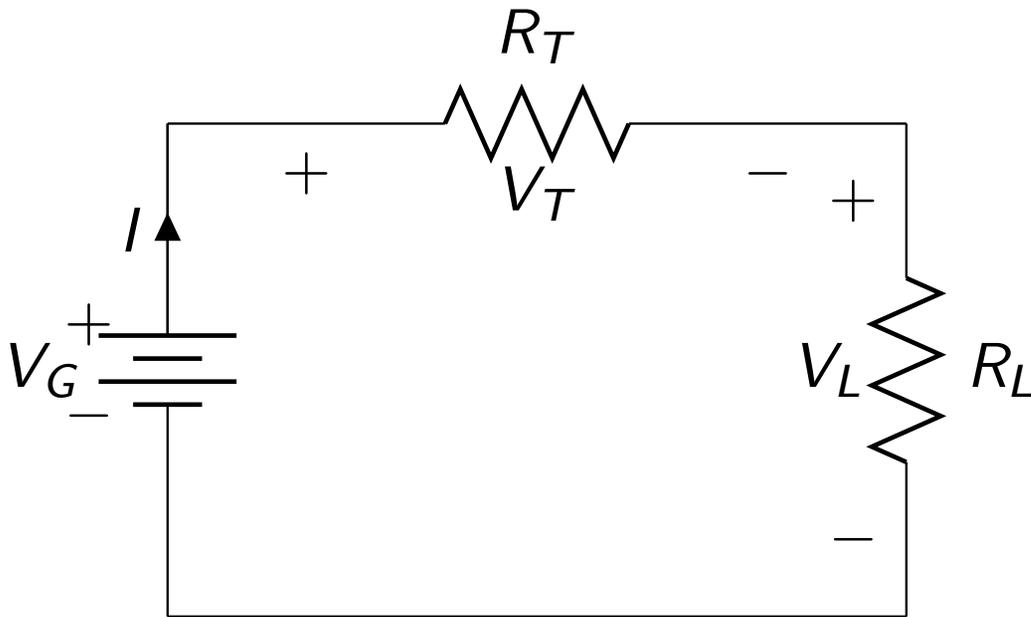

- The current $I = \frac{V_L}{R_L}$
- The power to the load

$$P_L = I^2 R_L = \frac{V_L^2}{R_L}$$
- Equating currents (from Kirchhoff's Laws), the transmission line power

$$P_T = I^2 R_T = \frac{R_T V_L^2}{R_L}$$
- The power ratio is then the ratio of resistances: $\frac{P_T}{P_L} = \frac{R_T}{R_L}$
- Generator power

$$P_G = P_L + P_T = \left(1 + \frac{R_T}{R_L} \frac{V_L^2}{R_L}\right)$$
- Generator voltage

$$V_G = \frac{P_G}{I} = 1 + \left(\frac{R_T}{R_L}\right) V_L$$

EFFICIENCY REQUIRES MOST POWER IS DISSIPATED IN THE LOAD

Example for Al and household V


- If $R_T/R_L \ll 1$, then $P_T \ll P_L$
 - Most of the voltage appears across the load.
 - So, we have very small transmission losses.
- For $P_L = 1.2$ GW and $V_L = 120$ V
 - Then $R_L = P_L/V_L^2 = 1.2 \times 10^{-5}\Omega$
 - For transmission assume $L = 50$ km (a short distance)
 - An Aluminum cable with $A = 5$ cm² (to minimize sag, Cu not used.)
 - Resistivity of Al, $\eta = 2.8 \times 10^{-8}\Omega\text{-m}$
 - $\therefore R_T = \eta L/A = 2.8\Omega \gg R_L$
 - Conclusion: not so good!

AC CAN BE USED TO INCREASE THE VOLTAGE

- With AC we can use transformers
- Step up the voltage at the generator
- Transmit power at high voltage, low current
- Step down the voltage at the load
- Transmitting at low current should reduce transmission losses



AN IDEAL TRANSFORMER

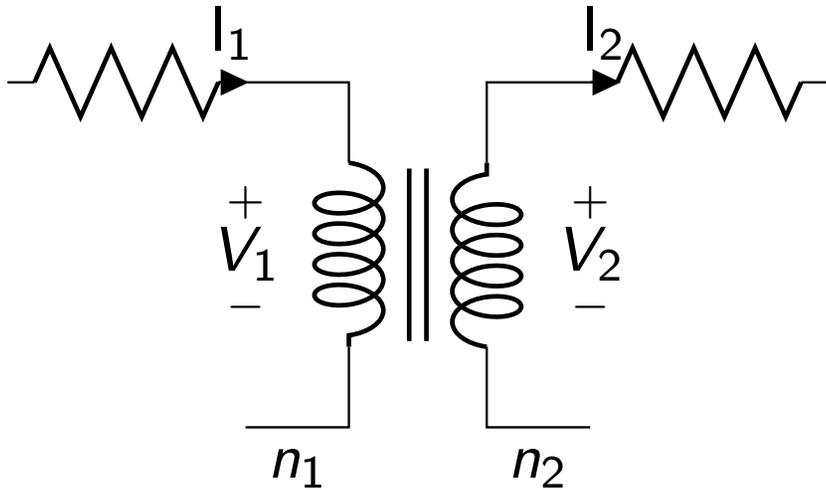

$$N = n_2 / n_1 = \text{turns ratio}$$


$$V_2 = NV_1$$

$$I_2 = I_1 / N$$

Physical process is conservation of magnetic flux/energy

AN IDEAL TRANSFORMER

Common examples of transformers:

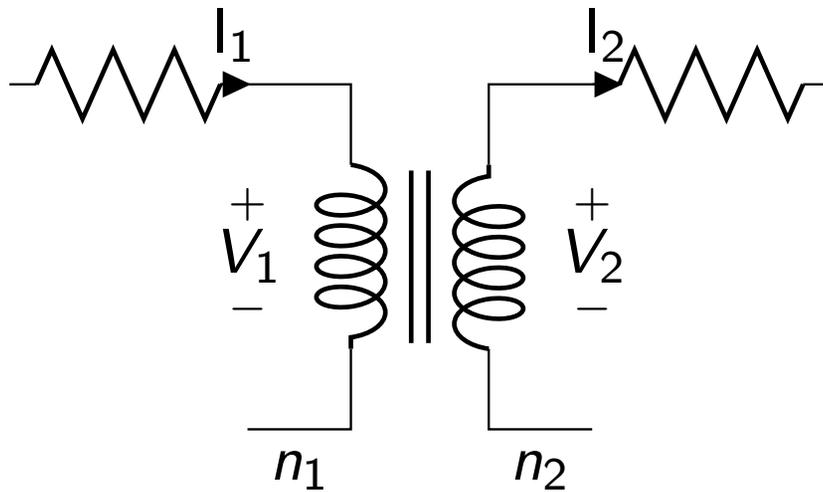

$$N = n_2/n_1 = \text{turns ratio}$$

$$V_2 = NV_1$$


$$I_2 = I_1/N$$

Physical process is conservation of magnetic flux/energy



Bottom right: Photo by [mdverde](#) on Flickr. Bottom left: Image by [Tau Zero](#) on Flickr.
Top right: Photo by [brewbooks](#) on Flickr.

AC TRANSMISSION REDUCES LOSSES

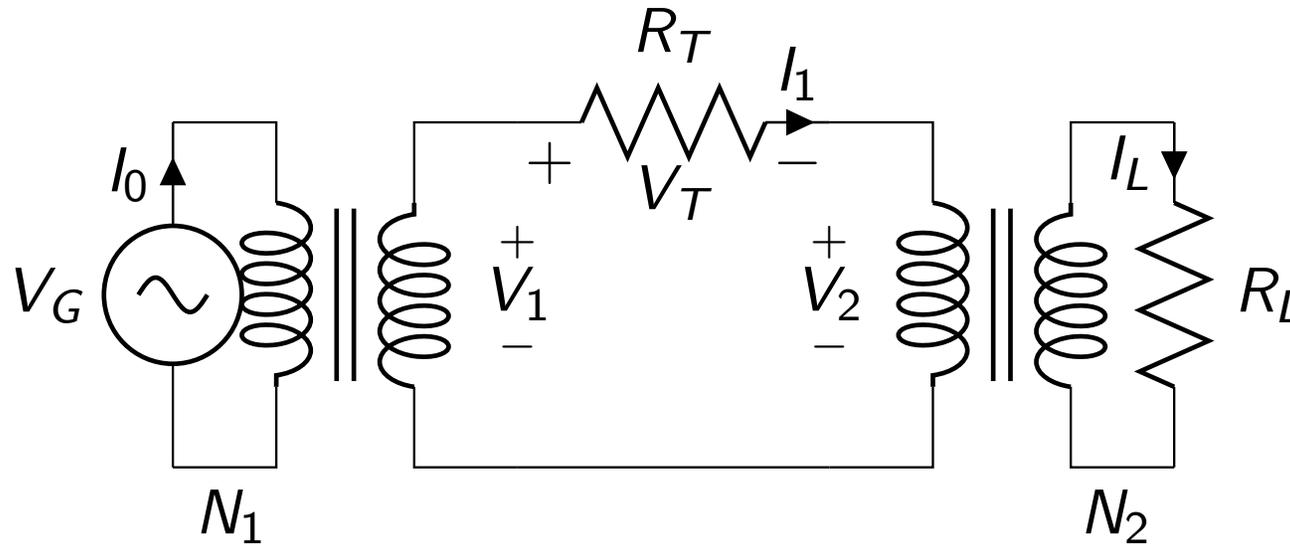

- As before, $P_L = 1.2 \text{ GW}$, $V_L = 120 \text{ V}$, $R_L = 1.2 \times 10^{-5} \Omega$
- What are transformer and transmission requirements,
- Such that $P_T \ll P_L$?

- From the circuit:

$$P_L = V_L I_L = R_L I_L^2$$

$$P_T = V_T I_1 = R_T I_1^2$$

- From the transformer relation, $I_L = N_2 I_1$, it follows

$$\frac{P_T}{P_L} = \frac{1}{N_2^2} \frac{R_T}{R_L}$$

- From the circuit:

$$P_L = V_L I_L = R_L I_L^2$$

$$P_T = V_T I_1 = R_T I_1^2$$

- From the transformer relation, $I_L = N_2 I_1$, it follows

$$\frac{P_T}{P_L} = \frac{1}{N_2^2} \frac{R_T}{R_L}$$



- For $N_2 \gg 1$ a huge reduction in transmission losses
- Practical numbers:
 $V_0 = 12kV$, $V_1 = 240kV$ (rms)
- This implies that $N_1 = V_1/V_0 = 20$
- Assume small voltage drop across the transmission line. Then $V_2 \approx V_1$
- Second turn ratio becomes
 $N_2 = V_2/V_L = 2000$
- Our transmission loss formula gives
 $P_T/P_L \approx 6\%$

THE DOWNSIDE TO AC: REACTIVE POWER


- ❑ A down side to AC: Reactive power
- ❑ Why? Load is not pure resistive
- ❑ Load usually has an inductive component
- ❑ Resistance absorbs power
- ❑ Inductor circulates power back and forth
- ❑ This oscillating power is the reactive power

RESISTORS, INDUCTORS AND CAPACITORS, OH MY!

There are three basic circuit elements having different Ohm's laws.

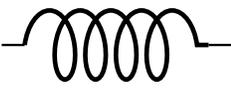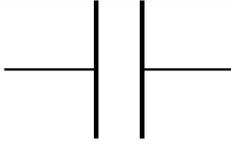Element	Resistor	Inductor	Capacitor
Symbol	R 	L 	C 
Ohm's Law	$V = RI$	$V = L \frac{dI}{dt}$	$\frac{dV}{dt} = I/C$
$I = \sin \omega t$	$V = R \sin \omega t$	$V = L \cos \omega t$	$V = -\frac{1}{C} \cos \omega t$
Phase shift	0	$\pi/2$	$-\pi/2$
Impedance $Z[\Omega] = V/I$	R	$j\omega L$	$\frac{-j}{\omega C}$


PHASE LAGS INCREASE REACTIVE POWER

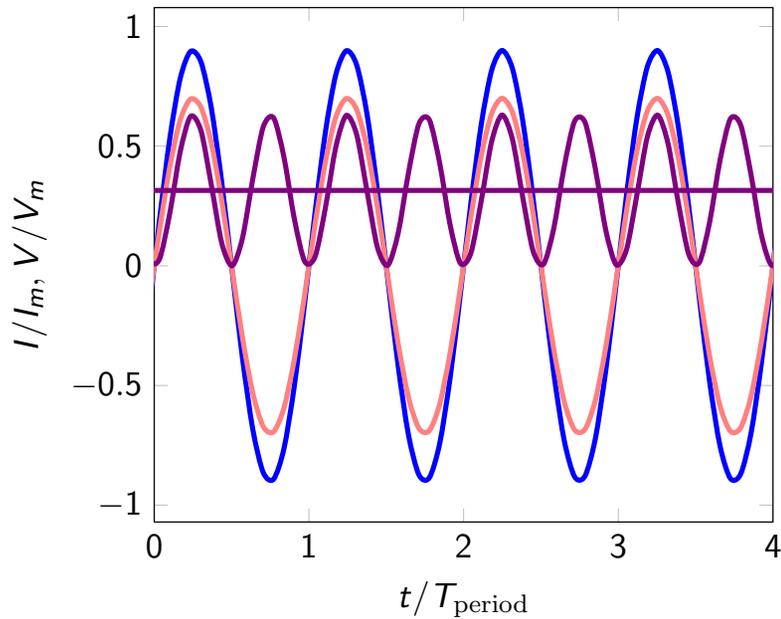

□ Current, $I = I_m \sin\left(\frac{2\pi t}{T_{\text{period}}}\right)$

□ Voltage, $V = V_m \sin\left(\frac{2\pi t}{T_{\text{period}}}\right)$

PHASE LAGS INCREASE REACTIVE POWER

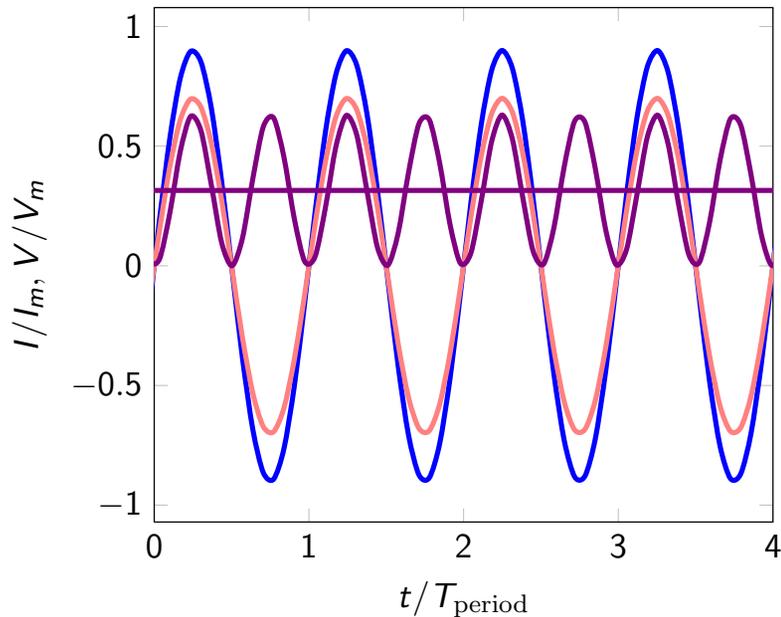

□ Current, $I = I_m \sin\left(\frac{2\pi t}{T_{\text{period}}}\right)$


□ Voltage, $V = V_m \sin\left(\frac{2\pi t}{T_{\text{period}}}\right)$

□ Power,

$$P = I \cdot V = I_m V_m \sin^2\left(\frac{2\pi t}{T_{\text{period}}}\right)$$

$$= \frac{1}{2} I_m V_m \left(1 - \cos\left(2\frac{2\pi t}{T_{\text{period}}}\right)\right)$$

PHASE LAGS INCREASE REACTIVE POWER

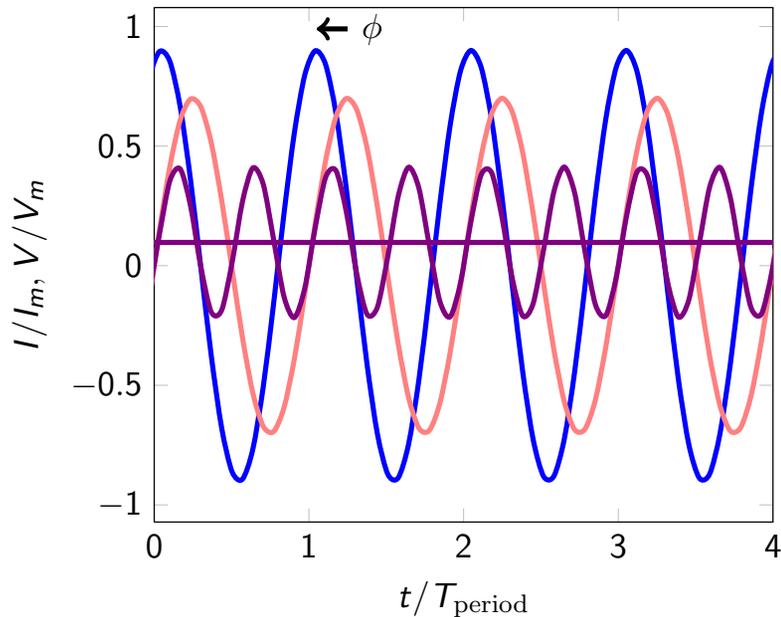

□ Current, $I = I_m \sin\left(\frac{2\pi t}{T_{\text{period}}} + \phi\right)$

□ Voltage, $V = V_m \sin\left(\frac{2\pi t}{T_{\text{period}}}\right)$

□ Power,

$$P = I \cdot V = I_m V_m \sin\left(\frac{2\pi t}{T_{\text{period}}}\right) \sin\left(\frac{2\pi t}{T_{\text{period}}} + \phi\right)$$

$$= \frac{1}{2} I_m V_m \left(\cos(\phi) - \cos\left(2\frac{2\pi t}{T_{\text{period}}} + \phi\right) \right)$$

$\cos(\phi)$ is known as the power factor


REACTIVE POWER MUST BE SUPPLIED.

- ❑ For parts of the AC cycle the instantaneous power is greater than the average power
- ❑ Generator must be able to deliver this higher power even though it is returned later
- ❑ Bottom line: generator must have a higher volt-amp rating than average power delivered: VARs and Watts.
- ❑ Higher rating → bigger size → higher cost




PHASE SHIFTS ARE INTRODUCED BY INDUCTANCE

- A motor will have an inductance, L .

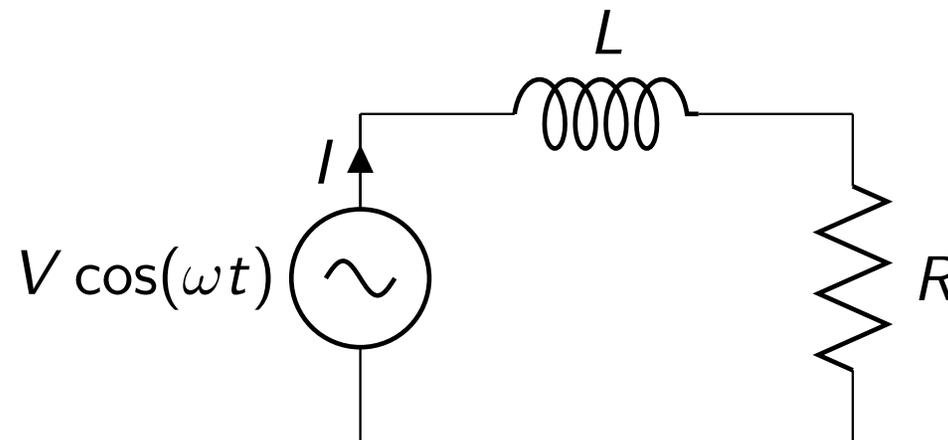

PHASE SHIFTS ARE INTRODUCED BY INDUCTANCE

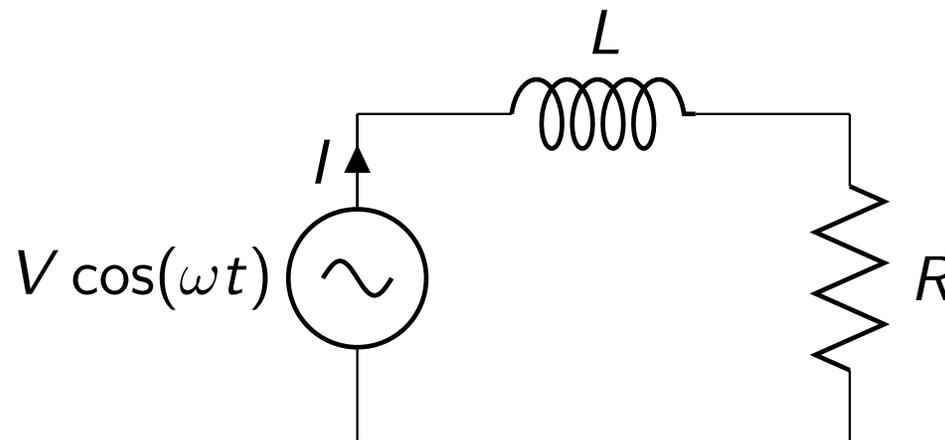
- A motor will have an inductance, L .
- It will introduce a phase shift given by $\tan \phi = \frac{\omega L}{R}$



PHASE SHIFTS ARE INTRODUCED BY INDUCTANCE

- A motor will have an inductance, L .
- It will introduce a phase shift given by $\tan \phi = \frac{\omega L}{R}$
- Amplitude of current will also be reduced.
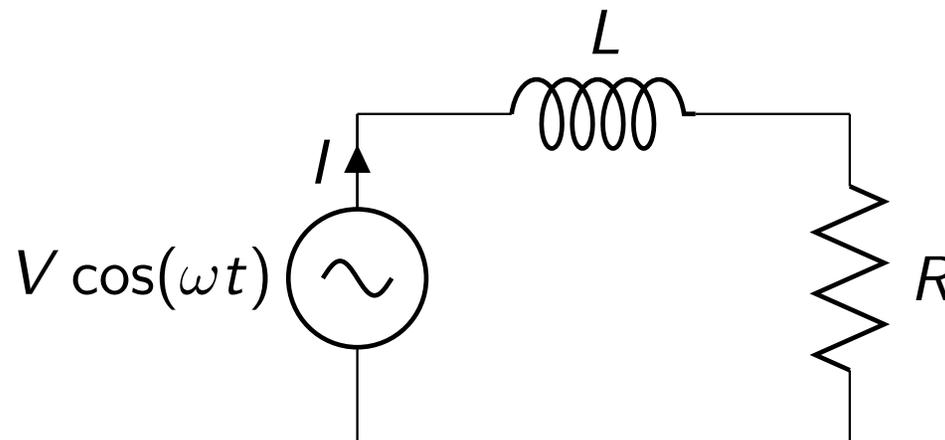
$$I = \frac{V}{(\omega^2 L^2 + R^2)^{1/2}}$$




PHASE SHIFTS ARE INTRODUCED BY INDUCTANCE

- A motor will have an inductance, L .
- It will introduce a phase shift given by $\tan \phi = \frac{\omega L}{R}$
- Amplitude of current will also be reduced.

$$I = \frac{V}{(\omega^2 L^2 + R^2)^{1/2}}$$

- This all follows from adding up the voltages for a simple circuit:
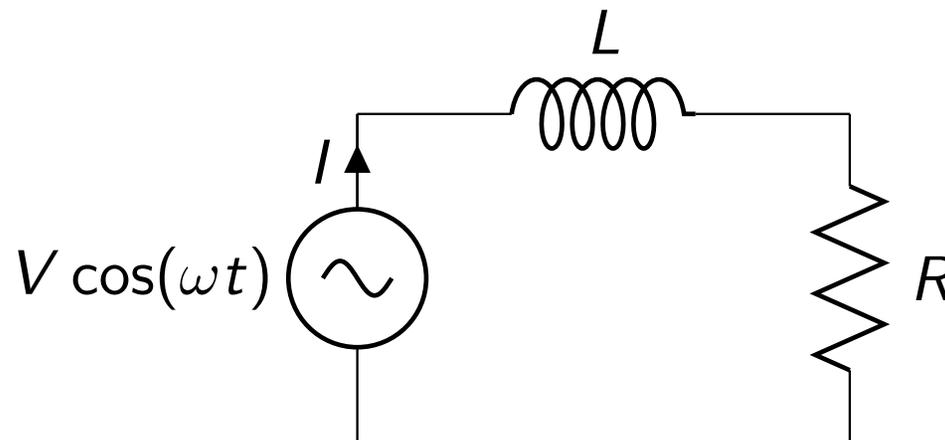
$$L \frac{di}{dt} + Ri = V \cos(\omega t)$$



HOW TO MINIMIZE THE VA REQUIREMENT?

- To minimize the VA requirements on the generator we want $\phi \rightarrow 0$
- Assume the average power absorbed by the load is $\langle P_L \rangle$
- Calculate the peak generator power $[P_G(t)]_{\max}$ as a function of $\langle P_L \rangle$
- Note: The peak is $2\times$ (rms volt-amp rating)
- Less generator power is cheaper.



PEAK POWER FROM INDUCTANCE

- The power dissipated in the load:

$$\begin{aligned}\langle P_L \rangle &= RI^2 \\ &= \frac{RV^2}{\omega^2 L^2 + R^2}\end{aligned}$$

- The peak power delivered by the generator

$$P_{\text{peak}} = VI(1 + \cos \phi) = \frac{V^2}{(\omega^2 L^2 + R^2)^{1/2}} \left(1 + \frac{R}{(\omega^2 L^2 + R^2)^{1/2}} \right)$$

- Using the expression for $\langle P_L \rangle$, we get:

$$\frac{P_{\text{peak}}}{2\langle P_L \rangle} = \frac{(\omega^2 L^2 + R^2)^{1/2} + R}{2R} \geq 1$$




CAPACITANCE CAN BALANCE OUT REACTIVE POWER

- Recall from our table that the phase lags are opposite for inductance and capacitance
- $\tan \phi_L = \frac{\omega L}{R}$, $\tan \phi_C = \frac{-1}{\omega C}$
- Short answer: there is a capacitance that will keep the current and voltage in phase (but not eliminate the power factor)

$$C = \frac{L}{R^2 + \omega^2 L^2}$$

- Long answer follows.

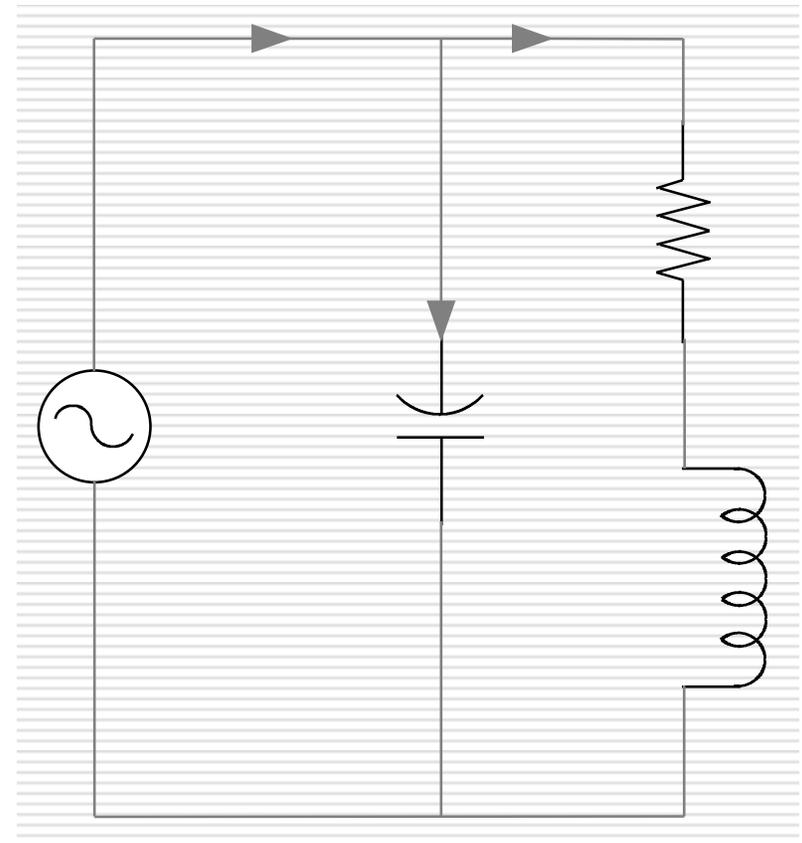

Analysis

- I – V relation for a capacitor

$$\hat{I}_1(t) = C \frac{dV_G}{dt}$$

- I – V relation for the load

$$V_G = R\hat{I}_2 + L \frac{d\hat{I}_2}{dt}$$

- Conservation of current

$$\hat{I}(t) = \hat{I}_1(t) + \hat{I}_2(t)$$

Solution

- Assume $V_G = V \cos(\omega t)$ (all voltages now rms)
- Current in the capacitor branch

$$\hat{I}_1(t) = -\omega C V \sin(\omega t)$$

- Current in the load branch (from before)

$$\hat{I}_2(t) = \frac{V}{(R^2 + \omega^2 L^2)^{1/2}} \cos(\omega t - \phi)$$

The total current

- The total current flowing from the generator

$$\begin{aligned}\hat{I}(t) &= \hat{I}_1(t) + \hat{I}_2(t) \\ &= V \left[\frac{\cos(\omega t - \phi)}{(R^2 + \omega^2 L^2)^{1/2}} - \omega C \sin(\omega t) \right] \\ &= V \left\{ \frac{\cos(\omega t) \cos \phi}{(R^2 + \omega^2 L^2)^{1/2}} + \left[\frac{\sin \phi}{(R^2 + \omega^2 L^2)^{1/2}} - \omega C \right] \sin(\omega t) \right\}\end{aligned}$$

The value of C

- Choose C for zero reactive power
- Set $\sin(t)$ coefficient to zero

$$\omega C = \frac{\sin \phi}{(R^2 + \omega^2 L^2)^{1/2}}$$

- Simplify by eliminating the power factor

$$C = \frac{L}{(R^2 + \omega^2 L^2)}$$

Calculate the peak power

- Calculate the peak power to learn what has happened to the VA rating

$$\begin{aligned}P_{peak} &= [P_G(t)]_{\max} = 2[VI]_{\max} \\&= 2V^2 \frac{\cos \phi}{(R^2 + \omega^2 L^2)^{1/2}} \\&= 2 \frac{RV^2}{(R^2 + \omega^2 L^2)} \\&= 2\langle P_L \rangle\end{aligned}$$

The Result

- It worked!!
- The VA requirement has been reduced

$$VA = \frac{P_{peak}}{2} = \langle P_L \rangle$$

DISCUSSION

- ❑ AC is good for transmission
- ❑ Have to manage reactive power

Other aspects:

- ❑ HVDC transmission lines
- ❑ AC losses from corona discharge
- ❑ Voltage and frequency tolerances
- ❑ Stability of the grid to perturbations, eg a power plant going offline or a transmission line going down.



MIT OpenCourseWare
<http://ocw.mit.edu>

22.081J / 2.650J / 10.291J / 1.818J / 2.65J / 10.391J / 11.371J / 22.811J / ESD.166J

Introduction to Sustainable Energy

Fall 2010

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.