

# Class 12: Outline

Hour 1:

Working with Circuits

Expt. 4. Part I: Measuring V, I, R


Hour 2:

RC Circuits

Expt. 4. Part II: RC Circuits



# Last Time: Resistors & Ohm's Law

# Resistors & Ohm's Law

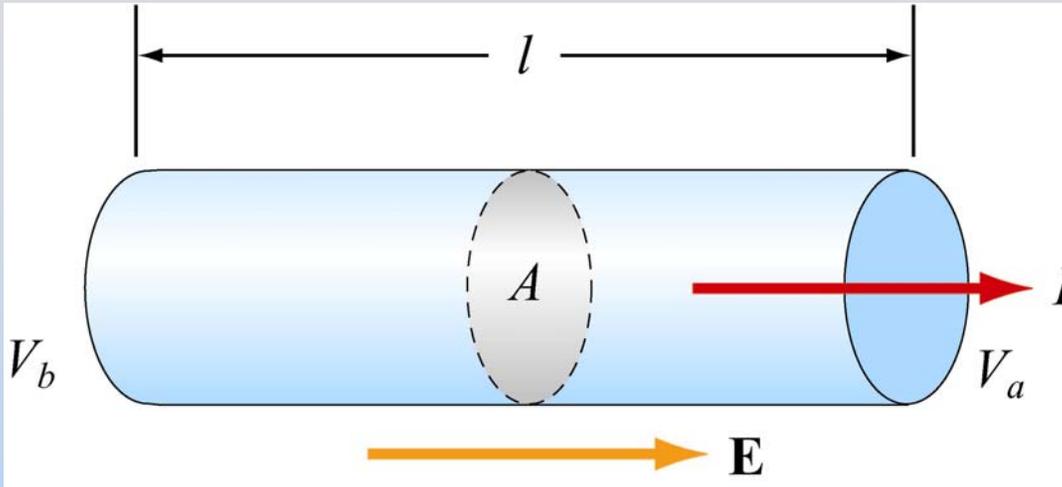

$$R = \frac{\rho l}{A}$$


$$\Delta V = IR$$

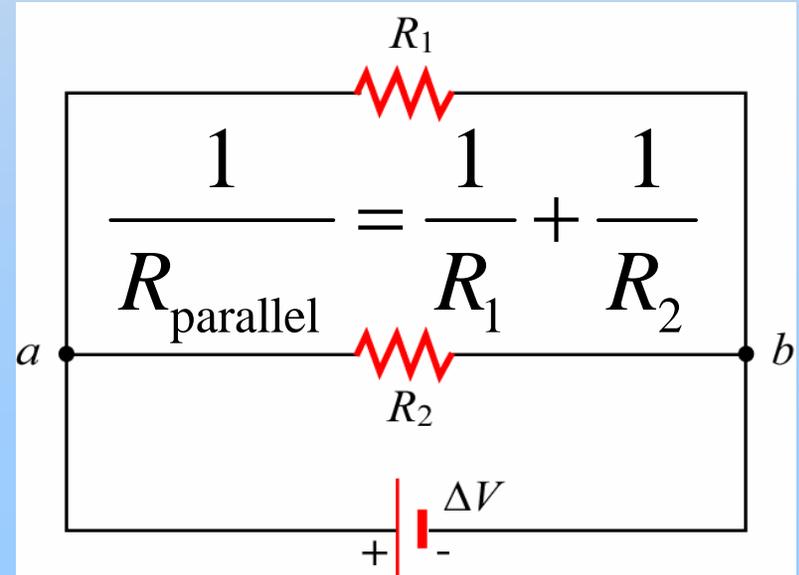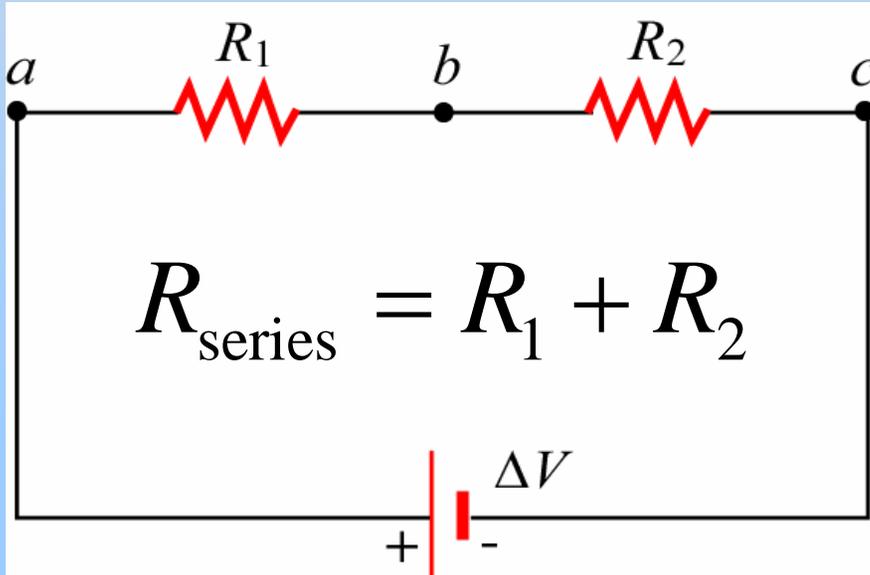

# Measuring Voltage & Current
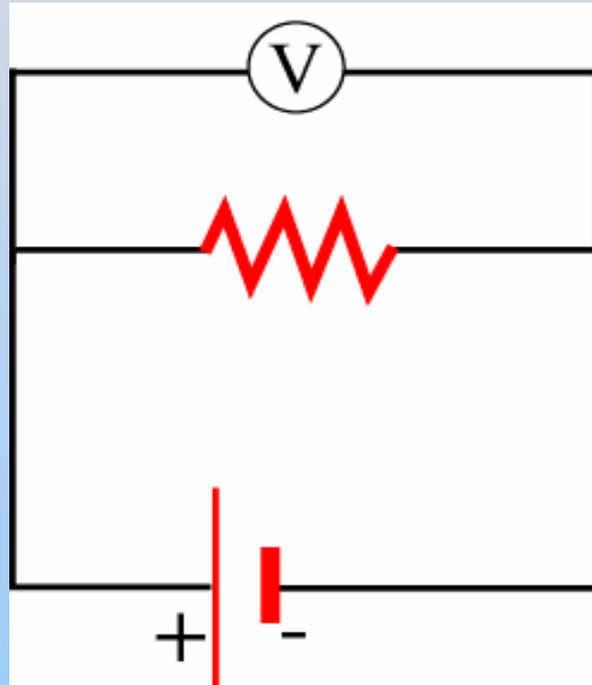
# Measuring Potential Difference


A voltmeter must be hooked in *parallel* across the element you want to measure the potential difference across



Voltmeters have a very large resistance, so that they don't affect the circuit too much
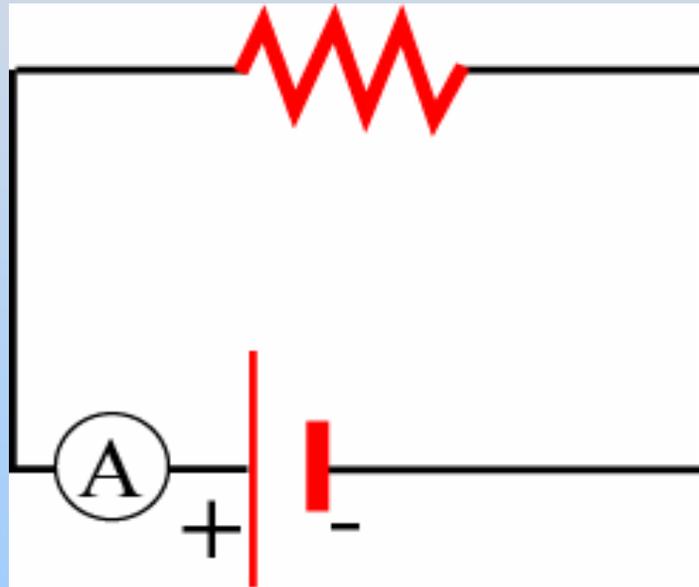
# Measuring Current


An ammeter must be hooked in *series* with the element you want to measure the current through



Ammeters have a very low resistance, so that they don't affect the circuit too much
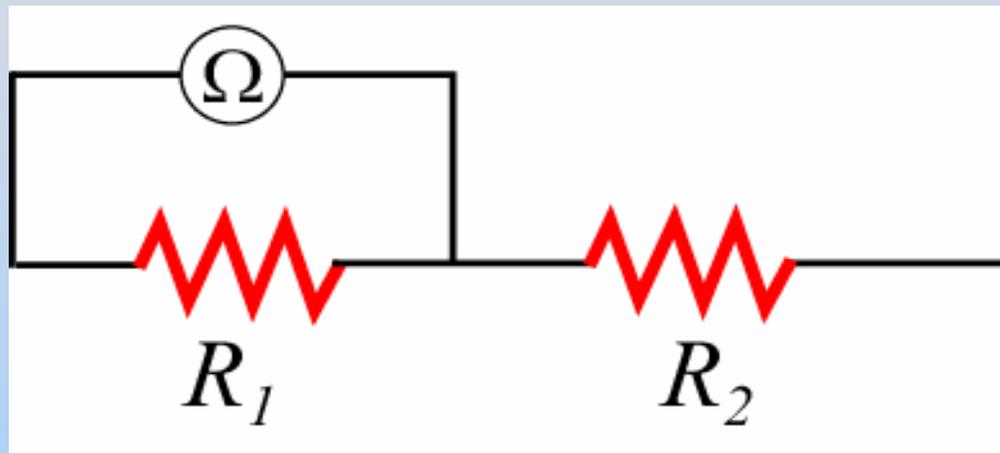
# Measuring Resistance

An ohmmeter must be hooked in *parallel* across the element you want to measure the resistance of



Here we are measuring  $R_1$

Ohmmeters apply a voltage and measure the current that flows. They typically won't work if the resistor is powered (connected to a battery)

# **Experiment 4:**


## **Part 1: Measuring V, I & R**

# RC Circuits

# (Dis)Charging a Capacitor


1. When the direction of current flow is toward the positive plate of a capacitor, then

$$I = + \frac{dQ}{dt}$$

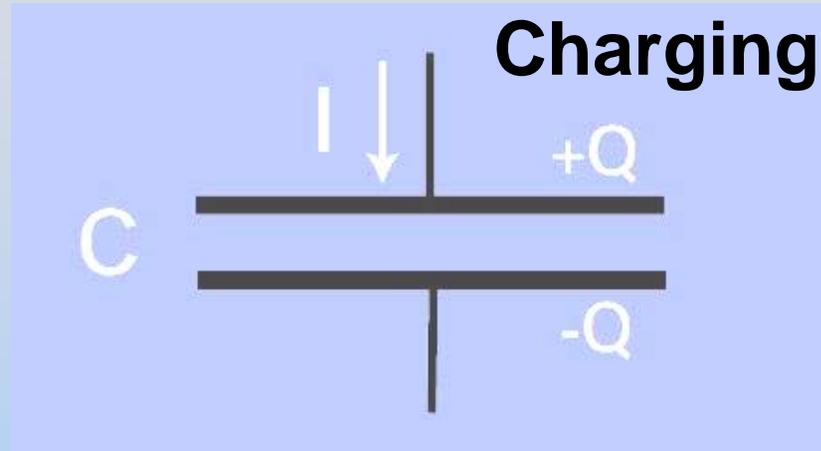


2. When the direction of current flow is away from the positive plate of a capacitor, then

$$I = - \frac{dQ}{dt}$$


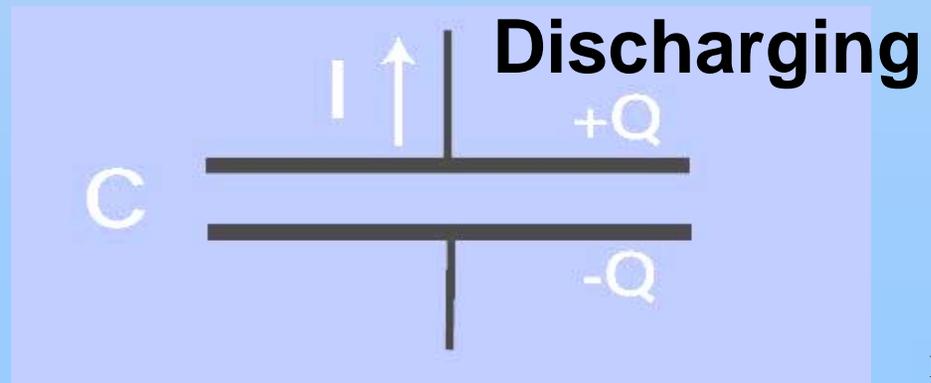


# Charging A Capacitor

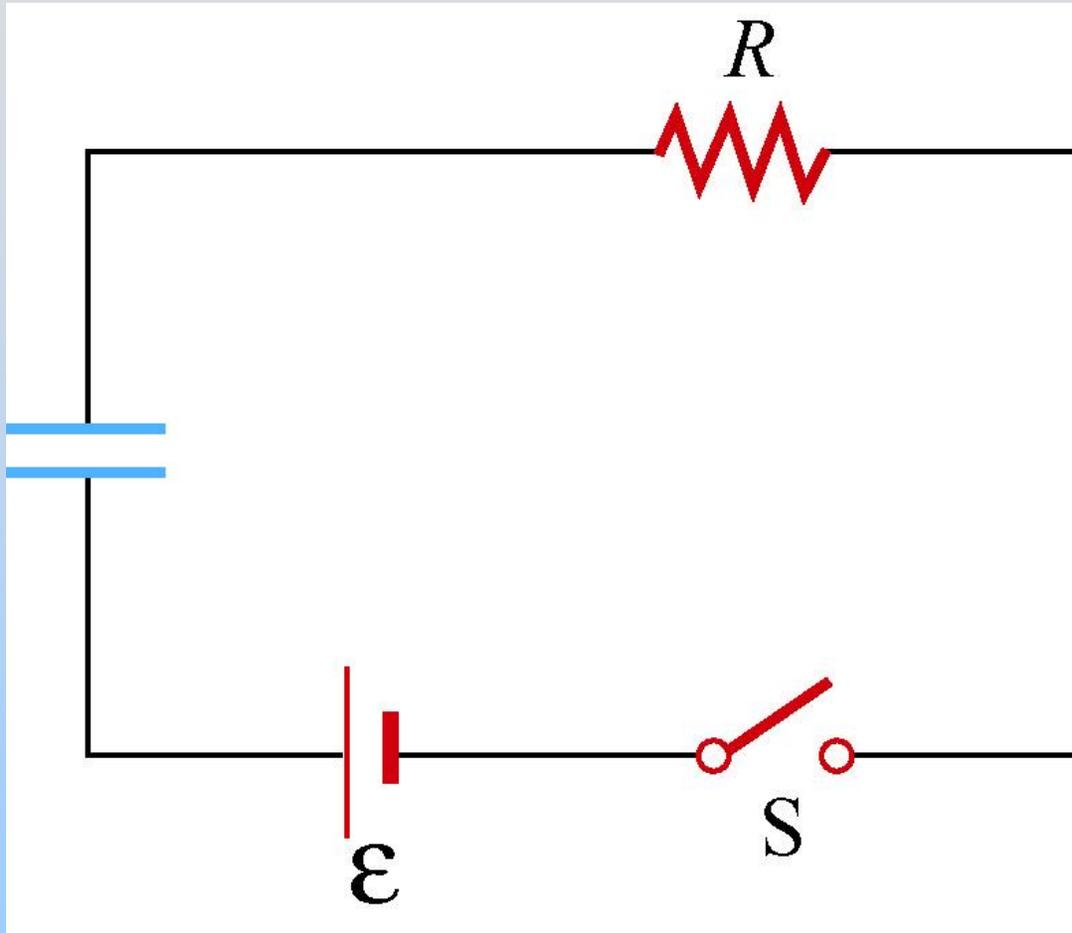

What happens when we close switch  $S$ ?


# Charging A Capacitor

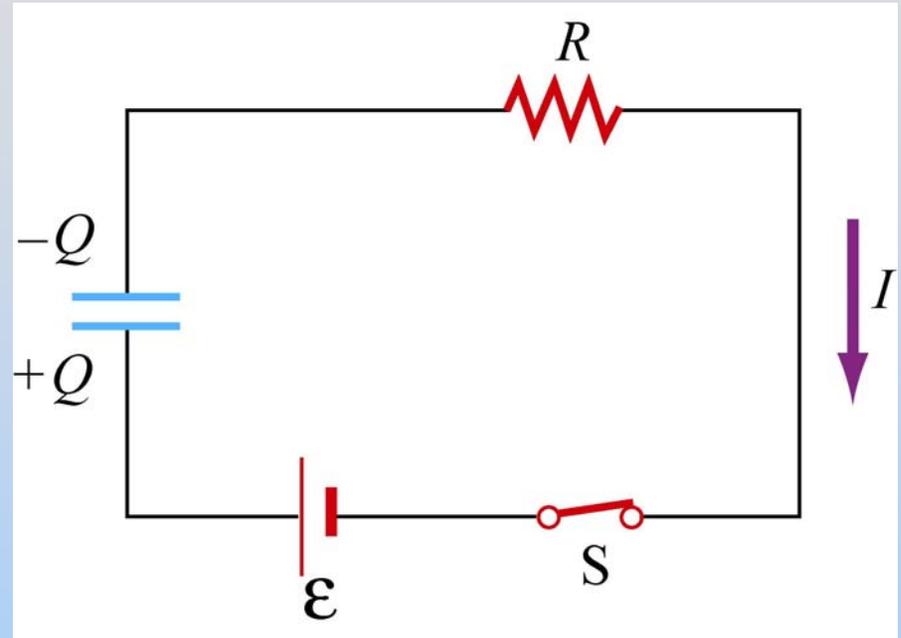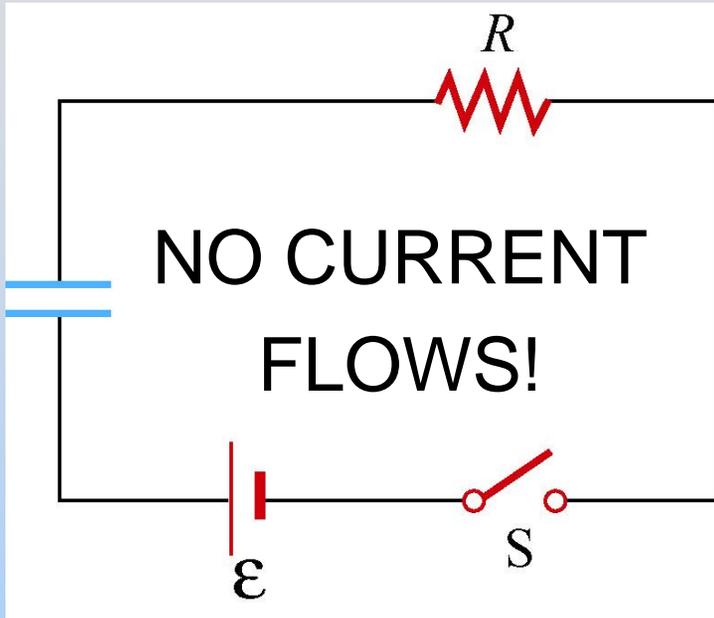

1. Arbitrarily assign direction of current
2. Kirchhoff (walk in direction of current):

$$\sum_i \Delta V_i = \mathcal{E} - \frac{Q}{C} - IR = 0$$

# Charging A Capacitor

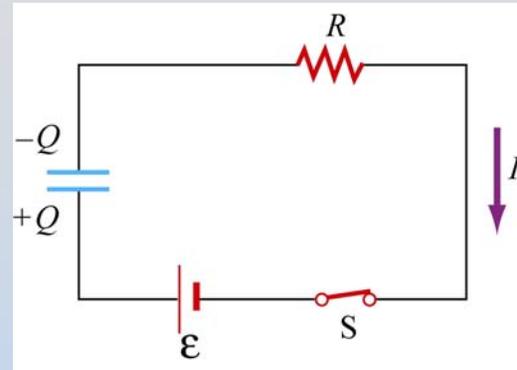

$$\mathcal{E} - \frac{Q}{C} = \frac{dQ}{dt} R \Rightarrow \frac{dQ}{Q - C\mathcal{E}} = -\frac{dt}{RC}$$


$$\int_0^Q \frac{dQ}{Q - C\mathcal{E}} = -\int_0^t \frac{dt}{RC}$$

A solution to this differential equation is:


$$Q(t) = C\mathcal{E} \left( 1 - e^{-t/RC} \right)$$

$RC$  is the time constant, and has units of seconds

# Charging A Capacitor

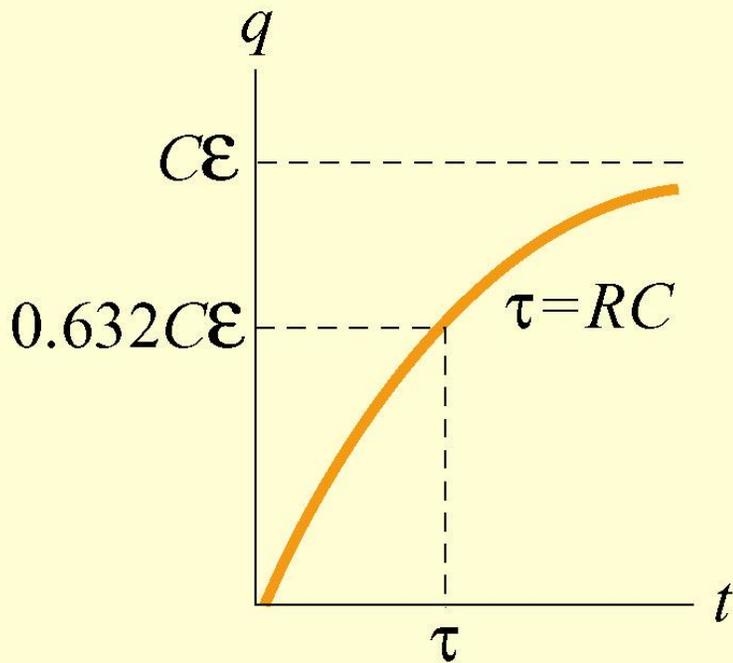

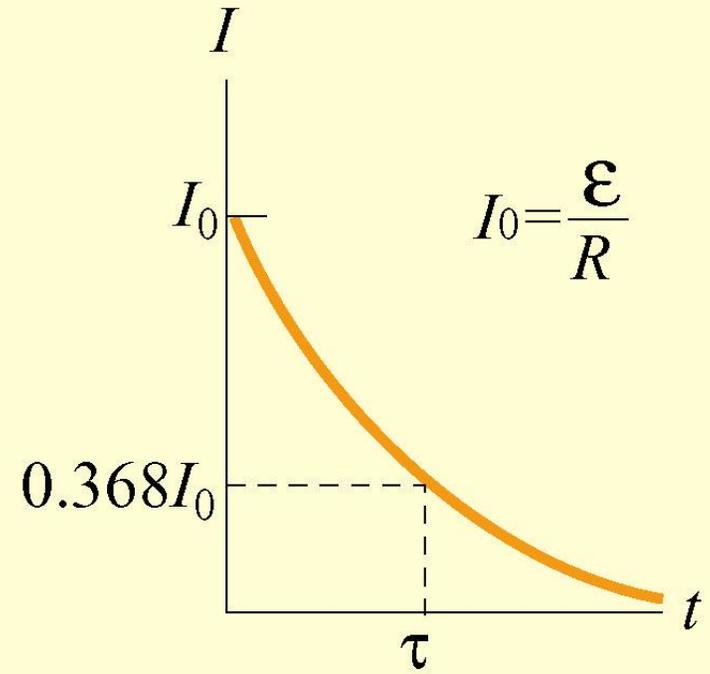
$$Q = C\mathcal{E} \left( 1 - e^{-t/RC} \right)$$



$$I = \frac{dQ}{dt} = \frac{\mathcal{E}}{R} e^{-t/RC}$$



# **PRS Questions: Charging a Capacitor**

# Discharging A Capacitor

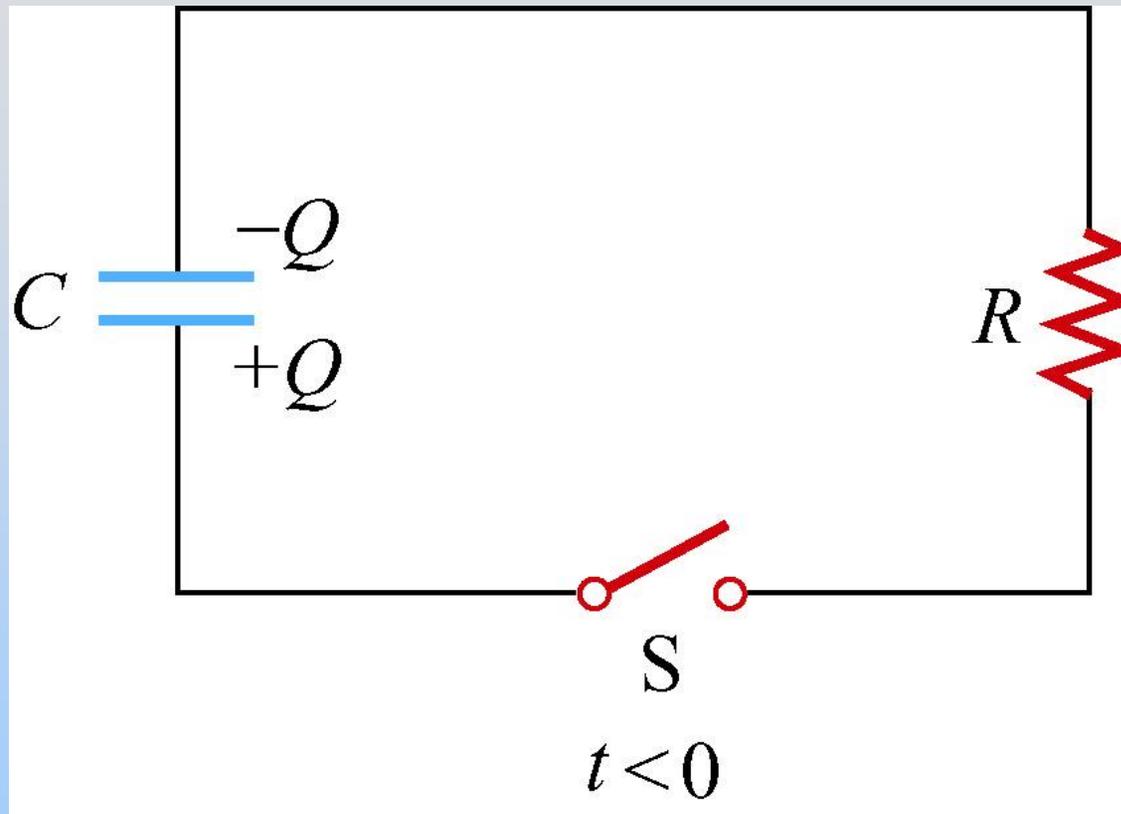

What happens when we close switch  $S$ ?

# Discharging A Capacitor

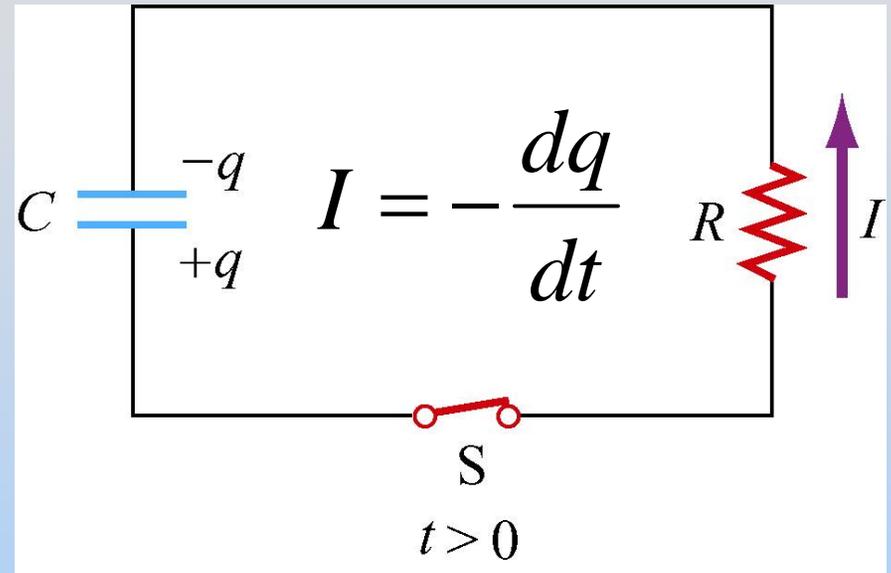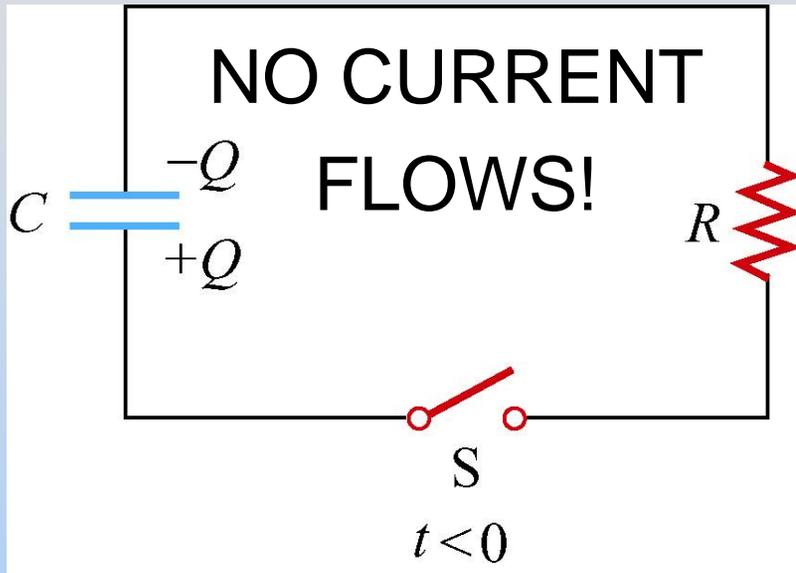


$$\sum_i \Delta V_i = \frac{q}{C} - IR = 0$$

# Discharging A Capacitor


$$\frac{dq}{dt} + \frac{q}{RC} = 0 \Rightarrow \int_{Q_0}^Q \frac{dq}{q} = - \int_0^t \frac{dt}{RC}$$

$$Q(t) = Q_0 e^{-t/RC}$$

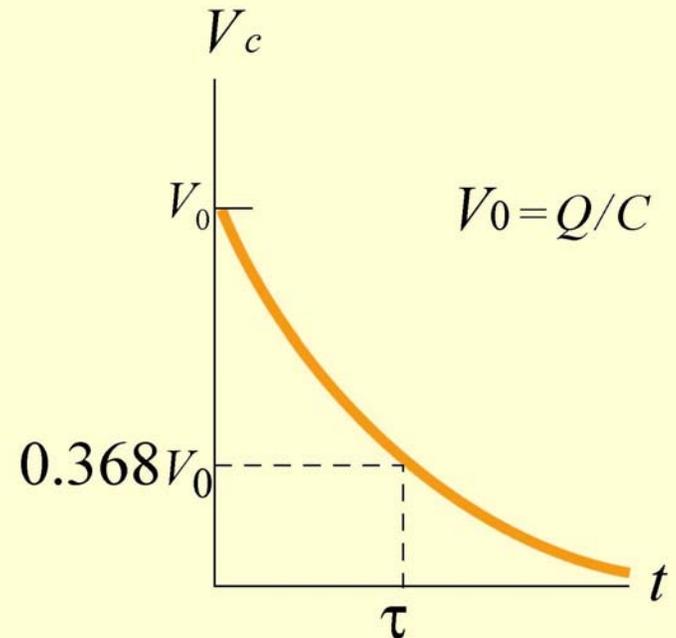


# General Comment: RC

All Quantities Either:

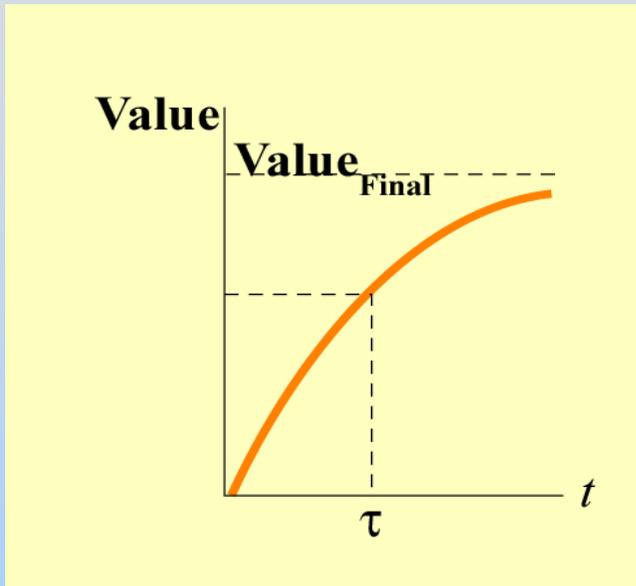

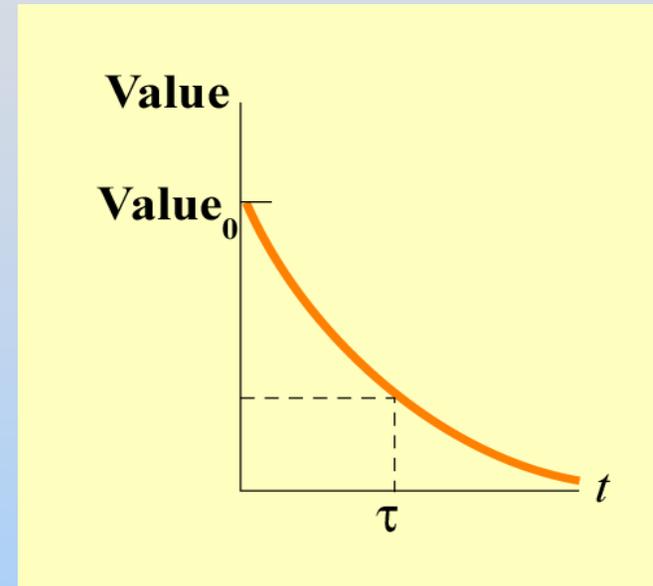
$$\text{Value}(t) = \text{Value}_{\text{Final}} \left(1 - e^{-t/\tau}\right)$$



$$\text{Value}(t) = \text{Value}_0 e^{-t/\tau}$$

$\tau$  can be obtained from differential equation  
(prefactor on  $d/dt$ ) e.g.  $\tau = RC$

# Exponential Decay

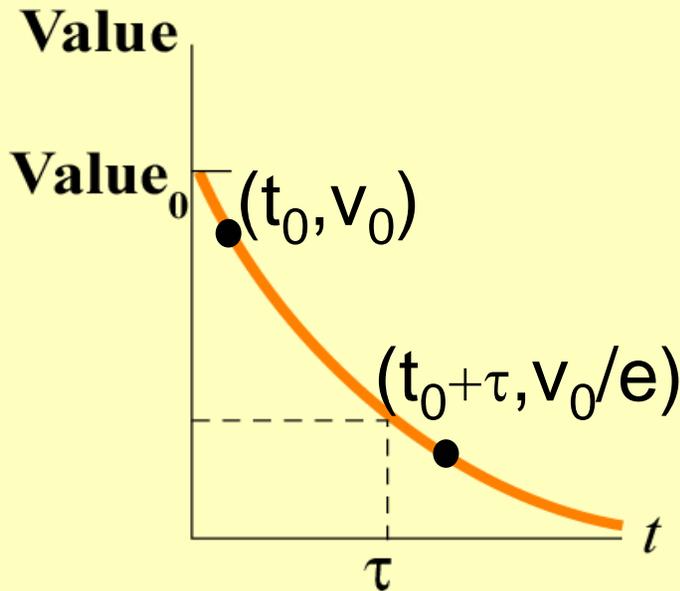

$$\text{Value}(t) = \text{Value}_0 e^{-t/\tau}$$

Very common curve in physics/nature

How do you measure  $\tau$ ?

- 1) Fit curve (make sure you exclude data at both ends)
- 2) a) Pick a point  
b) Find point with y value down by e  
c) Time difference is  $\tau$

# Demonstrations: RC Time Constants

# **Experiment 4:**

## **Part II: RC Circuits**

**PRS Question:  
Multiloop circuit with Capacitor  
in One Loop**