

# Class 26: Outline

Hour 1:

Driven Harmonic Motion (RLC)


Hour 2:

Experiment 11: Driven RLC Circuit


# Last Time: Undriven RLC Circuits
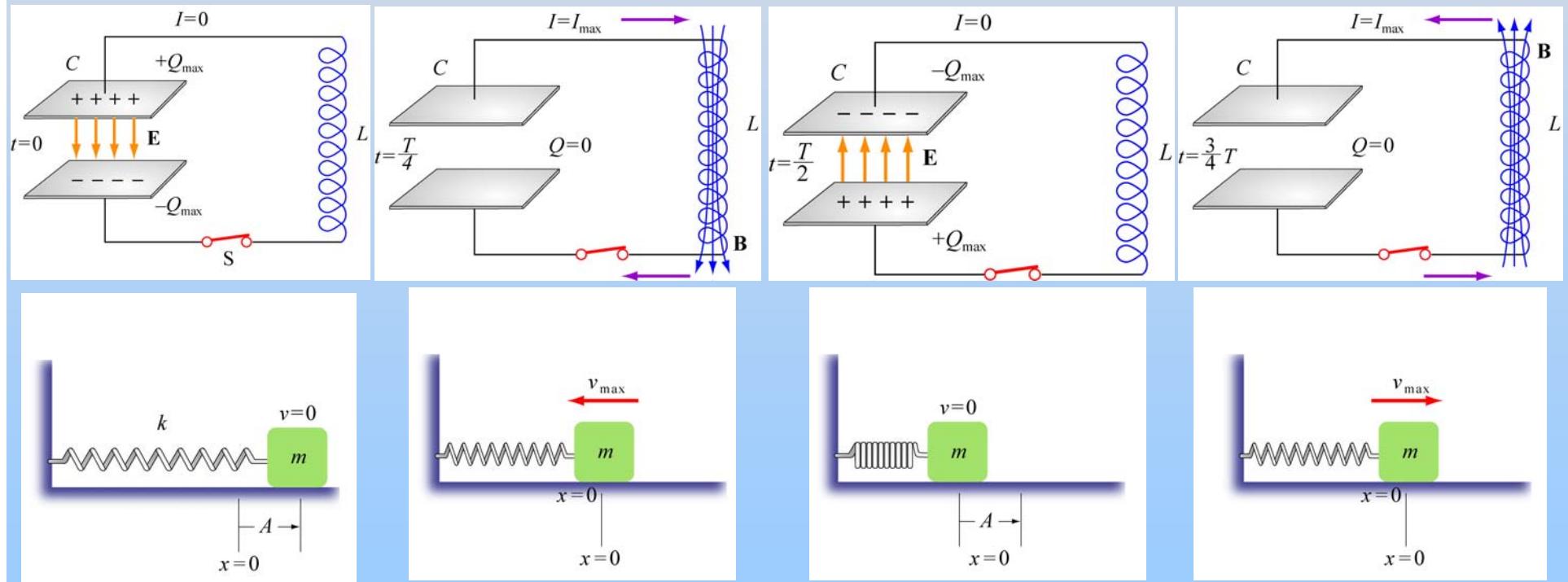
# LC Circuit


It undergoes simple harmonic motion, just like a mass on a spring, with trade-off between charge on capacitor (Spring) and current in inductor (Mass)



# Damped LC Oscillations

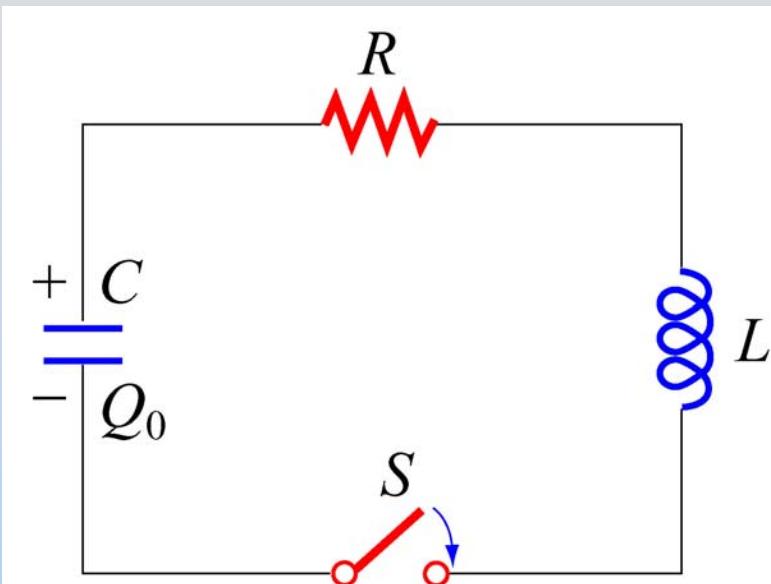

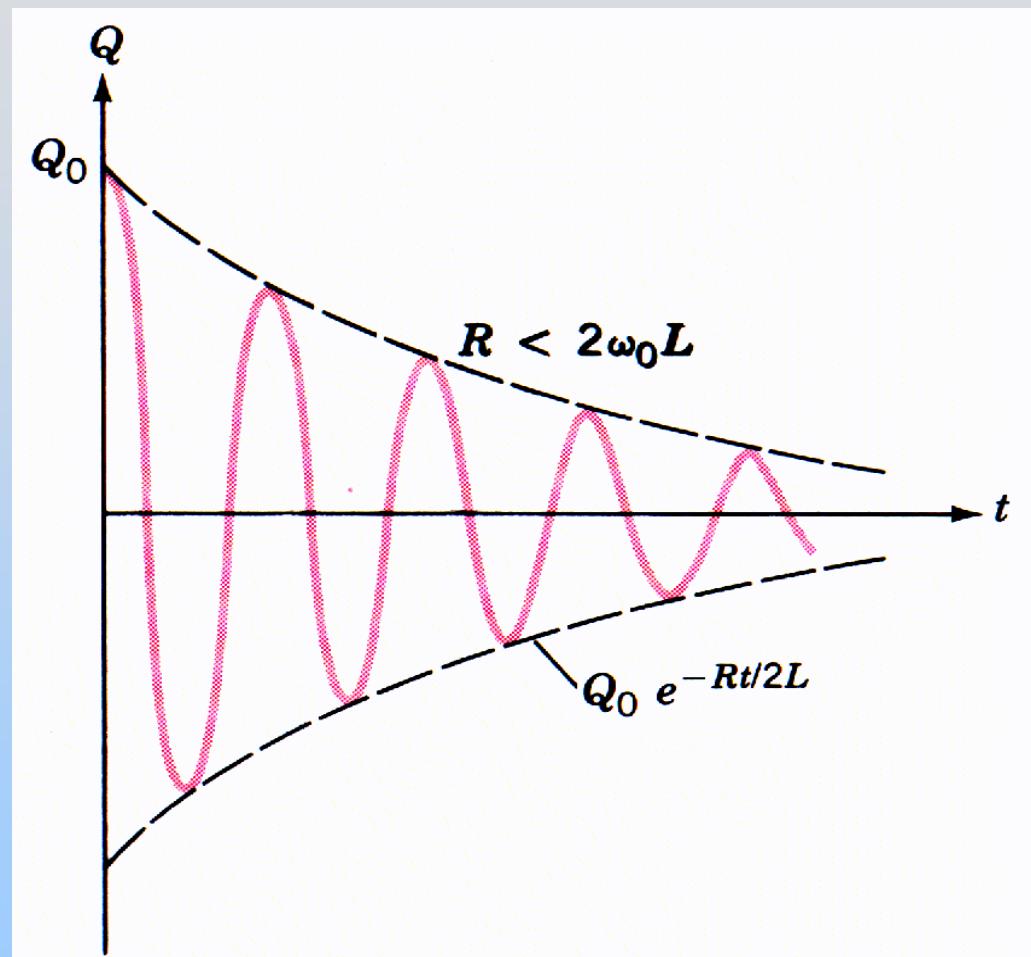
Resistor dissipates energy and system rings down over time




# Mass on a Spring: Simple Harmonic Motion` A Second Look

# Mass on a Spring


(1)

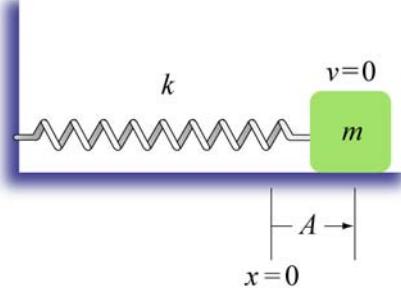


(2)

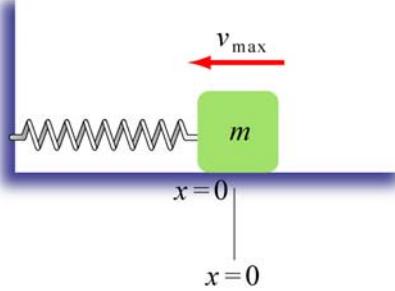

(3)

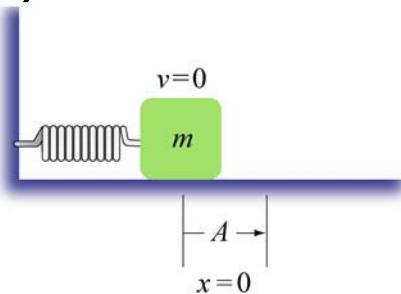

(4)

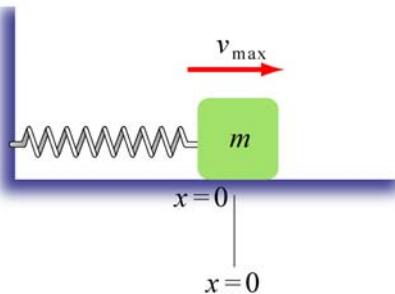

We solved this:

$$F = -kx = ma = m \frac{d^2x}{dt^2}$$

$$m \frac{d^2x}{dt^2} + kx = 0$$


Simple Harmonic Motion  
 $x(t) = x_0 \cos(\omega_0 t + \phi)$

Moves at natural frequency

What if we now move the wall?  
Push on the mass?

# **Demonstration: Driven Mass on a Spring Off Resonance**

# Driven Mass on a Spring

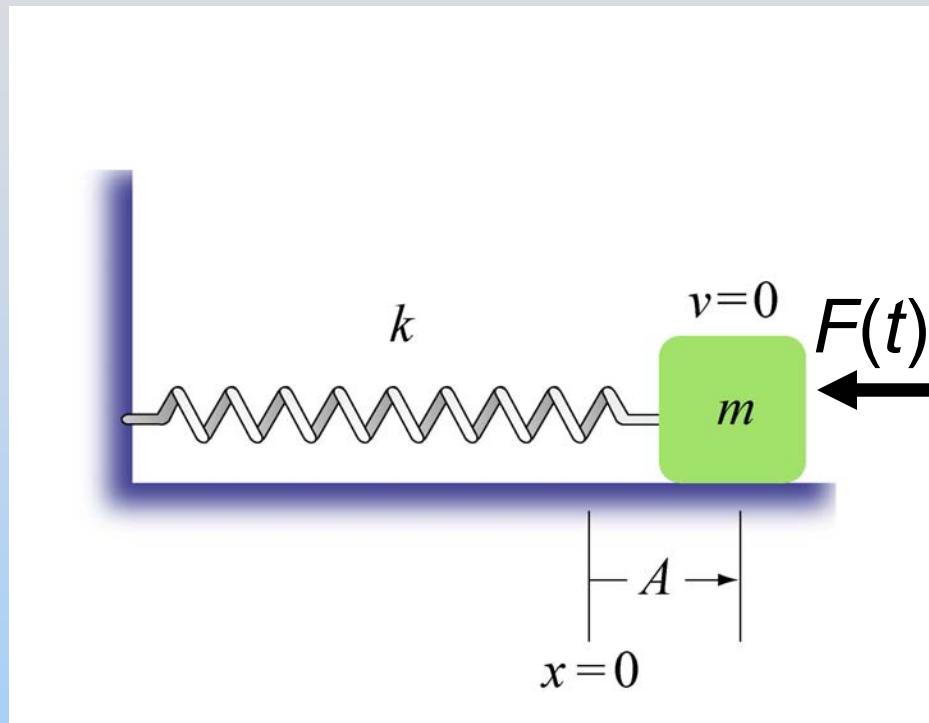

Now we get:

$$F = F(t) - kx = ma = m \frac{d^2x}{dt^2}$$

$$m \frac{d^2x}{dt^2} + kx = F(t)$$

Assume harmonic force:

$$F(t) = F_0 \cos(\omega t)$$

Simple Harmonic Motion


$$x(t) = x_{\max} \cos(\omega t + \phi)$$

Moves at driven frequency
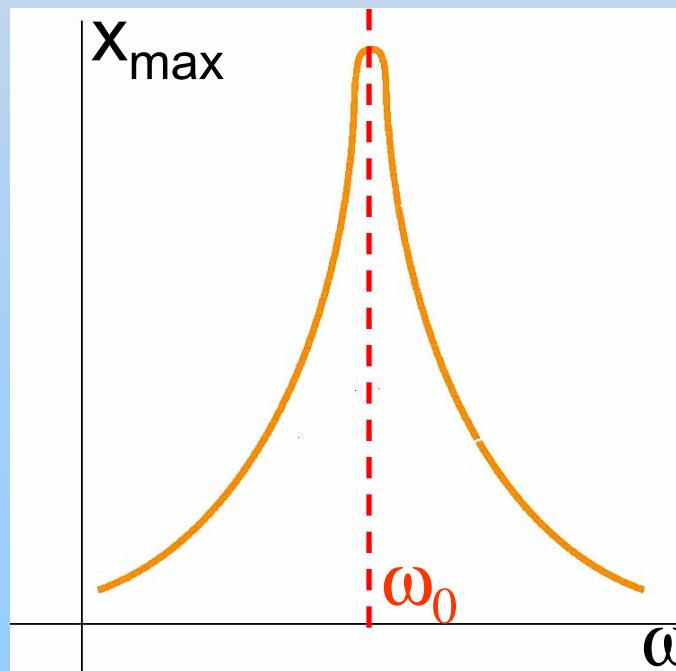
# Resonance

$$x(t) = x_{\max} \cos(\omega t + \phi)$$

Now the amplitude,  $x_{\max}$ , depends on how close the drive frequency is to the natural frequency




Let's  
See...

# **Demonstration: Driven Mass on a Spring**

# Resonance

$$x(t) = x_{\max} \cos(\omega t + \phi)$$

$x_{\max}$  depends on drive frequency

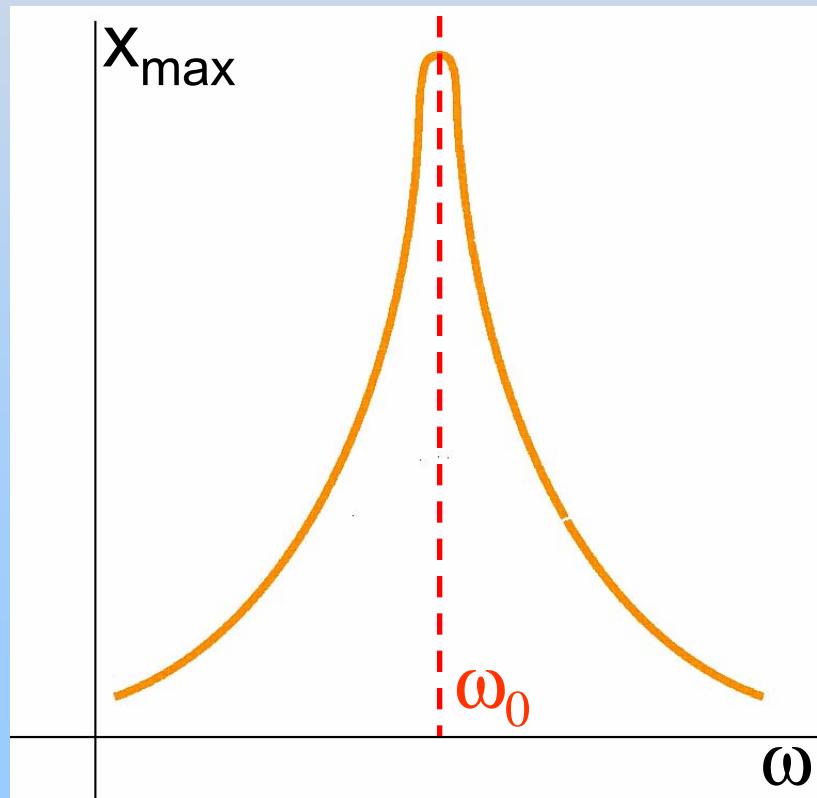

Many systems behave like this:  
Swings  
Some cars  
Musical Instruments  
...

# Electronic Analog: RLC Circuits

# Analog: RLC Circuit

Recall:

Inductors are like masses (have inertia)

Capacitors are like springs (store/release energy)

Batteries supply external force (EMF)

Charge on capacitor is like position,

Current is like velocity – watch them resonate

Now we move to “frequency dependent batteries:”

AC Power Supplies/AC Function Generators


# **Demonstration: RLC with Light Bulb**

# Start at Beginning: AC Circuits

# Alternating-Current Circuit

- direct current (dc) – current flows one way (battery)
- alternating current (ac) – current oscillates
- sinusoidal voltage source


$$V(t) = V_0 \sin \omega t$$

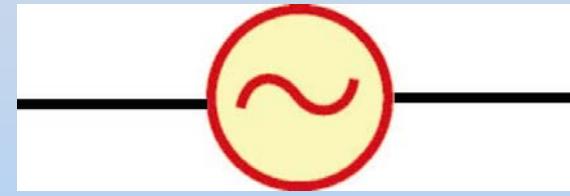

$\omega = 2\pi f$ : angular frequency

$V_0$ : voltage amplitude

# AC Circuit: Single Element

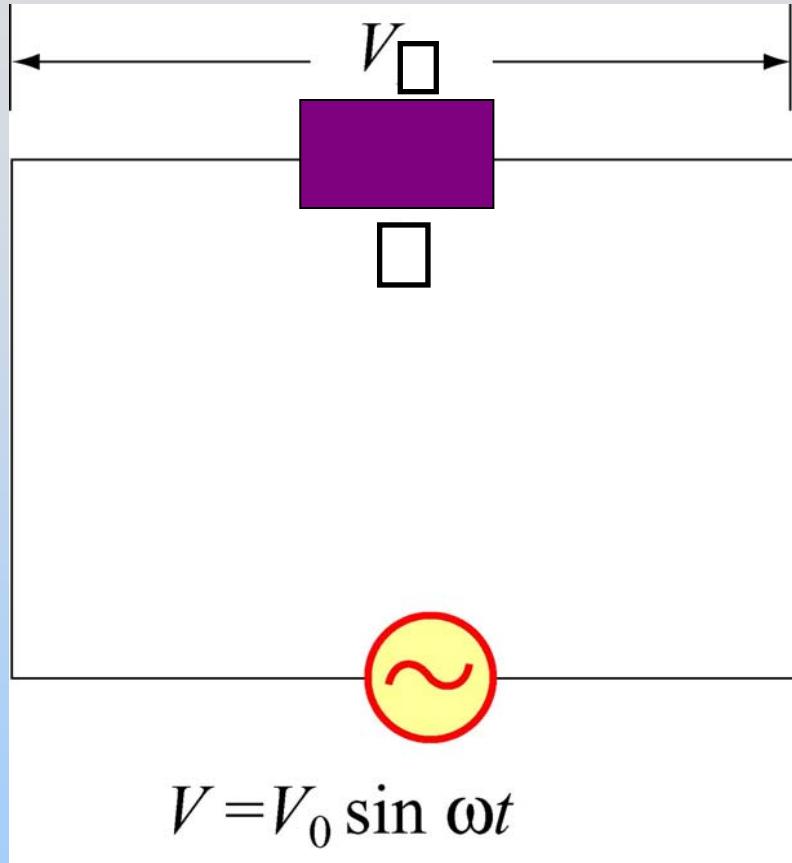

$$V_{\square} = V$$


$$= V_0 \sin \omega t$$

$$I(t) = I_0 \sin(\omega t - \phi)$$

Questions:

1. What is  $I_0$ ?
2. What is  $\phi$ ?


# AC Circuit: Resistors

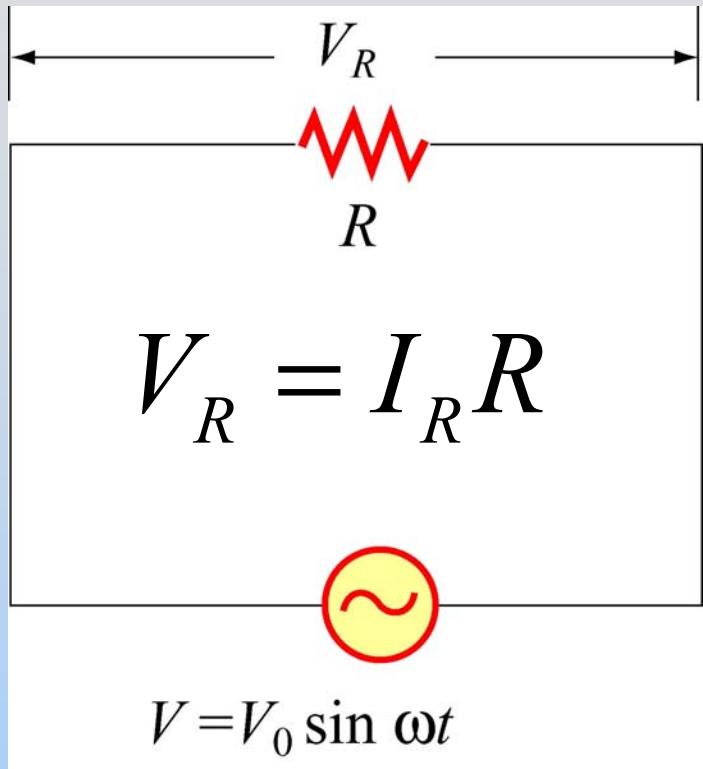


$$I_R = \frac{V_R}{R} = \frac{V_0}{R} \sin \omega t$$
$$= I_0 \sin (\omega t - 0)$$

$$I_0 = \frac{V_0}{R}$$
$$\varphi = 0$$

$I_R$  and  $V_R$  are in phase

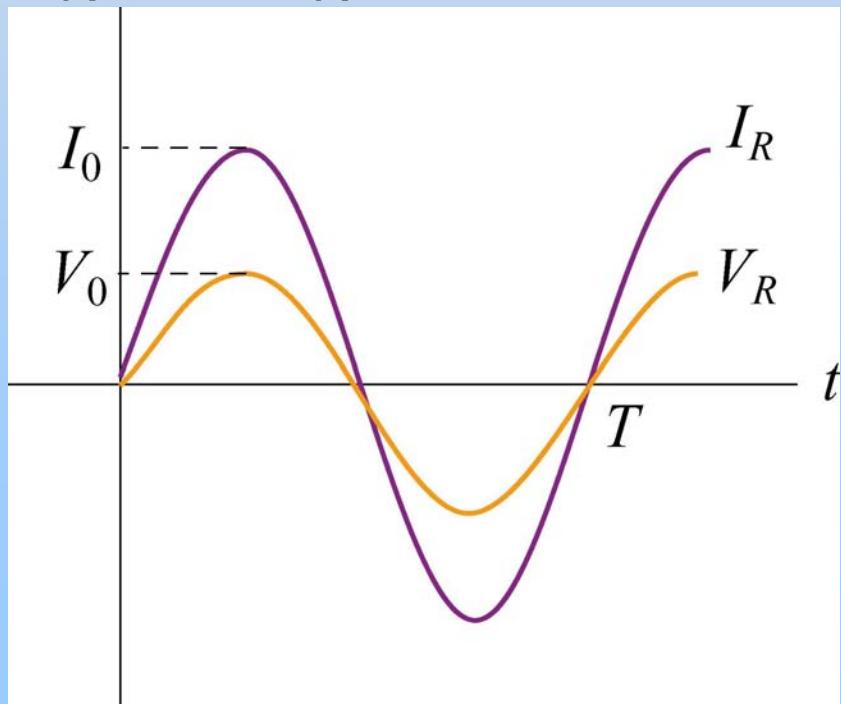


# AC Circuit: Capacitors

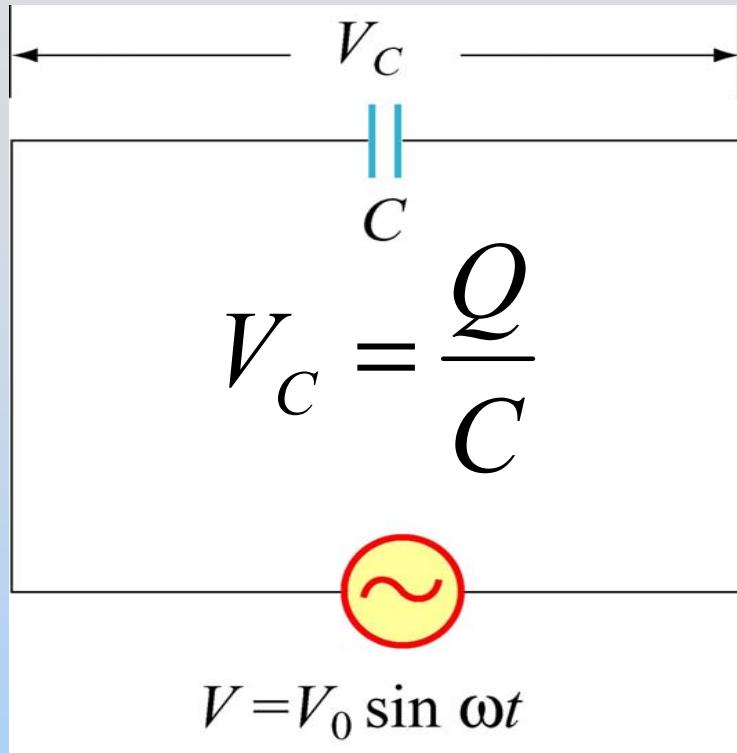

$$\begin{aligned} I_C(t) &= \frac{dQ}{dt} \\ &= \omega C V_0 \cos \omega t \\ &= I_0 \sin(\omega t - \pi/2) \end{aligned}$$


$$\begin{aligned} I_0 &= \omega C V_0 \\ \varphi &= -\pi/2 \end{aligned}$$

$I_C$  leads  $V_C$  by  $\pi/2$

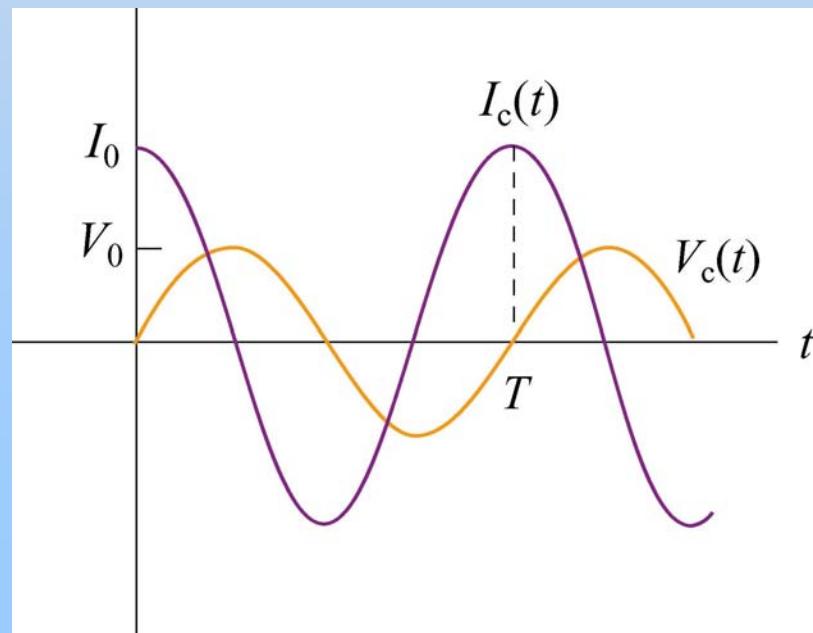

$$Q(t) = CV_C = CV_0 \sin \omega t$$

# AC Circuit: Inductors

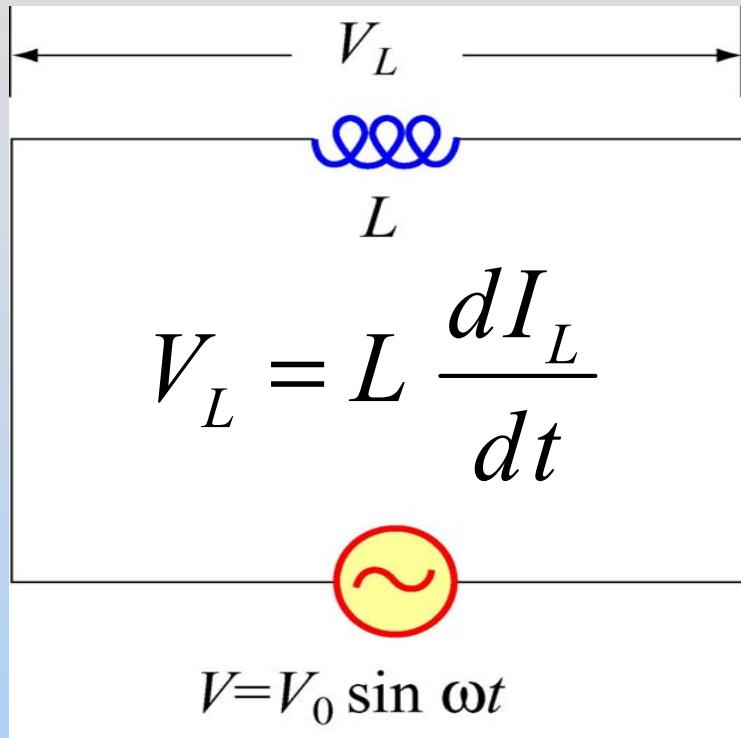


$$\frac{dI_L}{dt} = \frac{V_L}{L} = \frac{V_0}{L} \sin \omega t$$

$$\begin{aligned} I_L(t) &= \frac{V_0}{L} \int \sin \omega t \, dt \\ &= -\frac{V_0}{\omega L} \cos \omega t \\ &= I_0 \sin(\omega t - \pi/2) \end{aligned}$$

$$I_0 = \frac{V_0}{\omega L}$$

$$\varphi = \frac{\pi}{2}$$

$I_L$  lags  $V_L$  by  $\pi/2$

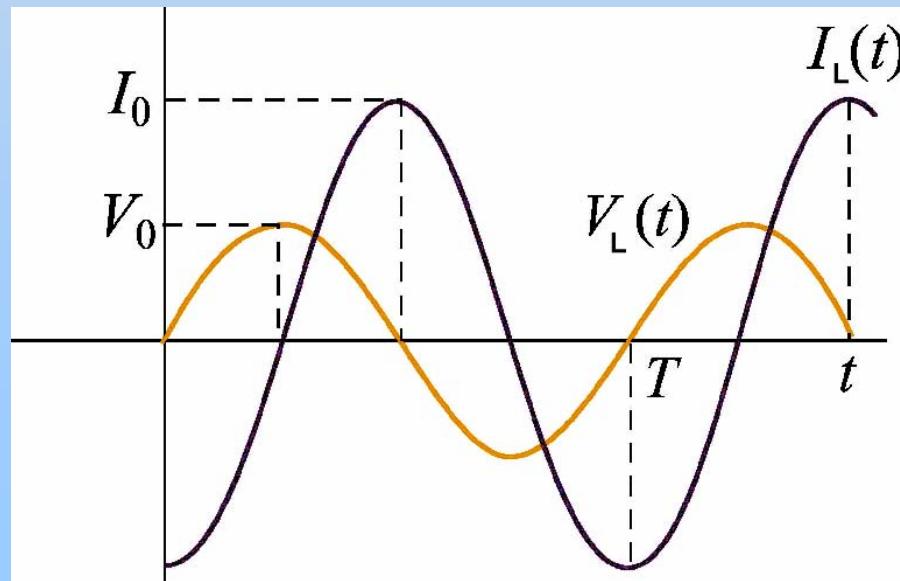

# AC Circuits: Summary

Element	$I_0$	Current vs. Voltage	Resistance Reactance Impedance
Resistor	$\frac{V_{0R}}{R}$	In Phase	$R = R$
Capacitor	$\omega C V_{0C}$	Leads	$X_C = \frac{1}{\omega C}$
Inductor	$\frac{V_{0L}}{\omega L}$	Lags	$X_L = \omega L$


Although derived from single element circuits,  
these relationships hold generally!

# **PRS Question: Leading or Lagging?**

# Phasor Diagram

Nice way of tracking magnitude & phase:


$$V(t) = V_0 \sin(\omega t)$$

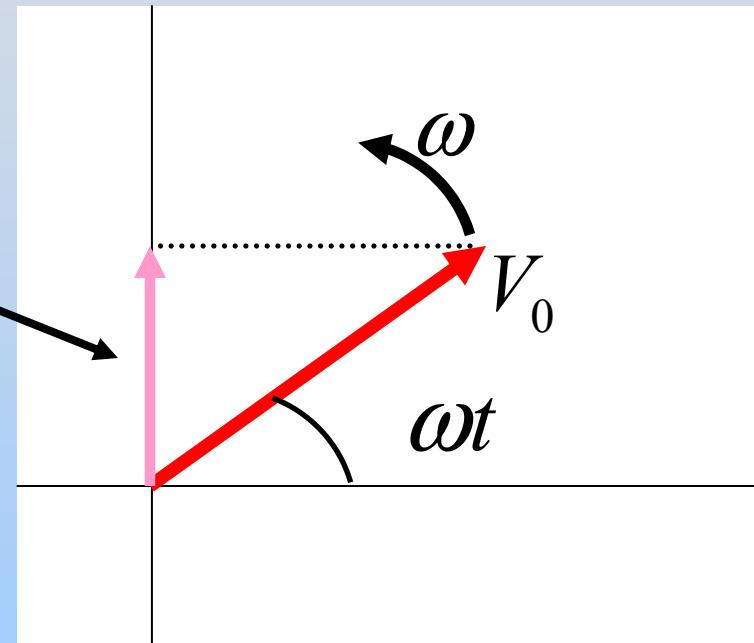

- Notes:
- (1) As the phasor (red vector) rotates, the projection (pink vector) oscillates
  - (2) Do both for the current and the voltage

# **Demonstration: Phasors**


# Phasor Diagram: Resistor

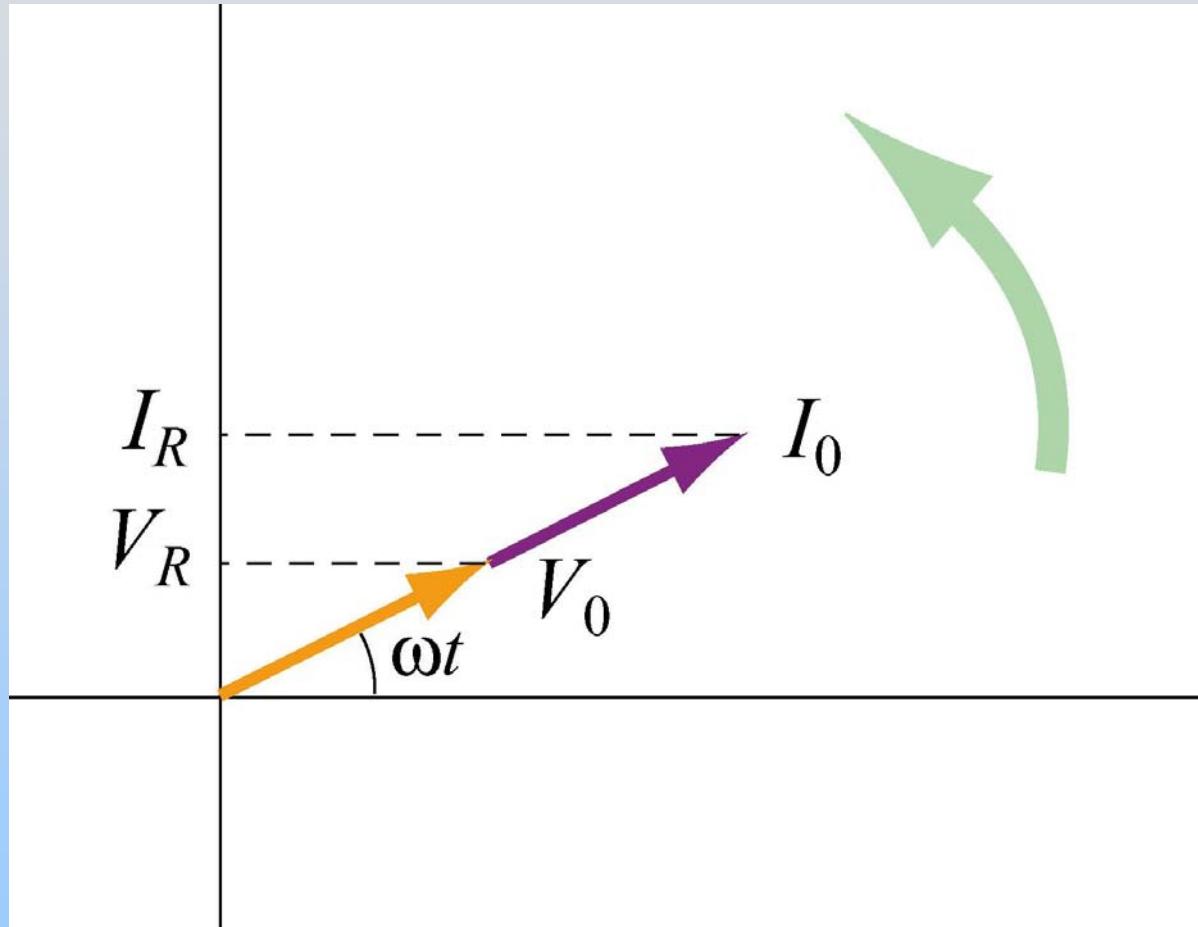

$$V_0 = I_0 R$$
$$\varphi = 0$$

$I_R$  and  $V_R$  are in phase


# Phasor Diagram: Capacitor

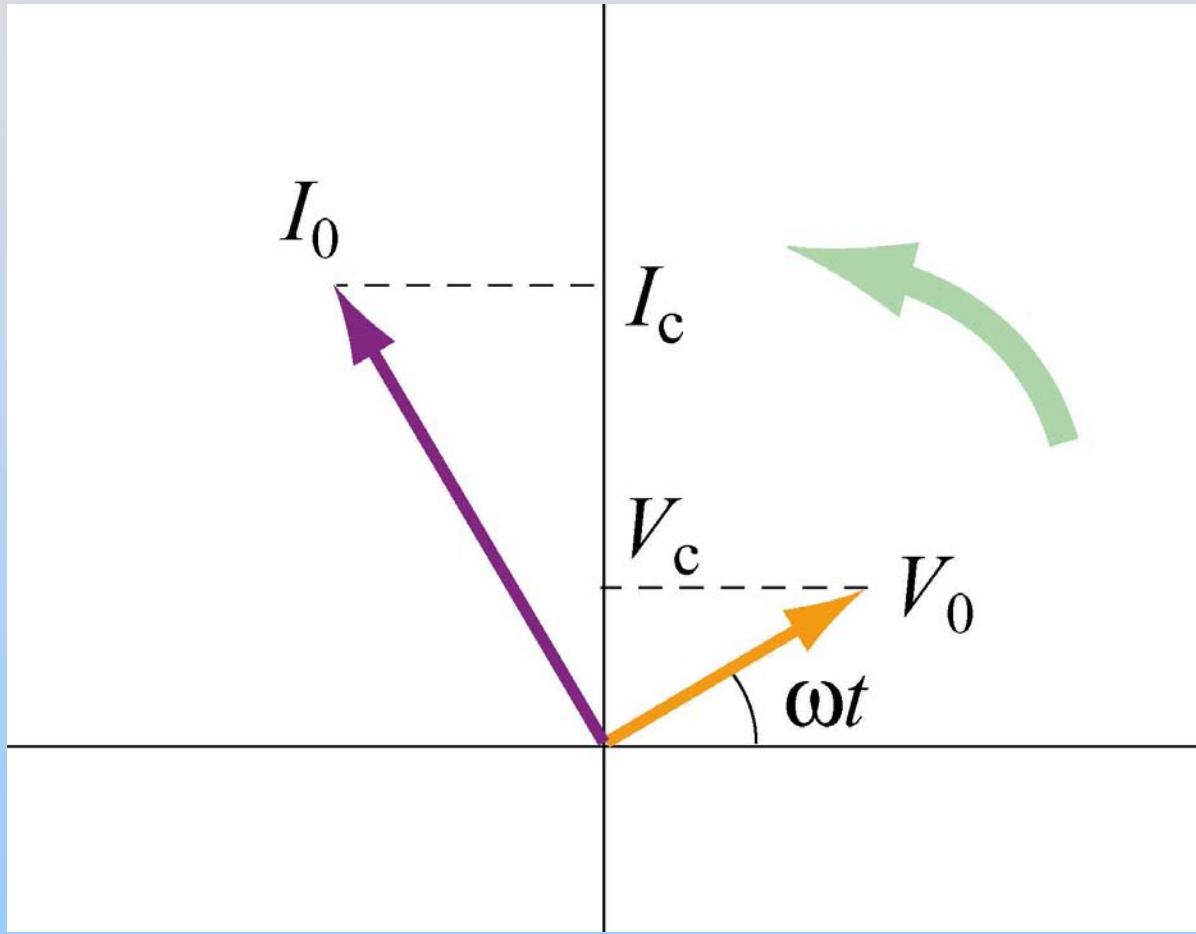

$I_C$  leads  $V_C$  by  $\pi/2$

$$\begin{aligned}V_0 &= I_0 X_C \\&= I_0 \frac{1}{\omega C} \\&\varphi = -\pi/2\end{aligned}$$

# Phasor Diagram: Inductor

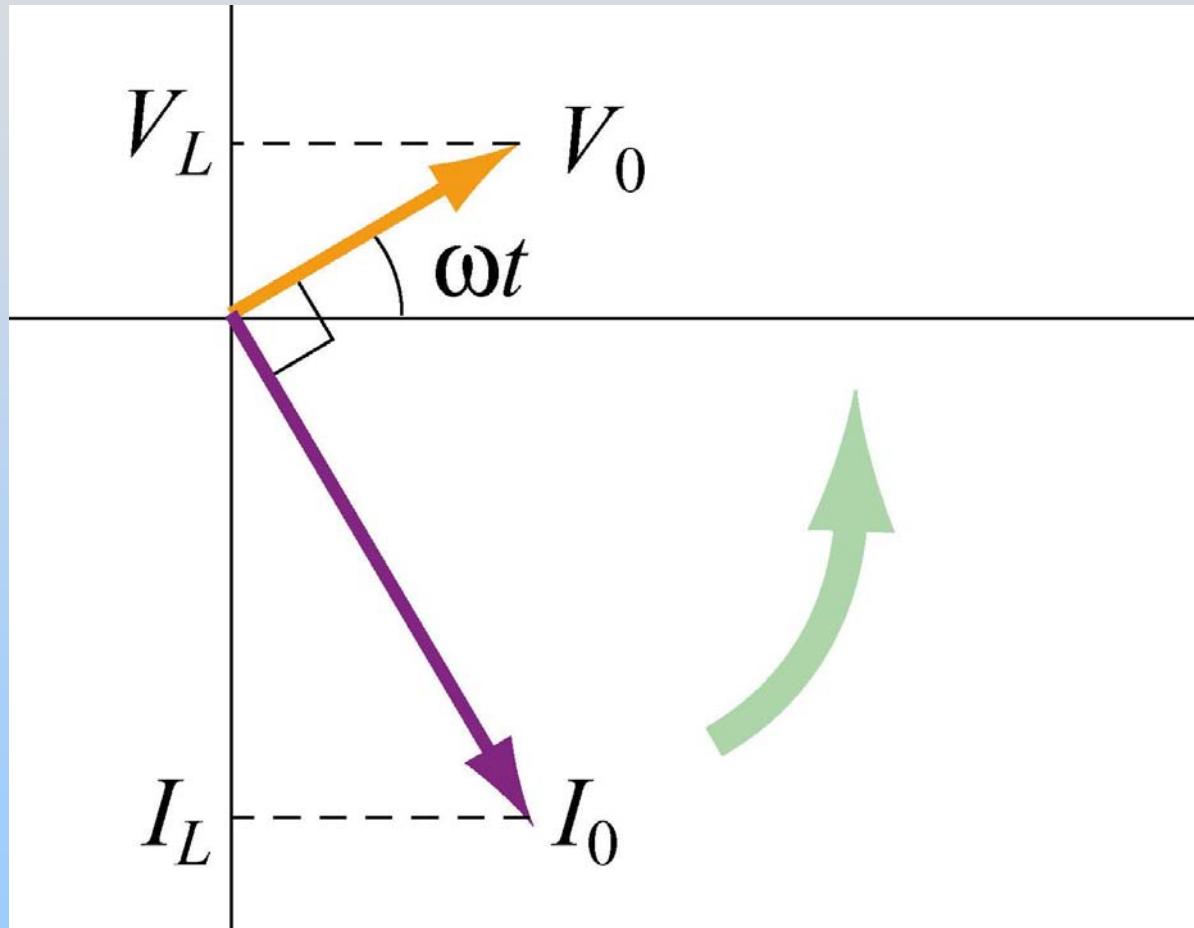

$$\begin{aligned}V_0 &= I_0 X_L \\&= I_0 \omega L \\\varphi &= \frac{\pi}{2}\end{aligned}$$

$I_L$  lags  $V_L$  by  $\pi/2$

# **PRS Questions: Phase**

# Put it all together: Driven RLC Circuits

# Question of Phase

We had fixed phase of voltage:


$$V = V_0 \sin \omega t \quad I(t) = I_0 \sin(\omega t - \phi)$$

It's the same to write:

$$V = V_0 \sin(\omega t + \phi) \quad I(t) = I_0 \sin \omega t$$

(Just shifting zero of time)

# Driven RLC Series Circuit

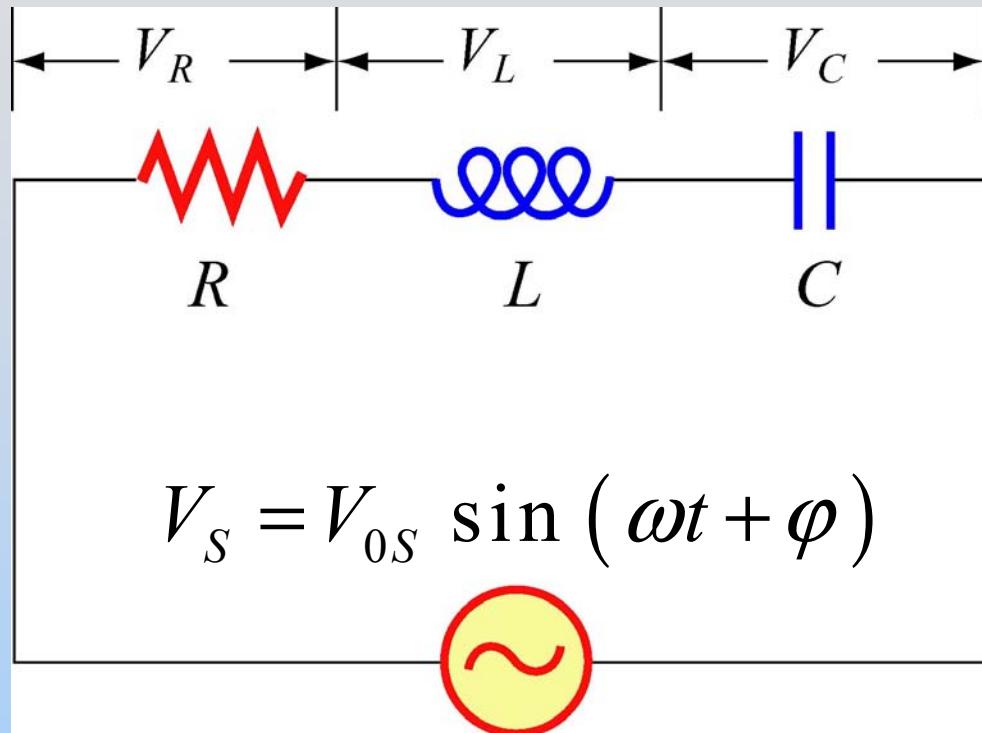

$$I(t) = I_0 \sin(\omega t)$$

$$V_R = V_{R0} \sin(\omega t)$$

$$V_L = V_{L0} \sin\left(\omega t + \frac{\pi}{2}\right)$$



$$V_C = V_{C0} \sin\left(\omega t - \frac{\pi}{2}\right)$$

What is  $I_0$  (and  $V_{R0} = I_0 R$ ,  $V_{L0} = I_0 X_L$ ,  $V_{C0} = I_0 X_C$ )?

What is  $\varphi$ ? Does the current lead or lag  $V_s$ ?

Must Solve:  $V_s = V_R + V_L + V_C$



# Driven RLC Series Circuit

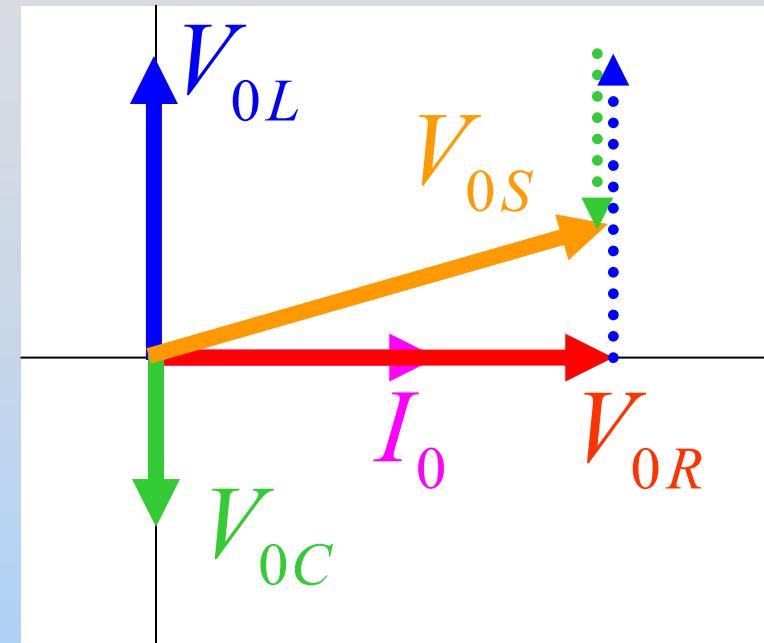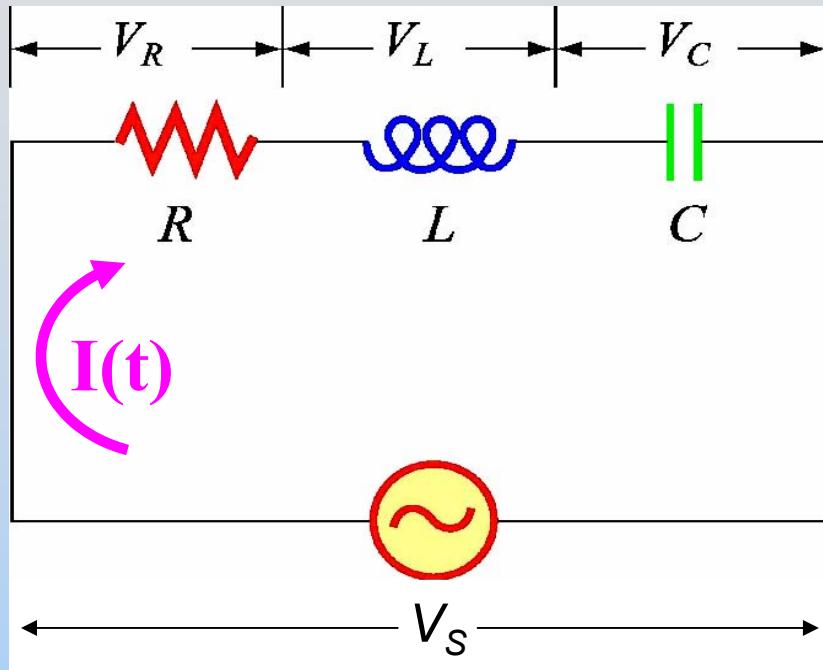

Now Solve:  $V_s = V_R + V_L + V_C$

Now we just need to read the phasor diagram!

# Driven RLC Series Circuit

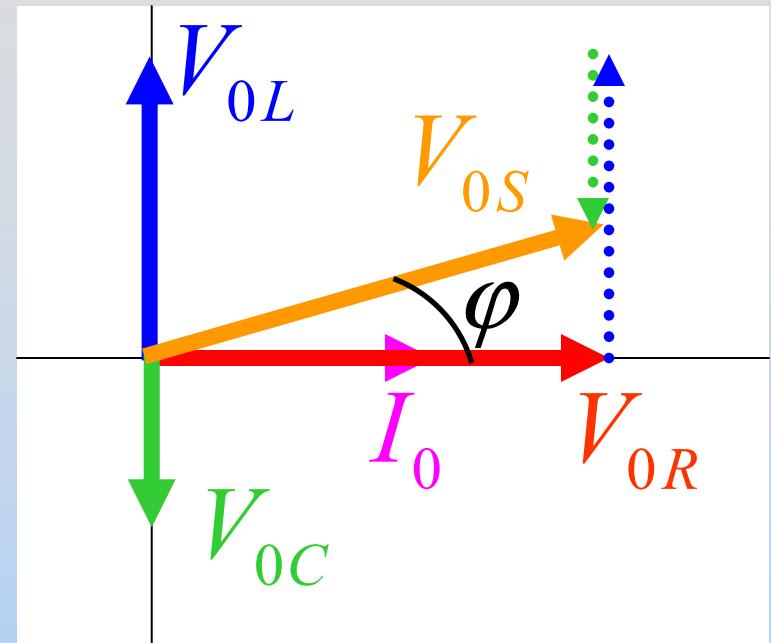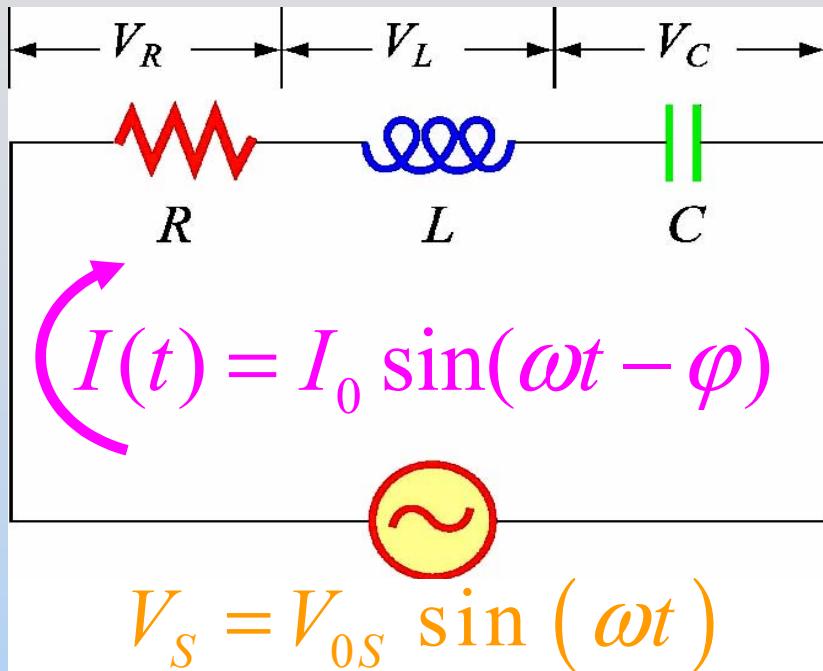

$$V_{0s} = \sqrt{V_{R0}^2 + (V_{L0} - V_{C0})^2} = I_0 \sqrt{R^2 + (X_L - X_C)^2} \equiv I_0 Z$$


$$I_0 = \frac{V_{0s}}{Z}$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

Impedance

$$\phi = \tan^{-1} \left( \frac{X_L - X_C}{R} \right)$$

# Plot I, V's vs. Time

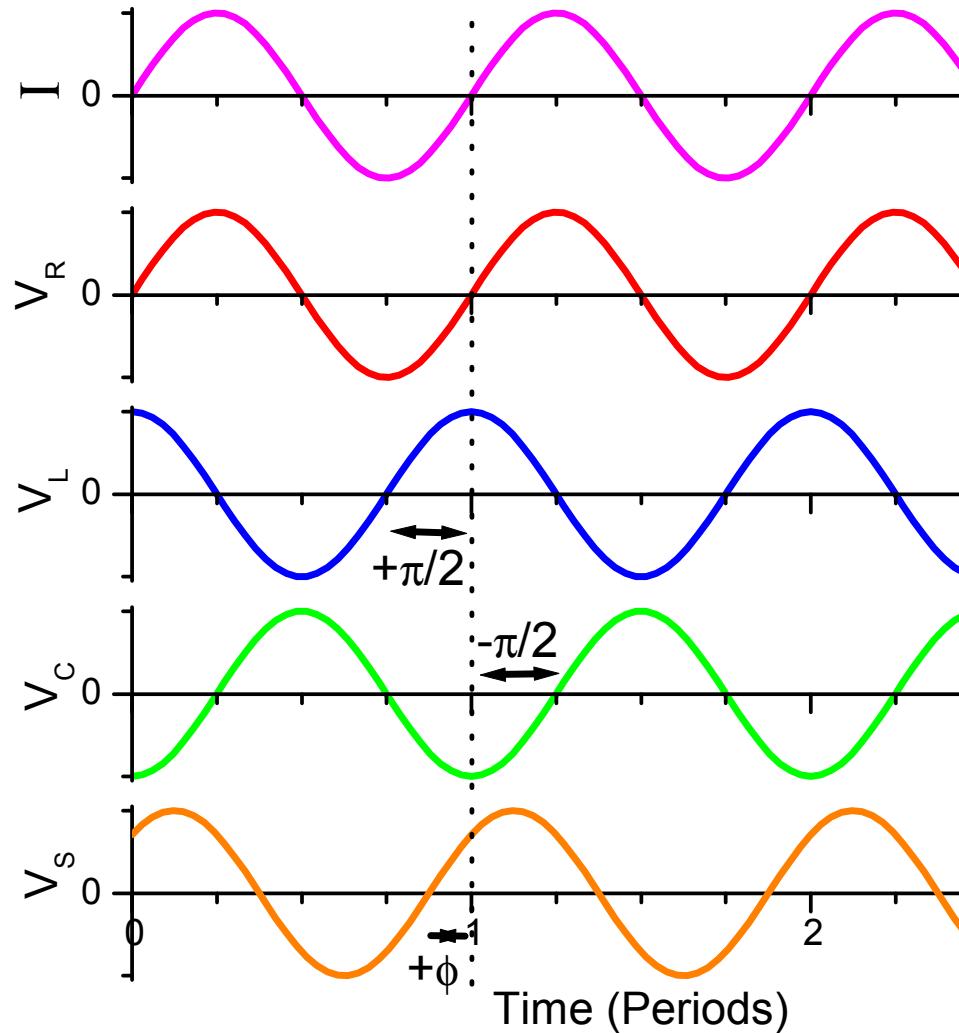

$$I(t) = I_0 \sin(\omega t)$$

$$V_R(t) = I_0 R \sin(\omega t)$$

$$V_L(t) = I_0 X_L \sin\left(\omega t + \frac{\pi}{2}\right)$$

$$V_C(t) = I_0 X_C \sin\left(\omega t - \frac{\pi}{2}\right)$$

$$V_S(t) = V_{S0} \sin(\omega t + \varphi)$$

# **PRS Question: Who Dominates?**

# RLC Circuits: Resonances

# Resonance

$$I_0 = \frac{V_0}{Z} = \frac{V_0}{\sqrt{R^2 + (X_L - X_C)^2}} ; \quad X_L = \omega L, \quad X_C = \frac{1}{\omega C}$$

At very low frequencies, C dominates ( $X_C \gg X_L$ ):  
it fills up and keeps the current low

At very high frequencies, L dominates ( $X_L \gg X_C$ ):  
the current tries to change but it won't let it


At intermediate frequencies we have **resonance**

$I_0$  reaches maximum when  $X_L = X_C$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$
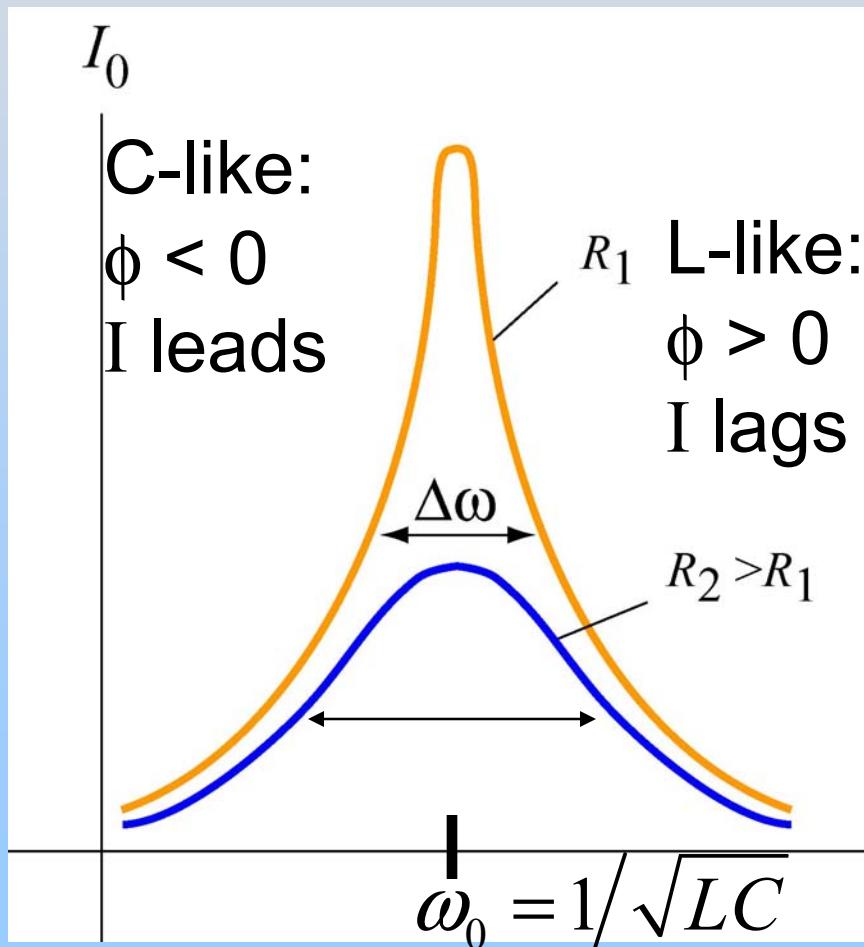
# Resonance

$$I_0 = \frac{V_0}{Z} = \frac{V_0}{\sqrt{R^2 + (X_L - X_C)^2}} ; \quad X_L = \omega L, \quad X_C = \frac{1}{\omega C}$$



$$\phi = \tan^{-1} \left( \frac{X_L - X_C}{R} \right)$$

# **Demonstration: RLC with Light Bulb**

# **PRS Questions: Resonance**

# **Experiment 11:**

# **Driven RLC Circuit**

# Experiment 11: How To

## Part I

- Use exp11a.ds
- Change frequency, look at I & V. Try to find resonance – place where I is maximum

## Part II

- Use exp11b.ds
- Run the program at each of the listed frequencies to make a plot of  $I_0$  vs.  $\omega$