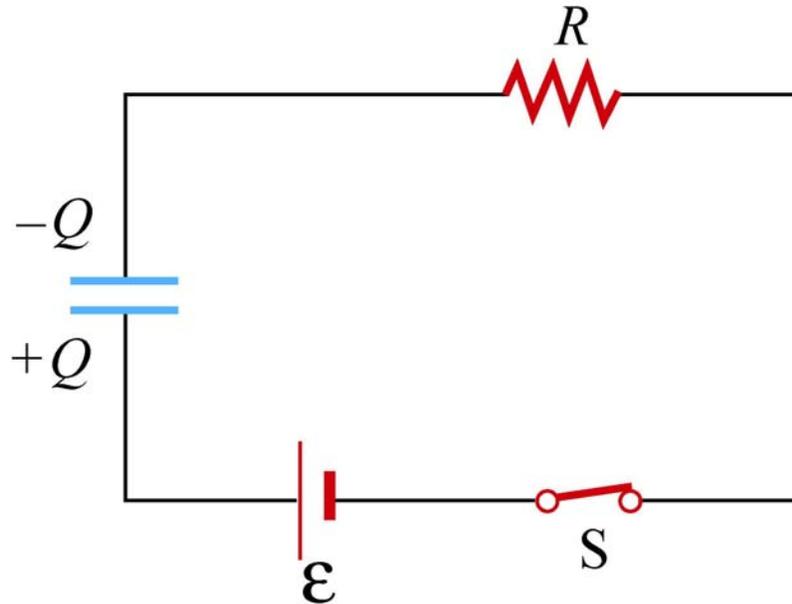



RC Circuit



An uncharged capacitor is connected to a dc voltage source via a switch. A resistor is placed in series with the capacitor. The switch is initially open. At $t = 0$, the switch is closed. A very long time after the switch is closed, the current in the circuit is

1. nearly zero
2. at a maximum and decreasing
3. nearly constant but non-zero

RC Circuit

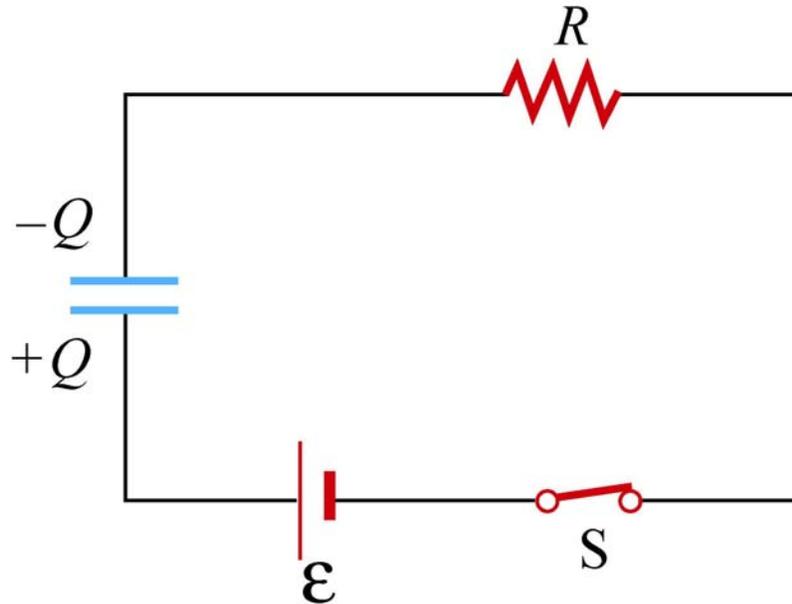


An uncharged capacitor is connected to a dc voltage source via a switch. A resistor is placed in series with the capacitor. The switch is initially open. At $t = 0$, the switch is closed. Just after the switch is closed, the current in the circuit is

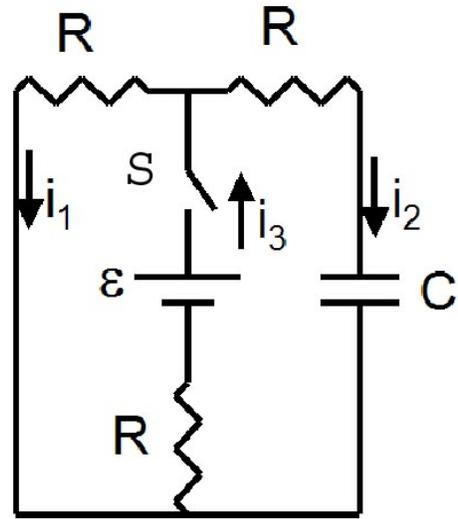1. zero and increasing
2. at a maximum and decreasing
3. constant but non-zero

MULTILOOP CIRCUIT WITH CAPACITOR

An uncharged capacitor is connected to a dc voltage source in the circuit shown. The switch is initially open. At $t = 0$, the switch is closed. A *long time after* the switch S is closed, the current i_3 is



- 1) $\epsilon / 3R$
- 2) $\epsilon / 2R$
- 3) $3\epsilon / 2R$
- 4) $2\epsilon / 3R$
- 5) Don't Know