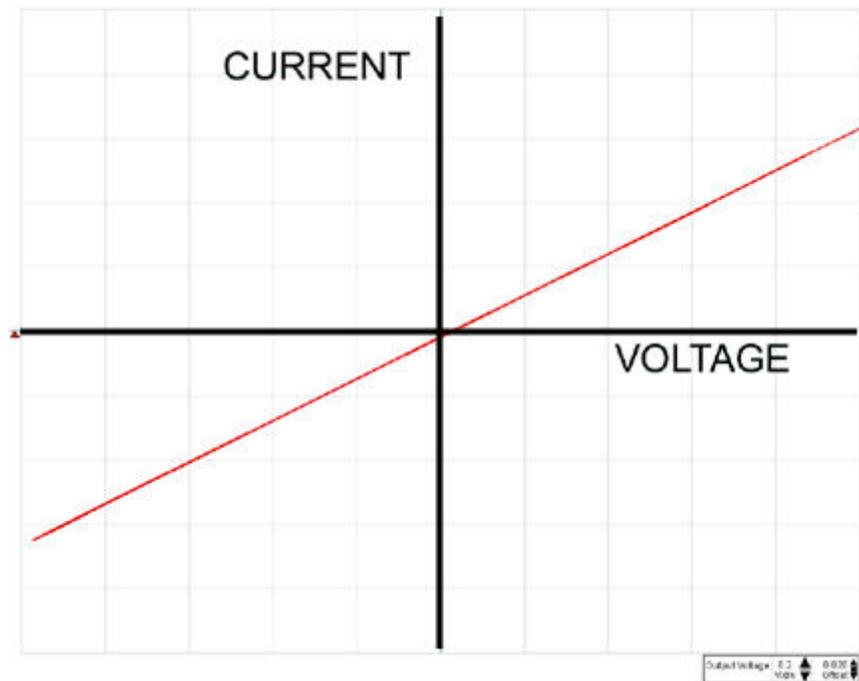



The plot shows the driving voltage V (black curve) and the current I (red curve) in a driven RLC circuit. In this circuit,

- 1. The current leads the voltage**
- 2. The current lags the voltage**
- 3. Don't have a clue**




The graph shows the current versus the voltage in a driven RLC circuit at a given driving frequency. In this plot

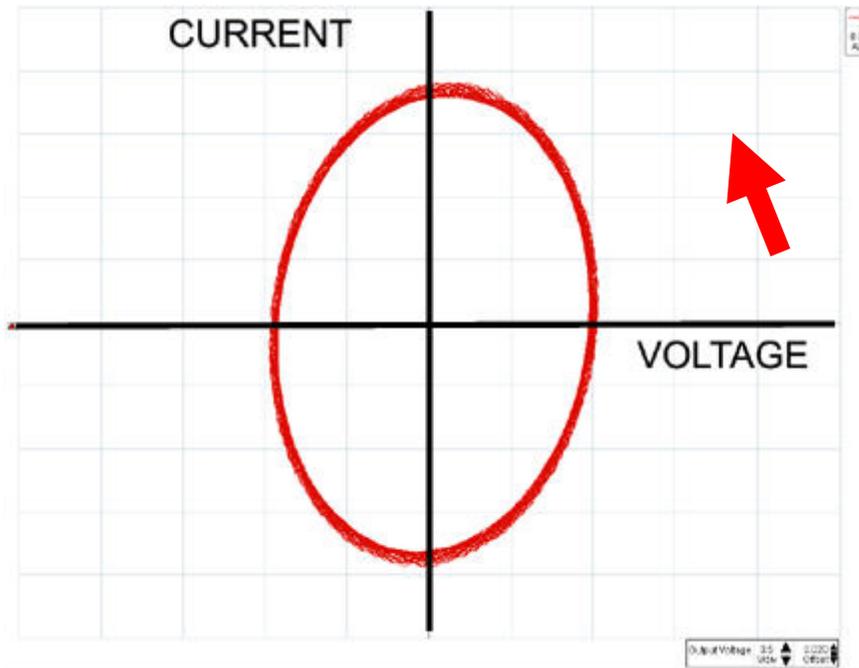- 1. The current leads the voltage by about 45 degrees.**
- 2. The current lags the voltage by about 45 degrees**
- 3. The current and the voltage are in phase**
- 4. Don't have a clue.**




The graph shows the current versus the voltage in a driven RLC circuit at a given driving frequency. In this plot

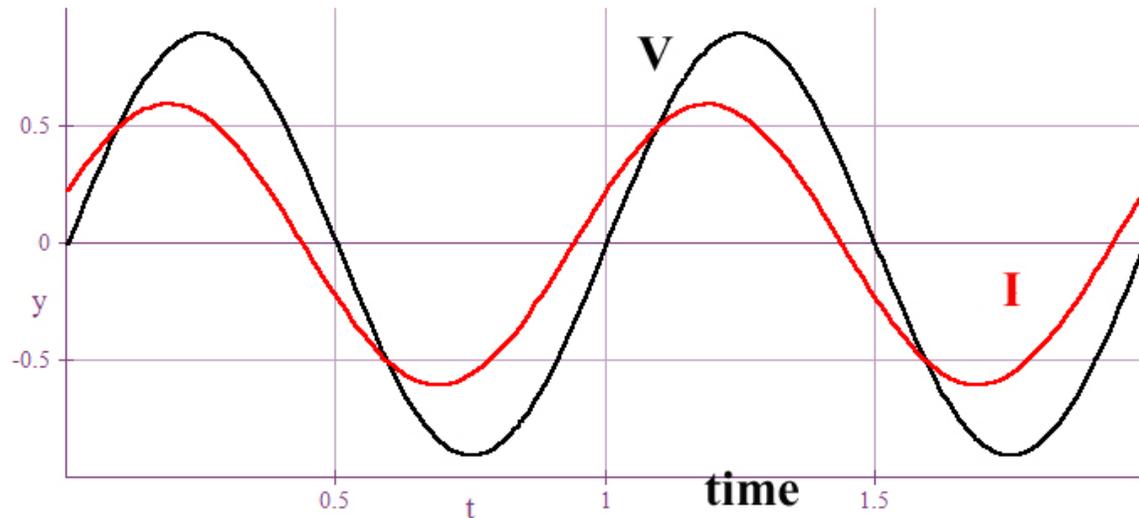- 1. Current lags voltage by $\sim 90^\circ$**
- 2. Current leads voltage by $\sim 90^\circ$**
- 3. Current and voltage are almost in phase**
- 4. We don't have enough information to say whether the current leads or lags (but they aren't in phase!)**



The graph shows the current versus the voltage in a driven RLC circuit at a particular driving frequency. At this frequency, the circuit is dominated by its

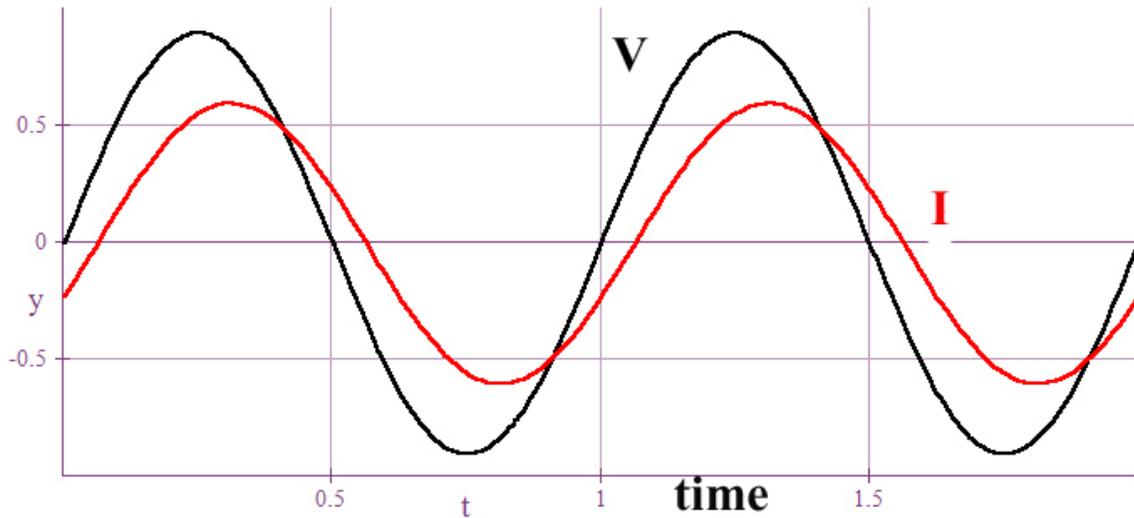- 1. Resistance**
- 2. Inductance**
- 3. Capacitance**
- 4. Don't have a clue**



The graph shows the current versus the voltage in a driven RLC circuit at a particular driving frequency. Is this frequency above or below the resonance frequency of the circuit?

- 1. Above the resonance frequency**
- 2. Below the resonance frequency**
- 3. Don't have a clue**