
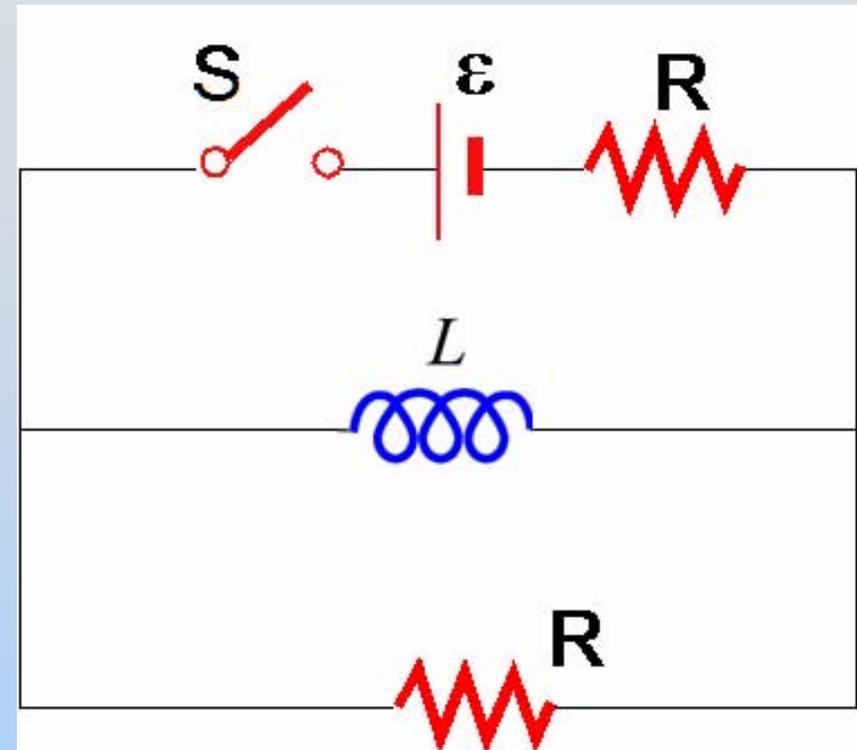


Group Problem: Circuits

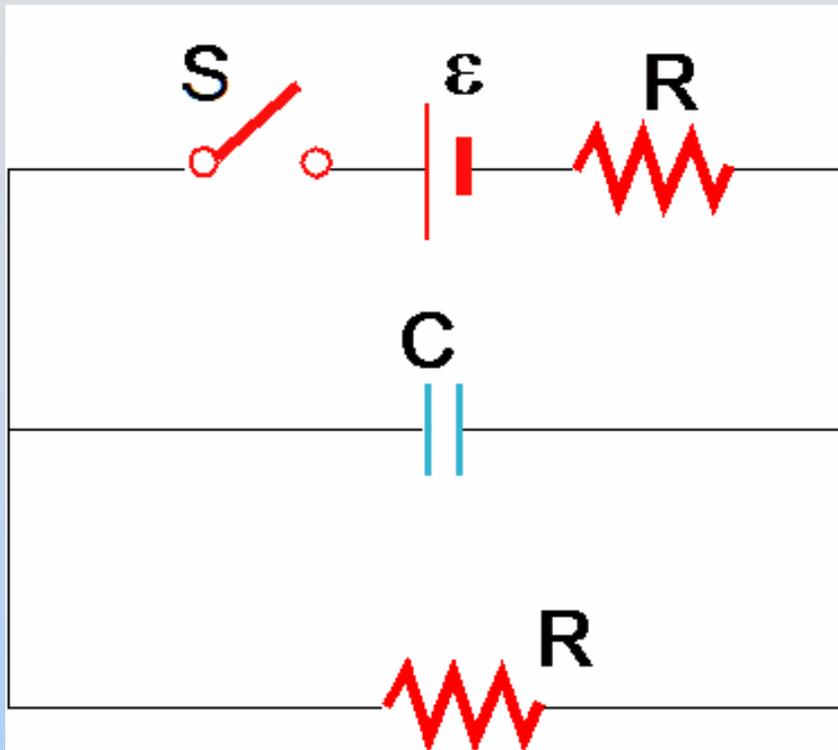

For the two above circuits sketch the currents through the two bottom branches as a function of time (switch closes at $t = 0$, opens at $t = T$). State values at $t = 0^+$, T^- , T^+