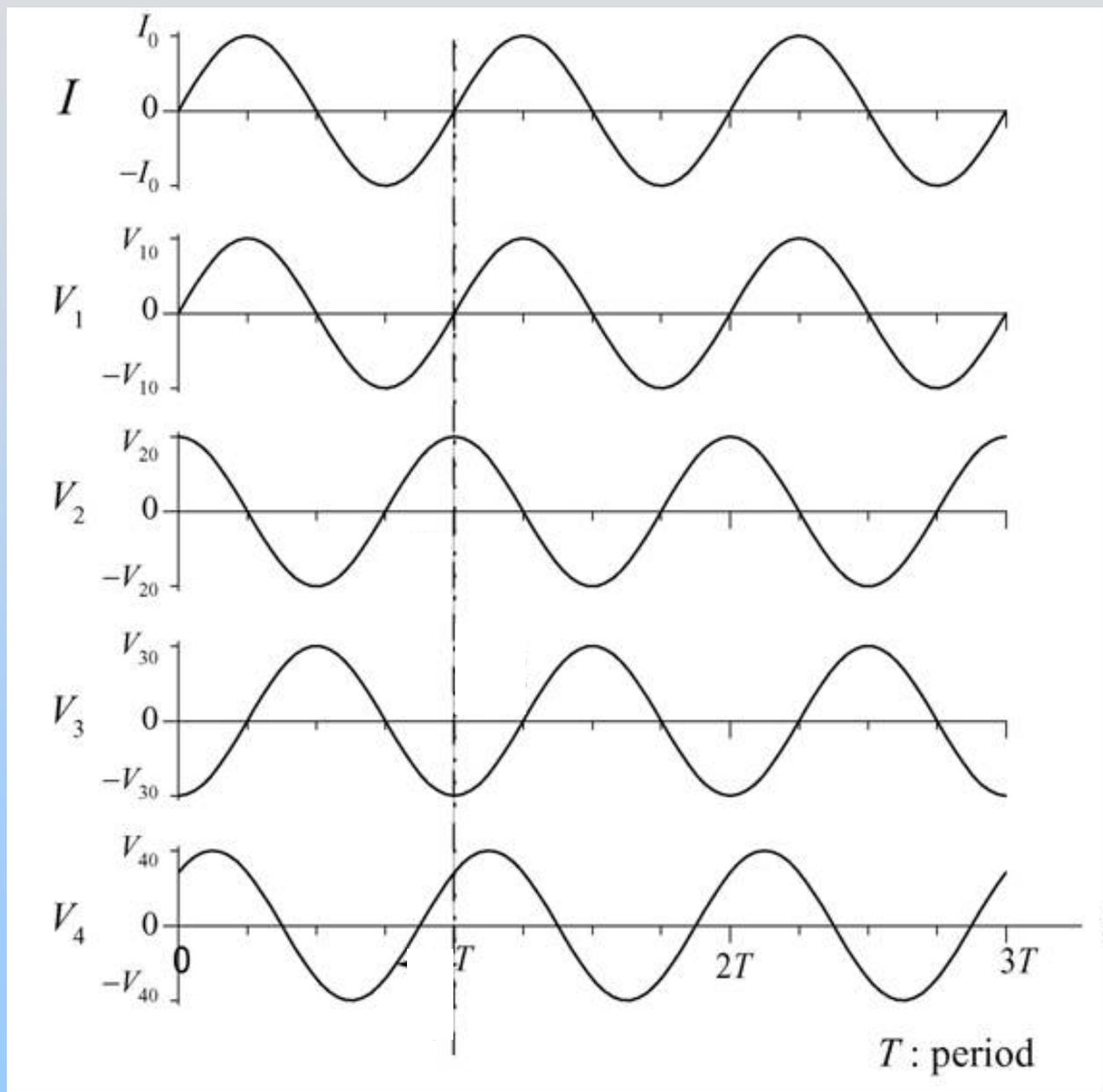


# Group Problem



Consider an RLC circuit. You measure the voltage across all 4 elements ( $V_1 \dots$ )  
 Which is which?  
 Are we above or below resonance?  
 What are  $R, L, C$ ?  
 What is  $\omega_0$ ?