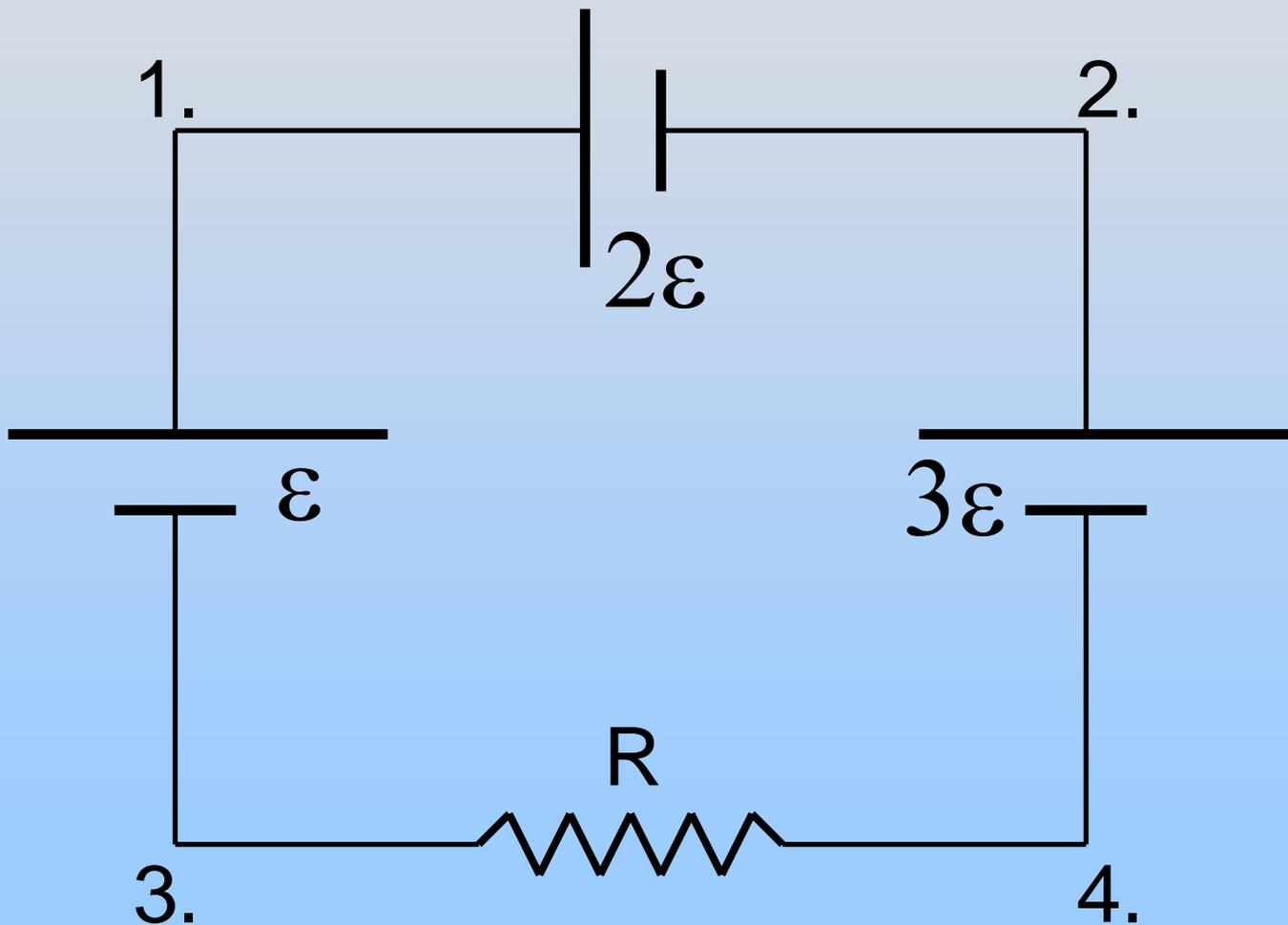


Concept Question: Potential in Circuits

Where is the potential the highest in the below circuit?




- 1. 1
- 2. 2
- 3. 3
- 4. 4

Concept Question: Bulbs & Batteries


An ideal battery is hooked to a light bulb with wires. A second identical light bulb is connected in parallel to the first light bulb. After the second light bulb is connected, the current from the battery compared to when only one bulb was connected.

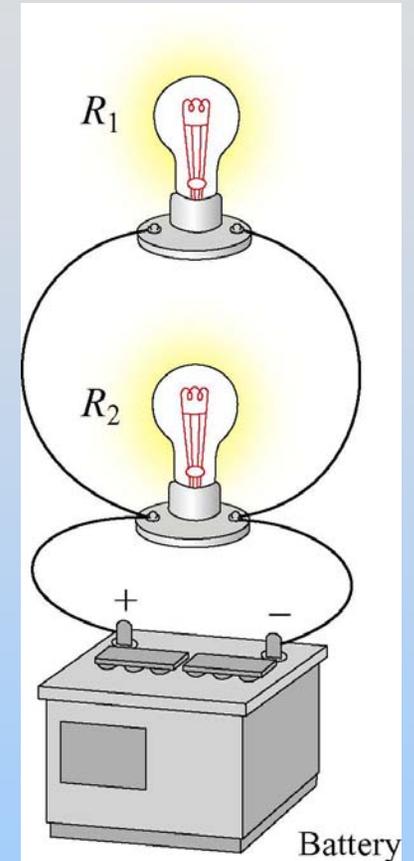1. Is Higher
2. Is Lower
3. Is The Same
4. Don't know



Concept Question: Bulbs & Batteries

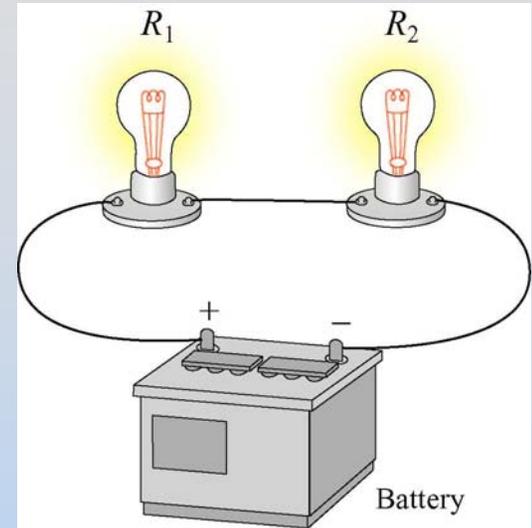An ideal battery is hooked to a light bulb with wires. A second identical light bulb is connected in series with the first light bulb. After the second light bulb is connected, the current from the battery compared to when only one bulb was connected.



1. Is Higher
2. Is Lower
3. Is The Same
4. Don't know

MIT OpenCourseWare
<http://ocw.mit.edu>

8.02SC Physics II: Electricity and Magnetism
Fall 2010

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.