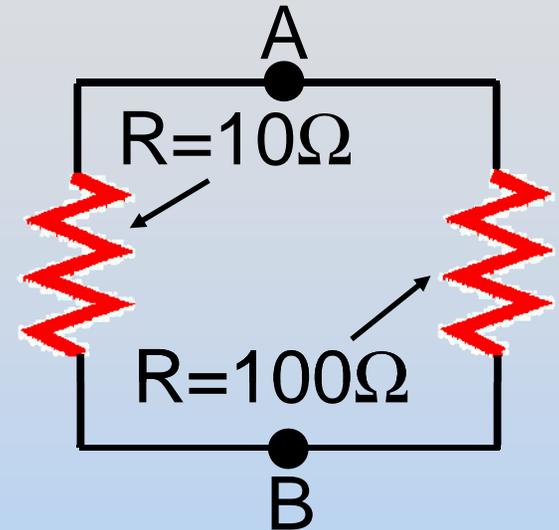


Concept Question: Faraday Circuit

A magnetic field B penetrates this circuit outwards, and is increasing at a rate such that a current of 1 A is induced in the circuit (which direction?).


The potential difference $V_A - V_B$ is:

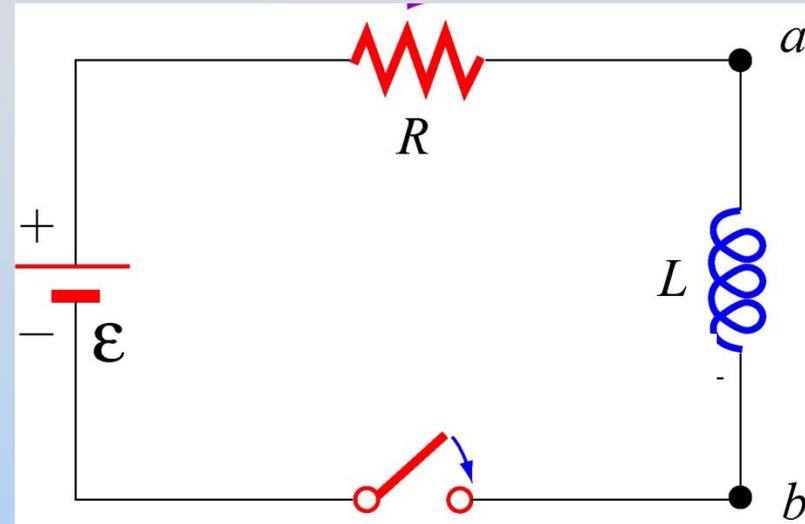1. $+10\text{ V}$
2. -10 V
3. $+100\text{ V}$
4. -100 V
5. $+110\text{ V}$
6. -110 V
7. $+90\text{ V}$
8. -90 V
9. None of the above



Concept Question: Voltage Across Inductor

In the circuit at right the switch is closed at $t = 0$. A voltmeter hooked across the inductor will read:



1. $V_L = \epsilon e^{-t/\tau}$
2. $V_L = \epsilon(1 - e^{-t/\tau})$
3. $V_L = 0$
4. I don't know


Concept Question: Inserting a Core

When you insert the iron core what happens?

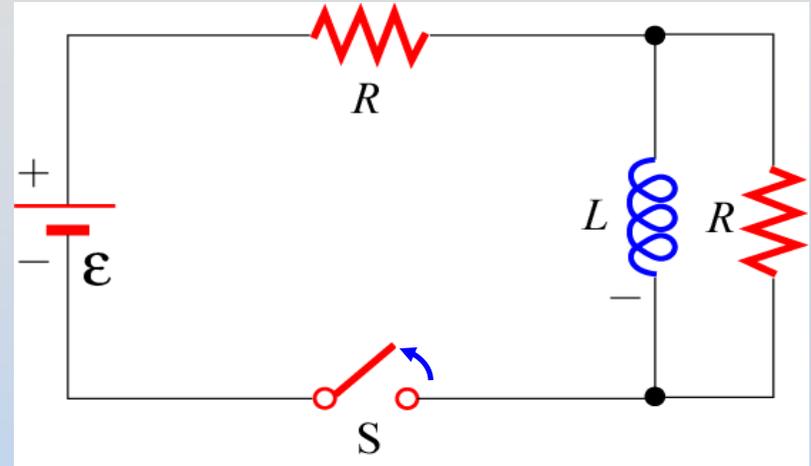1. B Increases so L does too
2. B Decreases so L does too
3. B Increases so L Decreases
4. B Decreases so L Increases
5. I don't know

Concept Q.: RL Circuit

In the circuit at right the switch S has been closed a very long time. At $t = 0$, the switch is opened. Taking downward current as positive, immediately after the switch is opened the current in the inductor is equal to



1. \mathcal{E}/R
2. $\mathcal{E}/2R$
3. $-\mathcal{E}/R$
4. $-\mathcal{E}/2R$
5. Zero
6. I don't know

MIT OpenCourseWare
<http://ocw.mit.edu>

8.02SC Physics II: Electricity and Magnetism
Fall 2010

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.