

# INDEX

- Absolute-value circuit, 458  
Active filters, 525  
All-pass transfer function, 530, 536  
Amplitude scaling, 513  
Amplitude stabilization, 487  
Analog computation, 502  
Analog multiplier, 501  
Analog-signal switching, 471  
Antilog circuit, 462  
Automatic gain control, 488  
Auxiliary equation, 115  
  
Band-gap voltage, 252  
Band-gap voltage reference, 288  
Bandpass amplifier, 135  
Bandwidth, 94  
Base-to-emitter voltage temperature coefficient, 252  
Base-width modulation, 310  
Base-width modulation factor, 313  
Block diagram, 22  
Bode plot, 85  
Bose oscillator, 502  
Butterworth filter, 508  
Butterworth transfer function, 80  
  frequency response of, 89  
  step response of, 83  
  
Bypass capacitors, 343  
  
CA3039 integrated circuit, 544  
Capacitive load, 169, 564, 597  
Capacitor selection, 448  
Cascode amplifier, current-source loaded, 320  
Characteristic equation, 44, 112  
Chopper stabilization, 522  
Closed-loop gain, 2  
Closed-loop zeros, 133  
Cofactor, 44  
Collector FET, 390  
Common-emitter amplifier, 33  
  current-source loaded, 315  
Common-mode input, 256  
Common-mode rejection ratio, 259, 434  
Compensating capacitor, 199  
Compensation, 165, 557  
  nonlinear, 240  
  series, 165  
Compensation that includes zero, 597  
Complementary Darlington connection, 292, 397  
Complementary emitter follower, 328  
Conditional stability, 234

- Convolution, 68  
Crossover distortion, 329  
Crossover frequency, 148  
Current repeater, 392  
Current source, 322, 452  
  
Darlington connection, 275  
Deadzone, 26  
Decibel, 84  
Decoupling capacitor, 171  
Demodulator, 474  
Describing function, 217  
table of, 223  
Desensitivity, 25  
Determinant, 44, 46  
Differential amplifier, 254, 397, 449  
Differential input, 256  
Differential output, 255  
Differentiator, 561  
Diode-connected transistor, 390  
Direct-coupled amplifiers, 249  
Divider, 211, 244  
Dominant pole, 78, 168  
Double integrator, 452  
Drift referred to the input, 250  
from resistor mismatches, 266  
from transistor mismatches, 262,  
268  
Duty-cycle modulation, 500  
  
Electronic switch, 518  
Emitter follower, 326, 327  
Error coefficients, 97  
Estimating open-loop gain, 65  
Exponentiating circuit, 547  
  
Feedback compensation, 196  
Feedback-network compensation, 563  
Feedforward, 304, 421, 630  
FET preamplifier, 424  
Field-effect transistor, 323, 471, 491  
  
Final-value theorem, 69  
First-order system, 78  
frequency response of, 86  
step response of, 79  
Fourier series, 218  
Frequency modulation, 502  
Frequency response, 81  
Function generator, 234, 428, 497,  
540  
  
Gain adjustment, 165  
Gain margin, 147  
Gain-phase plot, 88  
Gated operational amplifier, 472  
Gaussian pulse, 104  
Goldberg amplifier, 522  
Grounding problems, 446  
Gyrator, 456  
  
High-gain stages, 309  
Howland current source, 454, 549  
Hybrid-pi model, 310  
Hysteresis, 220, 234  
  
Impedance scaling, 46  
Initial-value theorem, 68  
Inner loop, 197  
Input bias current, 434  
Input common-mode range, 434  
Input compensation, 558  
Input current, 269  
Input-current cancellation, 271  
Input-current measurement, 438  
Input differential range, 434  
Input offset current, 434  
Input offset voltage, 434  
Integrator, 11  
Inverting amplifier, 4  
Inverted-transistor connection, 472  
  
Jump resonance, 642

- Lag network, 173, 179  
Lag transfer function, 558  
Laplace transforms, 67  
  properties of, 68  
  table of, 70  
Lateral-PNP transistor, 386  
Lead network, 172, 178  
Lead transfer function, 558  
Leakage current, 268  
Limit cycle, 217, 510  
Limiter, 232  
Linearization, 209  
LM101 operational amplifier, 401  
LM101A operational amplifier, 63, 206, 406  
LM108 operational amplifier, 415  
LM110 operational amplifier, 416  
LM118 operational amplifier, 421  
LM121, 425  
Load capacitor, 169, 564, 597  
Load regulation, 169  
Log circuit, 12, 18, 462, 568  
Loop, 44  
Loop transmission, 6, 24  
Low-current operation, 270
- Magnetic suspension, 214  
Major loop, 197  
MC1533 operational amplifier, 374  
MC1538R, 425  
MC1539 operational amplifier, 375  
 $\mu$ A702 operational amplifier, 421  
 $\mu$ A715 operational amplifier, 421  
 $\mu$ A726, 422  
 $\mu$ A727, 422  
 $\mu$ A733, 374  
 $\mu$ A740 operational amplifier, 424  
 $\mu$ A741 operational amplifier, 375  
 $\mu$ A776 operational amplifier, 410  
Miller effect, 300, 354  
Minor loop, 197
- Minor-loop compensation, 573  
Minor-loop instability, 600  
Modulator, 474  
MOS capacitor, 391  
Multiplexer, 473  
Multiplier, 211, 468
- Negative feedback, 24  
Negative impedance converter, 455  
Nichols chart, 150  
Node equations, 33  
Noninverting amplifier, 4  
Nonlinear oscillators, 496  
Nyquist criterion, 139
- Offset voltage, 251, 472  
Offset-voltage measurement, 438  
One-pole compensation, 575  
One-stage amplifier, 417  
Open-loop gain, 3  
  measurement of, 440  
Open-loop transfer function, 3  
  estimation of, 65  
Operational-amplifier specifications, 433  
Output amplifiers, 327  
Output impedance, 36  
Output resistance, 49, 169  
Output stages, 425  
Output voltage range, 434
- Padé approximate, 530  
Path, 44  
Peak detector, 459  
Phase detector, 537  
Phase margin, 147  
Phase plane, 511  
Phase-shift oscillator, 116, 231  
Phase shifter, 536  
Piecewise-linear circuit, 461  
Piecewise-linear network, 540

- Pinched resistor, 389  
Positive feedback, 9, 497  
Power amplifier, 202  
Power ground, 447  
Power-supply decoupling, 444  
Precision rectifier, 457  
Pulse signal, 71, 72
- Quadrature oscillator, 486, 519  
Quarter-square multiplier, 468
- Ramp error, 101  
Rejection amplifier, 134  
Resistor selection, 447  
Resolver, 243, 537  
Right-half-plane singularities, 130, 143  
Rise time, 92  
Root contours, 136  
Root-locus construction rules, 121  
Root-locus diagram, 119  
Routh criterion, 112
- Sallen and Key circuit, 525  
Sample-and-hold circuit, 103, 475, 519, 650  
Saturating nonlinearity, 219  
Schmitt trigger, 234, 497  
Second-order system, 79, 119  
    frequency response of, 87  
    step response of, 81  
Second-stage drift contributions, 279  
Settling time, 94  
    with lag compensation, 193  
709 operational amplifier, 305  
Signal-flow graph, 44  
Signal ground, 447  
Sine-wave shaping circuit, 540  
Single-ended output, 255  
Sinusoidal oscillators, 485  
Six-mask process, 383
- Slew rate, 364, 371, 435, 633  
Slew-rate measurement, 440  
Slow-rolloff compensation, 604  
Soft saturation, 224  
Speed regulator, 203  
Split collector transistor, 387, 393  
Square-rooting circuit, 244  
Stable-amplitude oscillation, 231  
Stability, defined, 109  
Step response, 187  
Substrate PNP transistor, 387  
Summing amplifier, 10  
Summation point, 22  
Super- $\beta$  transistor, 385, 415  
Superdiode, 457  
Supply-voltage-rejection ratio, 434  
    measurement of, 439  
Supply-voltage sensitivity, 434
- Tangent approximation, 210  
Taylor's series, 210  
Thermal protection, 422  
Thermal runaway, 330, 339  
Three-stage amplifier, 296  
Three-mode integrator, 516  
Time delay, 192, 530  
Time-division multiplier, 501  
Time scaling, 513  
Tracking filter, 538  
Transconductance multiplier, 468  
Transient response, 76  
Two-pole compensation, 586  
Two-port network, 359  
Two-stage amplifier, 198, 305  
    compensation of, 356
- Unity-gain frequency, 148
- Van der Pol's equation, 510  
Vertical-PNP transistor, 387  
Voltage reference, 286, 519, 553

Voltage regulator, 169, 292

Zener diode, 227

Wien-bridge oscillator, 485

RES.6-010 Electronic Feedback Systems  
Spring 2013

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.