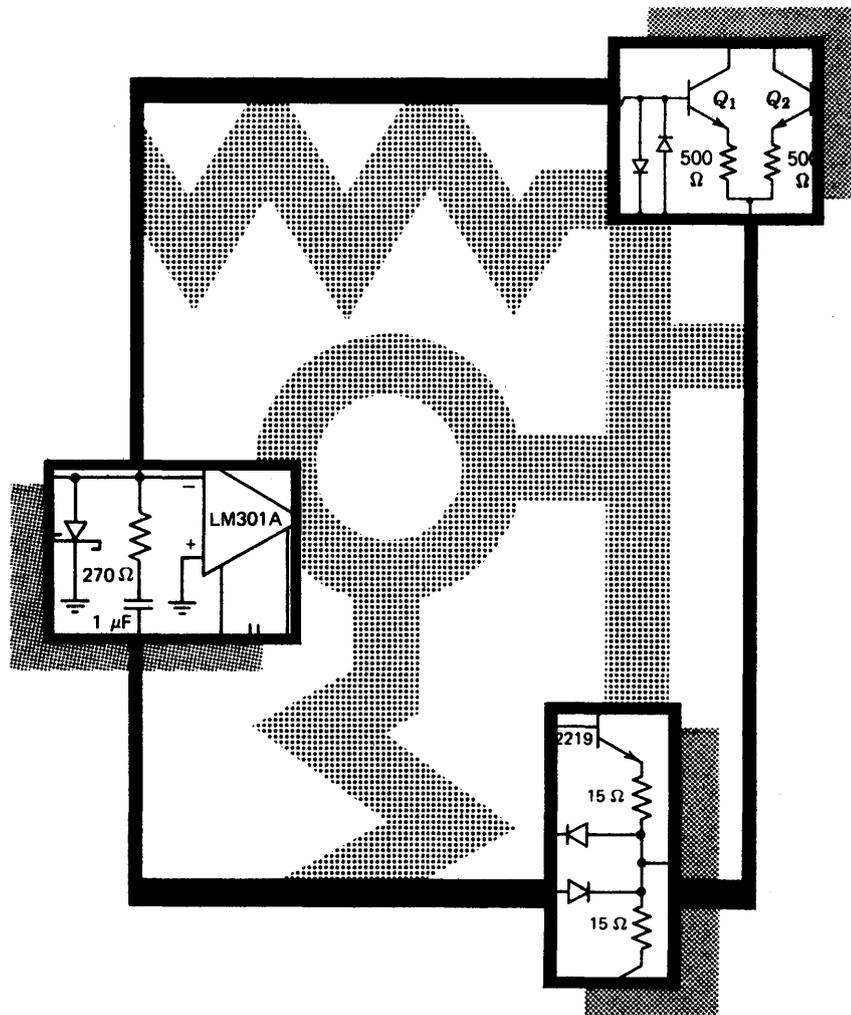


Feedback Compensation of an Operational Amplifier

12



Blackboard 12.1


Op-Amp Example
 Practical Considerations
 101A (or 301A)

Problems above ~1MHz
 $\frac{g_m}{2} \approx 2 \times 10^{-9}$ mho

Minor loop stability
 with $C_c = 30$ pF

$$\frac{g_m}{2C_c S} = \frac{2 \times 10^{-9}}{3 \times 10^{-11} S} = \frac{67 \times 10^6}{S}$$

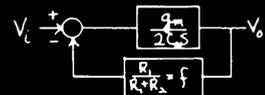
$$\frac{g_m}{2C_c \omega} = 1 @ \omega = 6.7 \times 10^6 \text{ r/s} \approx 1 \text{ MHz}$$



$$A \approx \frac{\frac{g_m}{2C_c S}}{1 + \frac{g_m R}{2C_c S}}$$


$$= \frac{1}{f} \frac{1}{\frac{2C_c S}{f} + 1}$$

Two-pole:

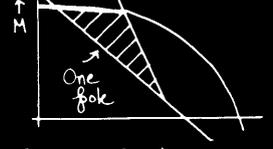

$$\frac{g_m}{2C_c S} = \frac{K(S+1)}{S^2}$$
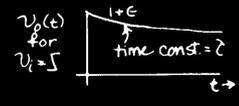
$$\frac{V_o}{V_i} = \frac{(1+\epsilon)S+1}{S+1}$$




12-1

Blackboard 12.2


$A_0 = \frac{1}{f}$	$t_r, 20\text{pF}$	$t_r, \text{"optimum"} C_c$
1	150 ns	
10	15 μ s	250 ns
100	15 μ s	500 ns
1000	150 μ s	1 μ s

12-2


Viewgraph 12.1

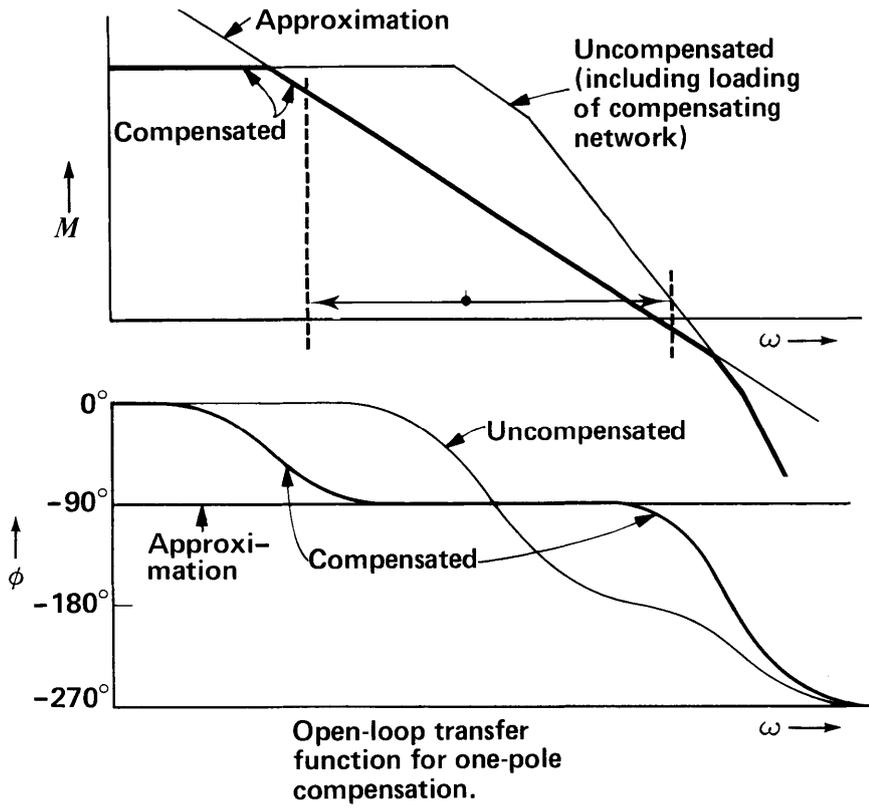


Viewgraph 12.2

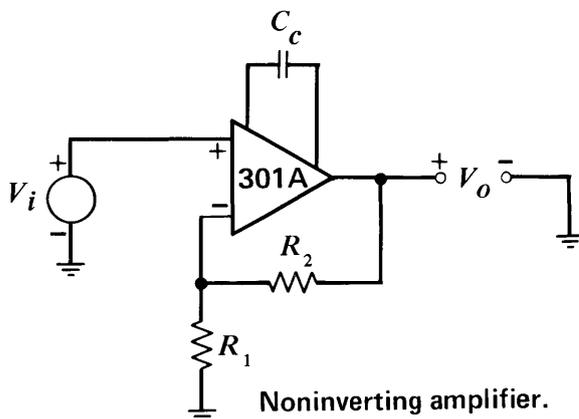


Viewgraph 12.3

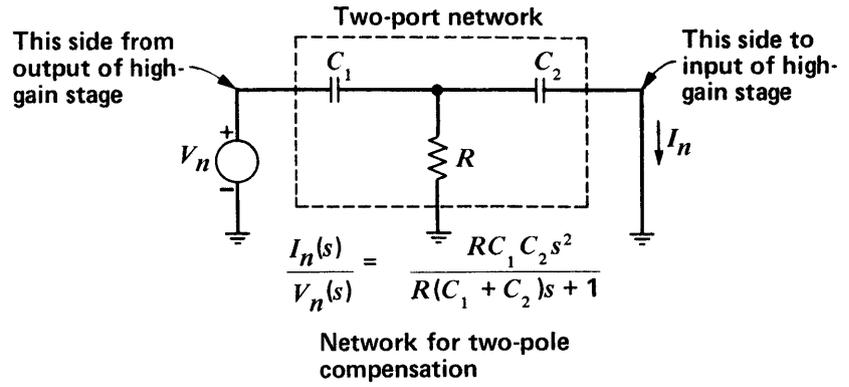

Viewgraph 12.4

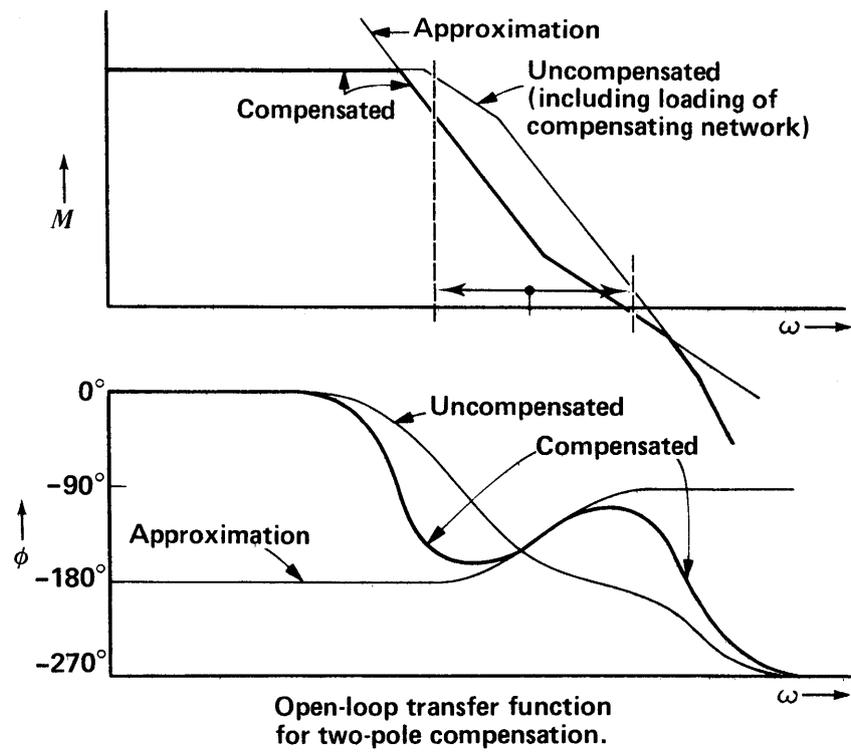


Viewgraph 12.5

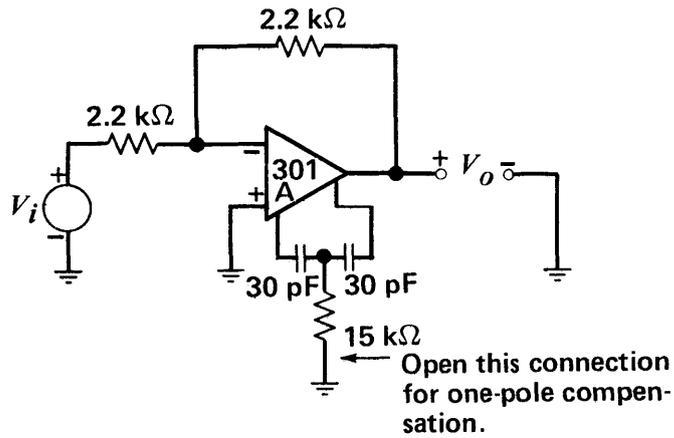


Unity-gain inverter with two-pole compensation.


Viewgraph 12.6

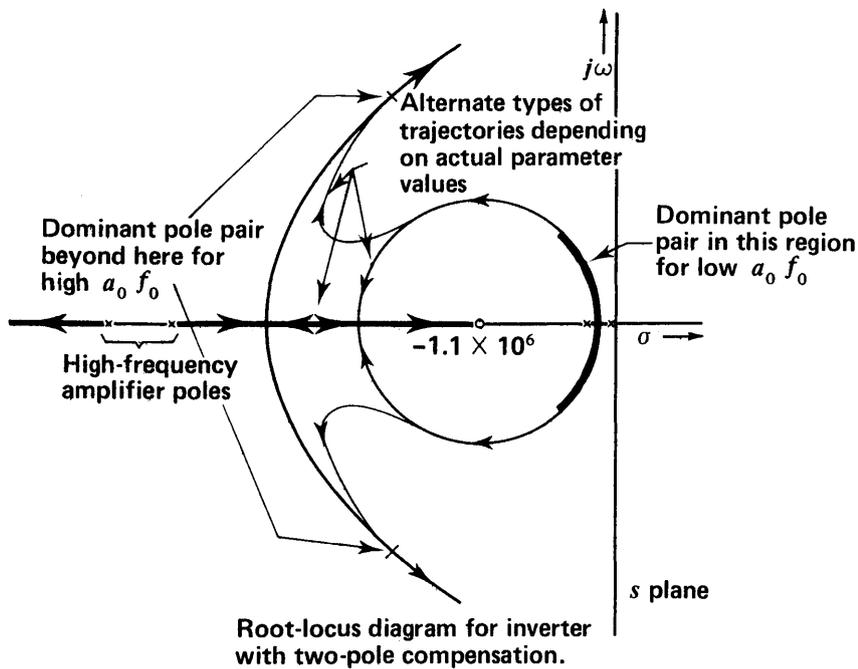

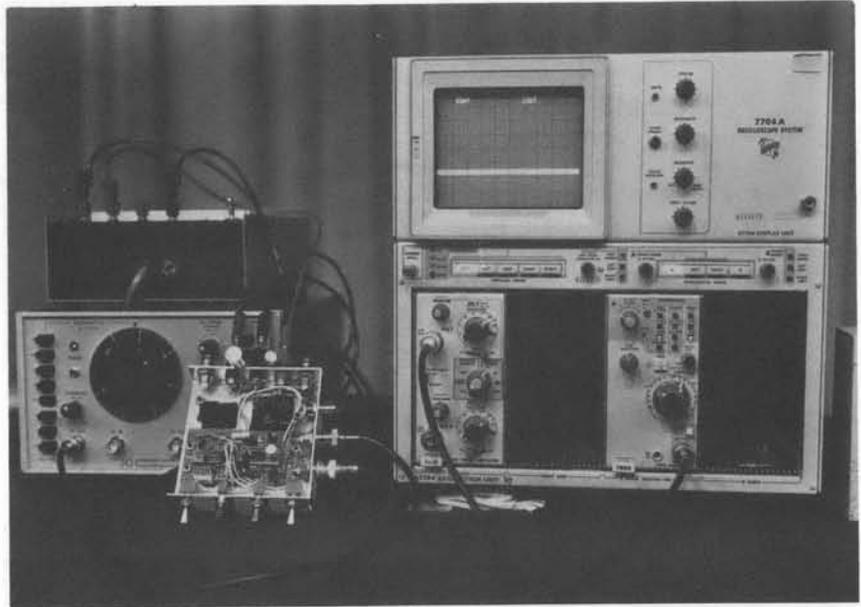Demonstration Photograph
12.1 Operational-amplifier compensation demonstration



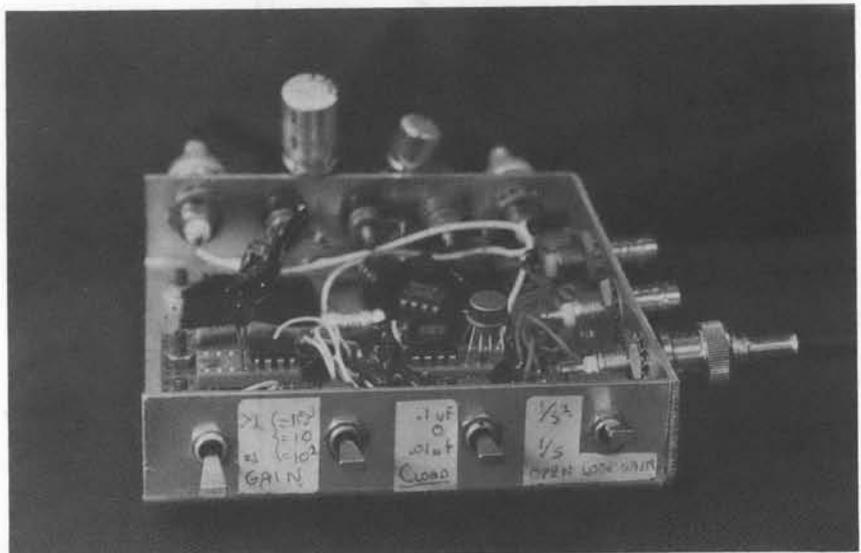Demonstration Photograph
12.2 Close-up of operational-amplifier for compensation circuit



In this session we show how minor-loop compensation is used to control the dynamics of an available integrated-circuit operational amplifier. We find that in certain applications, dramatic performance improvements are possible compared with a similar amplifier that uses fixed compensation that is selected for unity-gain stability.

Comments

While specific values for the compensating components are selected based on parameters of the amplifier type used, the general methods are applicable to any amplifier that allows the choice of the components used for minor-loop compensation.

In about the middle of the first blackboard I give the expression for the closed-loop gain as:

Correction

$$A \simeq \frac{\frac{g_m}{2C_c s}}{1 + \frac{g_m f}{2C_c s}} = \frac{1}{f} \frac{1}{\frac{2C_c s}{g_m f} + 1}$$

The final expression should read:

$$\frac{1}{f} \frac{1}{\frac{2C_c s}{g_m f} + 1}$$

(There is a g_m missing in the equation on the blackboard.)

Textbook: Sections 13.3.2 and 13.3.3.

Reading

Problems

Problem 12.1 (P13.5)

Problem 12.2 (P13.6)

Problem 12.3 (P13.7)

Problem 12.4 (P13.8)

MIT OpenCourseWare
<http://ocw.mit.edu>

RES.6-010 Electronic Feedback Systems
Spring 2013

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.