
The Thermal Domain II

Joel Voldman*

Massachusetts Institute of Technology

***(with thanks to SDS)**

Outline

- > **Review**
- > **Lumped-element modeling: self-heating of resistor**
- > **Analyzing problems in space and 1/space**
 - **The DC Steady State – the Poisson equation**
 - » **Finite-difference methods**
 - » **Eigenfunction methods**
 - **Transient Response**
 - » **Finite-difference methods**
 - » **Eigenfunction methods**
- > **Thermoelectricity**

The generalized heat-flow equation

> Last time we generated
a general conservation
equation

> Include a flux that
depends on a “force”
gradient

> And a “capacity”
relation

$$\frac{\partial b}{\partial t} = -\nabla \cdot \mathbf{F} + G$$

$$\frac{d\tilde{Q}}{dt} + \nabla \cdot \mathbf{J}_Q = \tilde{P} \Big|_{sources}$$

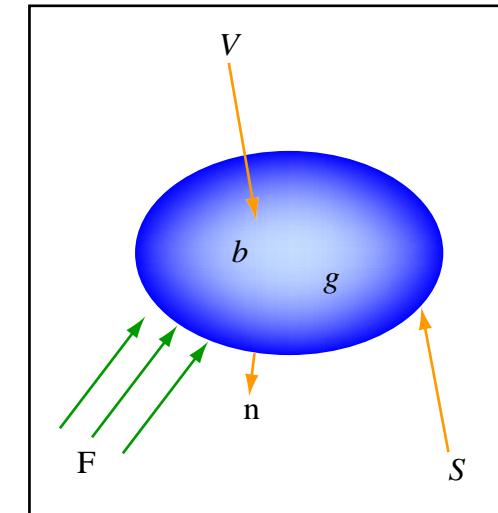


Image by MIT OpenCourseWare.

$$\mathbf{J}_Q = -\kappa \nabla T$$

$$\frac{\partial \tilde{Q}}{\partial T} = \tilde{C}$$

The generalized heat-flow equation

> We get a generalized conduction equation

- Assume homogeneous region

> Applies to

- Heat flow
- Mass transport (diffusion)
- Squeezed-film damping

> Provides a rich set of solution methods

$$\tilde{C} \frac{\partial T}{\partial t} - \kappa \nabla^2 T = \tilde{P} \Big|_{sources}$$

$$\frac{\partial T}{\partial t} - D \nabla^2 T = \frac{1}{\tilde{C}} \tilde{P} \Big|_{sources}$$


$$[m^2/s] \quad D = \frac{\kappa}{\tilde{C}} \quad [W/m-K] \\ [J/K-m^3]$$

Thermal diffusivity

Thermal domain lumped elements


> Thermal resistor

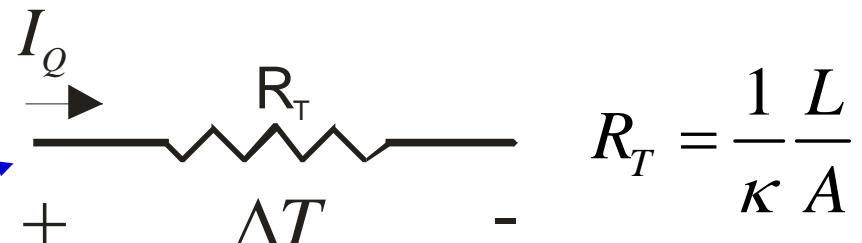- Resistance to heat flow
- Three types
 - » Conduction
 - » Convection
 - » Radiation




> Thermal capacitor

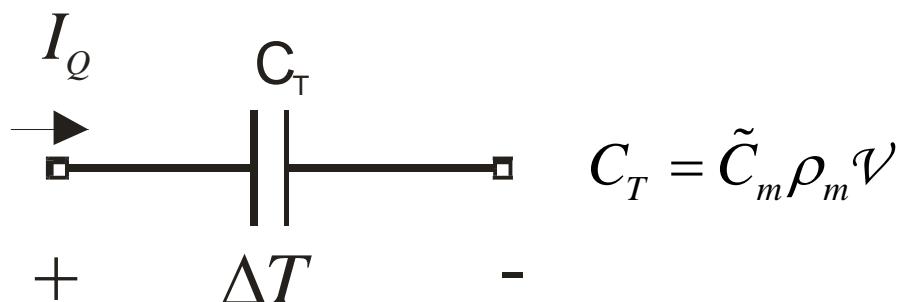- Store thermal energy
- Specific heat \times volume \times density



> Electrothermal transducer

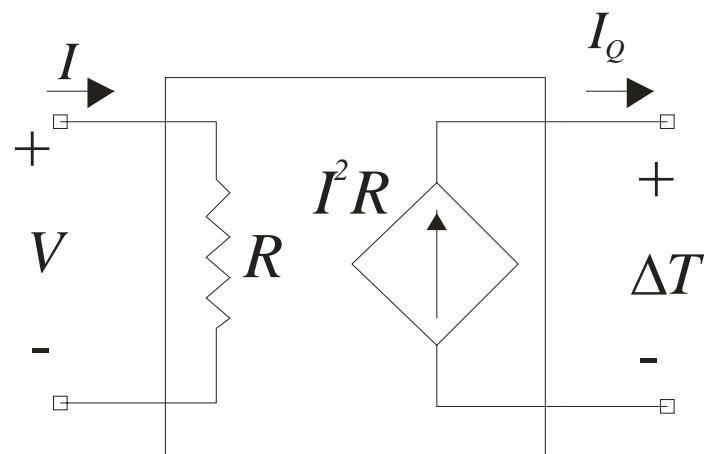- Converts electrical dissipation into heat current



Outline

- > Review
- > Lumped-element modeling: self-heating of resistor
- > Analyzing problems in space and 1/space
 - The DC Steady State – the Poisson equation
 - » Finite-difference methods
 - » Eigenfunction methods
 - Transient Response
 - » Finite-difference methods
 - » Eigenfunction methods
- > Thermoelectricity

Measuring temperature with the bolometer

- > So far, we know how to convert an input heat flux into a temp change
- > How do we convert that temp change back into the electrical domain?


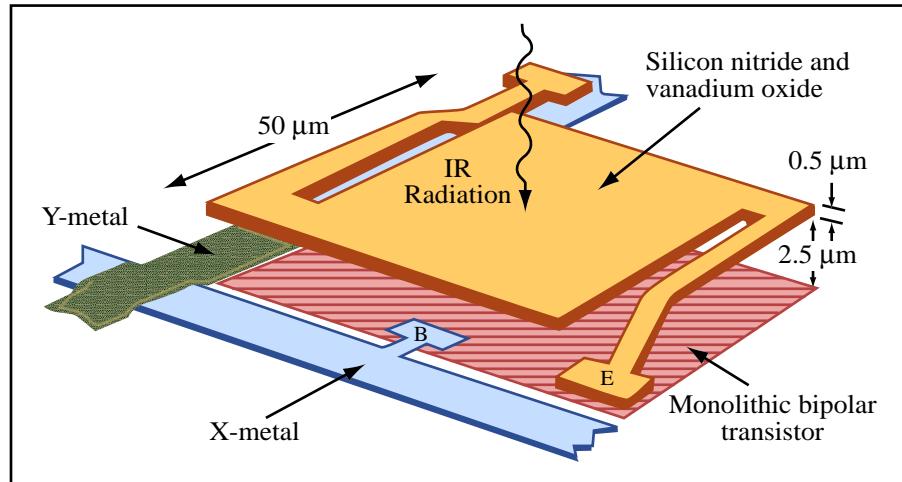


Image by MIT OpenCourseWare.

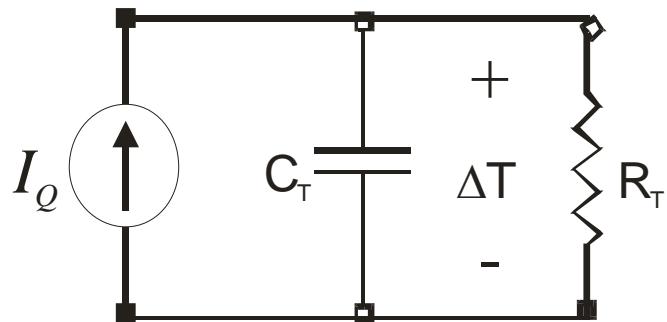

$$\Delta T = I_Q \left(R_T // \frac{1}{C_T s} \right) = \frac{R_T I_Q}{1 + R_T C_T s}$$

$$\Delta T_{ss} = R_T I_Q$$

$$\tau = R_T C_T$$

TCR

- > Resistance changes with temperature (TCR)
 - Beware, TCR is not constant!
- > We can use resistor as a hotplate or a temperature sensor

$$R(T) = R_0 [1 + \alpha_R (T - T_0)]$$

$$\Delta R = \frac{R - R_0}{R_0} = \alpha_R \Delta T$$

metal	resistivity [Ωcm]	TCR [$10^{-4}/\text{K}$]
Pt	10.6e-6	39.2
Nichrome	101e-6	1.7
Ni	6.84e-6	68.1
Al	2.83e-6	38
Au	2.4e-6	40
Cr	1.26e-5	30
Ti	3.84e-5	38
W	4.9e-6	45
Cu	1.72e-6	41
Fe	9.71e-6	65.1
poly-Si	10.6e-6	-12 to 12

V_2O_5


-200

Coupling back into the electrical domain

> We can define a transducer that uses TCR to convert back into electrical domain

> In order to *measure* electrical R, we need to introduce a voltage & current


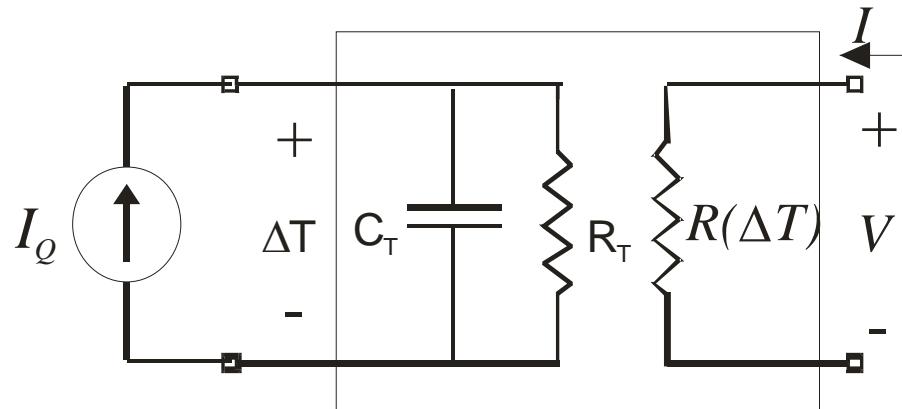
> This current will couple back and induce its own ΔT




$$R(\Delta T) = R_0 (1 + \alpha_R \Delta T)$$

Thermo – electrical coupling

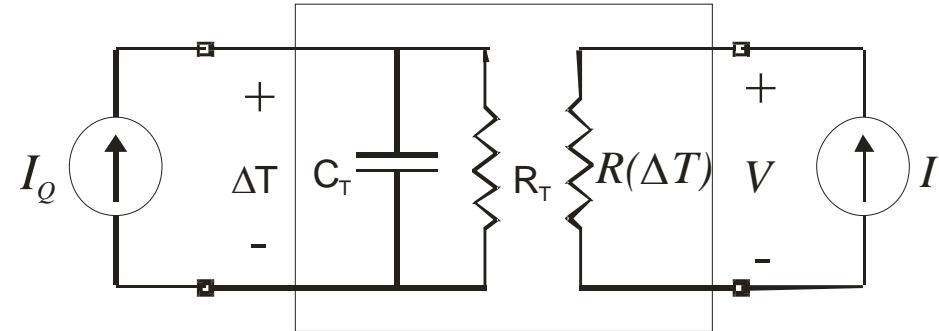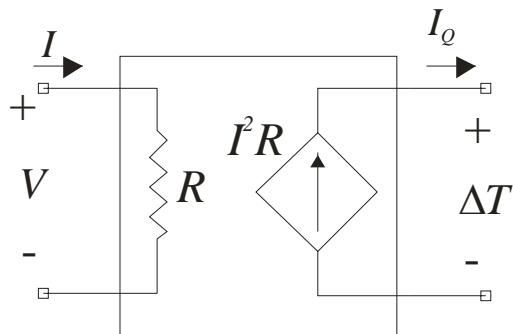- > This is our prior electrothermal transducer



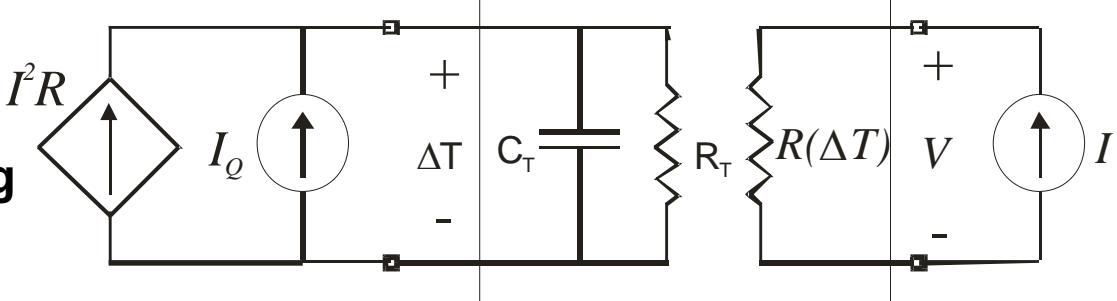- > We can add in the current source due to Joule heating
- > The current source is dependent on R , which is dependent on ΔT , and so on
- > What we will want is for $I_Q \gg I^2R$




Example: Self-heating of a resistor

> First, assume input $I_Q=0$

> Now, electrical port is input, temp change is output
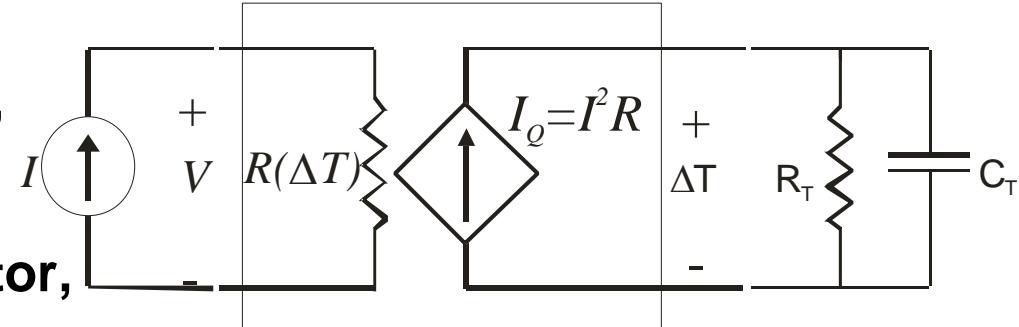
> Two ways to drive the resistor, current source or voltage source – it sometimes matters



Current-source drive

$$\frac{\Delta T}{I_Q} = \frac{R_T}{1 + R_T C_T s}$$

Expand out
into D.E.

$$\Delta T(1 + R_T C_T s) = I_Q R_T$$

$$\Delta T + \frac{d\Delta T}{dt} R_T C_T = I^2 R_0 (1 + \alpha_R \Delta T) R_T$$

$$\Delta T + \frac{d\Delta T}{dt} R_T C_T = I_Q R_T$$

$$I_Q = I^2 R = I^2 R_0 (1 + \alpha_R \Delta T)$$

Plug in for
 I_Q

Example: Self-heating of a resistor

> First-order system with feedback results

$$\frac{d\Delta T}{dt} R_T C_T = -\Delta T (1 - I^2 R_0 \alpha_R R_T) + I^2 R_0 R_T$$

Collect terms
and rearrange

$$\frac{d\Delta T}{dt} + \Delta T \frac{(1 - I^2 R_0 \alpha_R R_T)}{R_T C_T} = \frac{I^2 R_0}{C_T}$$

Recognize
D.E. form

$$\frac{dy}{dt} + ay = b$$

Pick out quantities
of interest

$$\tau_I = \frac{R_T C_T}{(1 - I^2 R_0 \alpha_R R_T)}$$

$$\Delta T_{ss,I} = \frac{\frac{I^2 R_0}{C_T}}{\frac{(1 - I^2 R_0 \alpha_R R_T)}{R_T C_T}} = \frac{R_0 R_T I^2}{1 - \alpha_R R_0 R_T I^2}$$

This blows up when

$$I^2 = \frac{1}{\alpha_R R_0 R_T}$$

For $\alpha_R > 0$

Example: Self-heating of a resistor

> What changes for voltage-drive?

$$\frac{\Delta T}{I_Q} = \frac{R_T}{1 + R_T C_T s}$$

$$\Delta T(1 + R_T C_T s) = I_Q R_T$$


$$\Delta T + \frac{d\Delta T}{dt} R_T C_T = I_Q R_T$$

$$I_Q = \frac{V^2}{R} = \frac{V^2}{R_0(1 + \alpha_R \Delta T)}$$

$$I_Q \approx \frac{V^2}{R_0} (1 - \alpha_R \Delta T)$$



Same
T.F.

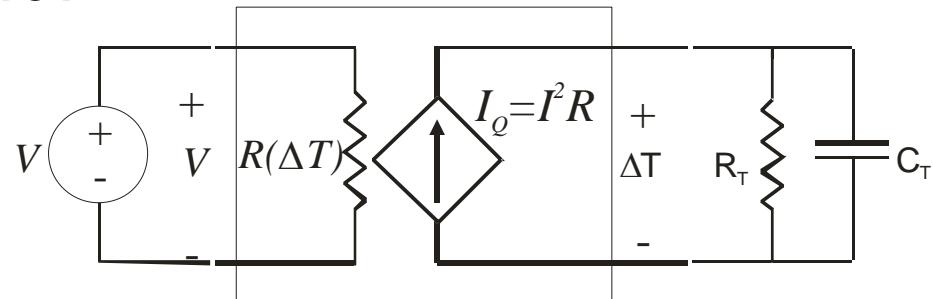

I_Q is now
different



This leads to
negative feedback
for $\alpha_R > 0$

Voltage-source drive

$$\Delta T_{SS,V} = \frac{R_T V^2 / R_0}{1 + \alpha_R R_T V^2 / R_0}$$

Results of modeling

- > A positive TCR resistor driven from a current source can go unstable – fuse effect
- > When dealing with the electrostatic actuator, we observed that very different behavior was found depending on whether the system was voltage-driven or current-driven
- > Here we see that, depending on the way the electrical domain couples to the thermal energy domain, it is also important to look at the drive conditions of a system.

Back to the bolometer

> Assume we want to measure $I_Q=1 \text{ nW}$ with 1% accuracy

$$\Delta T_{SS,I} = \frac{R_0 R_T I^2}{1 - \alpha_R R_0 R_T I^2} \approx R_0 R_T I^2$$

> This limits current one can use for measurement

$$\Delta T_{SS,V} = \frac{R_T V^2 / R_0}{1 + \alpha_R R_T V^2 / R_0} \approx R_T V^2 / R_0$$

> For Honeywell bolometer,
 $R_0 \sim 50 \text{ k}\Omega$, $\alpha_R \sim -2\%/\text{K}$, $R_T \sim 10^7 \text{ K/W}$

$$\Delta R_{meas} = \alpha_R R_T \frac{V^2}{R_0}$$

> Input signal will create $\Delta T = 10 \text{ mK}$

$$\Delta R_{signal} = \alpha_R R_T I_Q$$

> This produces $\Delta R_{signal} = 2 \times 10^{-4}$, or a 10Ω resistance change

$$\Delta R_{meas} = \alpha_R R_T \frac{V^2}{R_0} \leq 0.01 \alpha_R R_T I_Q$$

> Voltage must be $< 0.7 \text{ mV}$

$$V \leq \sqrt{\frac{I_Q R_0}{100}}$$

Outline

- > Review
- > Lumped-element modeling: self-heating of resistor
- > Analyzing problems in space and 1/space
 - The DC Steady State – the Poisson equation
 - » Finite-difference methods
 - » Eigenfunction methods
 - Transient Response
 - » Finite-difference methods
 - » Eigenfunction methods
- > Thermoelectricity

Space and reciprocal space

- > We have thus far focused on “big” lumped-element modeling to design and analyze systems
- > This isn’t the *only* way to proceed
- > We can chop up the model into many small “lumped elements → discretize in space
- > Or we can approximate the answer using series methods → discretize in reciprocal space

DC Steady State

> The Poisson Equation

$$\frac{\partial T}{\partial t} - D\nabla^2 T = \frac{1}{\tilde{C}} \tilde{P} \Big|_{sources}$$

> Boundary conditions

- Dirichlet – sets value on boundary

Fixes $T(r) \Big|_{boundary}$

- Neumann – sets slope on boundary → Flux

Fixes $\frac{dT}{dn} \Big|_{boundary}$

- Mixed – sets some function of value and slope

> The Poisson Equation is linear


- Can use superposition methods

 At steady state


$$D\nabla^2 T = -\frac{1}{\tilde{C}} \tilde{P} \Big|_{sources}$$

Finite-Difference Solution

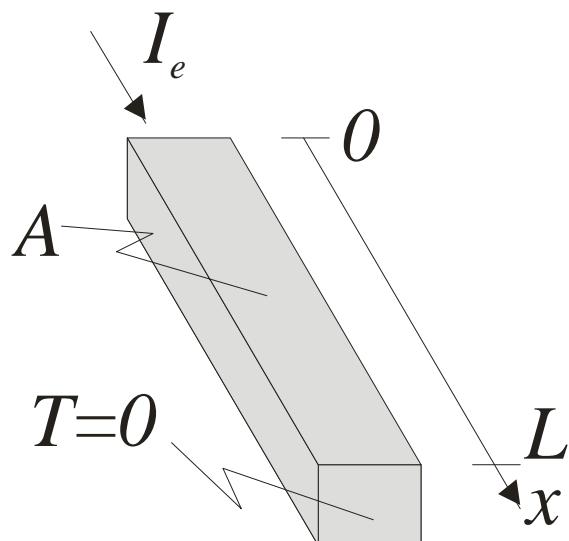- > We can generate an equivalent circuit by discretizing the equation in space
- > A numerical algorithm with a circuit equivalent
- > In 1-D, divide bar into N segments and N+1 nodes



$$D\nabla^2 T = -\frac{1}{\tilde{C}} \tilde{P} \Big|_{sources}$$
$$D \frac{d^2 T}{dx^2} = -\frac{1}{\tilde{C}} \tilde{P} \Big|_{sources}$$
$$\left. \frac{d^2 T}{dx^2} \right|_{x_n} \cong \frac{T(x_n + h) + T(x_n - h) - 2T(x_n)}{h^2}$$

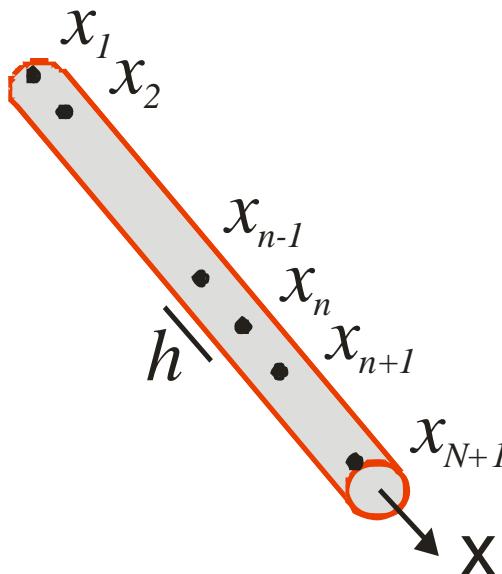

Equivalent Circuit

- > Can create an equivalent circuit for this equation

$$\frac{T(x_n + h) + T(x_n - h) - 2T(x_n)}{h^2} = -\frac{\tilde{P}(x_n)}{\kappa}$$

$$(T_{n+1} - T_n) + (T_{n-1} - T_n) = -h^2 \frac{\tilde{P}(x_n)}{\kappa}$$

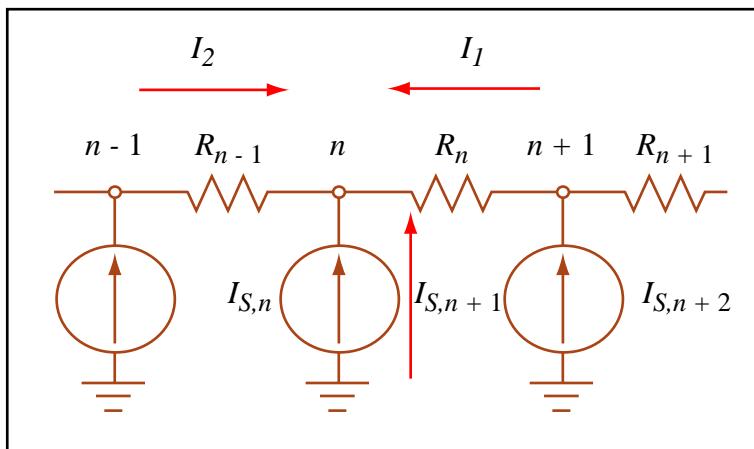


Image by MIT OpenCourseWare.

Adapted from Figure 12.1 in Senturia, Stephen D. *Microsystem Design*. Boston, MA: Kluwer Academic Publishers, 2001, p. 302. ISBN: 9780792372462.

$$I_{S,n} = (hA)\tilde{P}(x_n)$$



$$(T_{n+1} - T_n) + (T_{n-1} - T_n) = -h \frac{I_{S,n}}{A\kappa}$$


$$\frac{(T_{n+1} - T_n)}{R_n} + \frac{(T_{n-1} - T_n)}{R_{n-1}} + I_{S,n} = 0$$

This is KCL at a node

Define local resistance $R_n = R_{n-1} = \frac{1}{\kappa A} h$

Equivalent Circuit
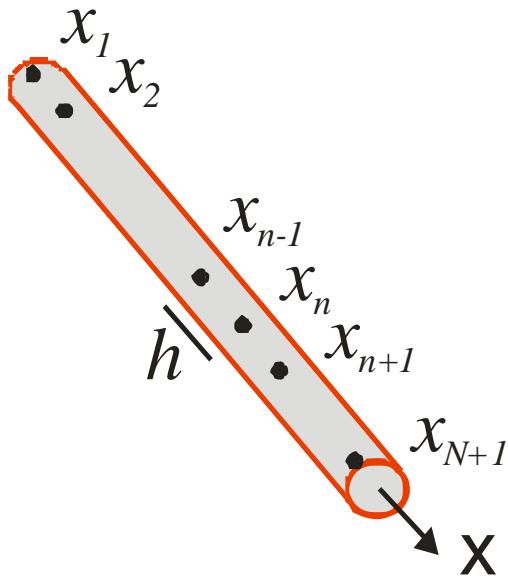
> Let's apply this to 1-D
self-heated resistor



At node N:

$$G_n = I/R_n \quad \frac{(T_{n+1} - T_n)}{R_n} + \frac{(T_{n-1} - T_n)}{R_{n-1}} = -I_{S,n}$$
$$G_n = G_{n+1} \quad G_n(T_{n+1} - T_n) + G_{n-1}(T_{n-1} - T_n) = -I_{S,n}$$
$$-GT_{n+1} + 2GT_n - GT_{n-1} = I_{S,n}$$

Example: Self-heated resistor

- > Set up conductance

matrix

- > Solve

- > Very appropriate for MATLAB

- > Can even generate the conductance matrix with MATLAB scripts

- > At edges, impose B.C's

$$\begin{bmatrix} 1 & 0 & 0 & \dots & 0 \\ -G & 2G & -G & \dots & 0 \\ 0 & -G & 2G & \ddots & 0 \\ \vdots & \ddots & \ddots & \ddots & \vdots \\ 0 & & \ddots & 2G & -G & 0 \\ 0 & & & \ddots & -G & 2G & -G & \ddots & 0 \\ 0 & & & 0 & -G & 2G & \ddots & & 0 \\ \vdots & & & & \ddots & \ddots & \ddots & & \vdots \\ 0 & & & & & \ddots & 2G & -G & 0 \\ 0 & & & & & & \ddots & -G & 2G & -G \\ 0 & & & & & & \dots & 0 & 0 & 1 \end{bmatrix} \begin{pmatrix} T_1 \\ T_2 \\ T_3 \\ \vdots \\ T_{n-1} \\ T_n \\ T_{n+1} \\ \vdots \\ T_{N-1} \\ T_N \\ T_{N+1} \end{pmatrix} = hAP_o$$

$$GT = P$$

Eigenfunction Solution

- > This is a standard method for solving linear partial differential equations
- > It leads to what amount to series expansion solutions, discretized in *reciprocal space*
- > Typically problems converge with only a few terms – THIS IS WHY IT IS USEFUL

$$\nabla^2 T = -\frac{\tilde{P}(x)}{K}$$

Eigenfunctions of ∇^2 : $\frac{d^2 \psi_i}{dx^2} = \lambda_i \psi_i$

Can use any linear combination of $e^{\pm jkx}$, including $\sin(kx)$ and $\cos(kx)$

Values of k are determined by the boundary conditions

Eigenfunctions can be made orthonormal

$$\int \psi_j^* \psi_i dx = \delta_{ij}$$

Eigenfunction Expansion

Assume:


$$T(x) = \sum_{n=1}^{\infty} A_n \psi_n(x)$$

**Eigenfunctions
for this problem:**

$$\psi_n(x) = c_n \sin(k_n x)$$

Apply BC at $x=0, L$:
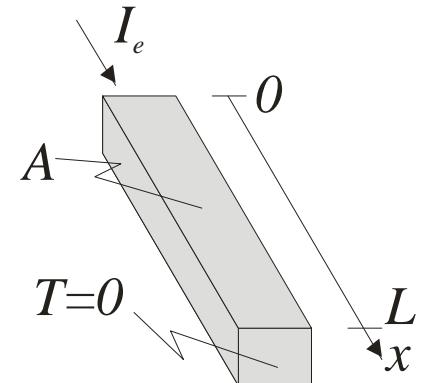
$$\sin(k_n L) = 0 \Rightarrow k_n = \frac{n\pi}{L} \quad \text{for } n = 1, 2, 3, \dots$$



Normalize:

$$1 = \int_0^L \psi_n^2(x) dx = \int_0^L c_n^2 \sin^2(k_n x) dx \Rightarrow \sqrt{\frac{2}{L}} \sin(k_n x)$$

Plug into DE:

$$\frac{d^2 T}{dx^2} = -\frac{\tilde{P}(x)}{\kappa}$$

$$\sum_1^{\infty} k_n^2 A_n \psi_n(x) = \frac{\tilde{P}(x)}{\kappa}$$

Eigenfunction Expansion

$$\sum_1^{\infty} k_n^2 A_n \psi_n(x) = \frac{\tilde{P}(x)}{K}$$

**Multiply by
orthogonal
eigenfunction and
integrate:**

$$\sum_1^{\infty} \int_0^L k_n^2 A_n \psi_n(x) \psi_m(x) dx = \int_0^L \frac{\tilde{P}(x)}{K} \psi_m(x) dx$$

$$k_m^2 A_m = \frac{1}{K} \int_0^L \sqrt{\frac{2}{L}} \sin\left(\frac{m\pi x}{L}\right) \tilde{P}(x) dx$$

$$A_m = \frac{1}{k_m^2 K} \sqrt{\frac{2}{L}} \int_0^L \sin\left(\frac{m\pi x}{L}\right) \tilde{P}(x) dx$$

Eigenfunction Expansion

For uniform power density:

$$A_m = \frac{\tilde{P}_0}{k_m^2 K} \sqrt{\frac{2}{L}} \int_0^L \sin\left(\frac{m\pi x}{L}\right) dx$$

$$A_n = \frac{\tilde{P}_0}{k_n^3 K} \sqrt{\frac{2}{L}} \left(1 - (-1)^n\right)$$

$$T(x) = \sum_{n=1}^{\infty} A_n \psi_n(x)$$

$$T(x) = \sum_{n=1}^{\infty} \frac{\tilde{P}_0}{k_n^3 K} \sqrt{\frac{2}{L}} \left(1 - (-1)^n\right) \sqrt{\frac{2}{L}} \sin\left(\frac{n\pi x}{L}\right)$$

$$T(x) = \frac{4L^2 \tilde{P}_0}{\pi^3 K} \sum_{n \text{ odd}} \frac{1}{n^3} \sin\left(\frac{n\pi x}{L}\right)$$

The Details

Final answer: $T(x) = \frac{4\tilde{P}_o L^2}{\kappa\pi^3} \sum_{n \text{ odd}} \frac{\sin(n\pi x/L)}{n^3}$

Power density: $\tilde{P}_o = \frac{I_e^2 R}{volume} = \frac{I_e^2}{\sigma_e A^2}$

At $x=L/2$: $T_{\max} = \left(\frac{4}{\pi^3}\right) \frac{I_e^2 L^2}{\sigma_e \kappa A^2} \left[1 - \frac{1}{3^3} + \frac{1}{5^3} + \dots \right]$

Even if we consider only the first term in the expansion, we find

$$T_{\max} = \left(\frac{1}{7.75}\right) \frac{I_e^2 L^2}{\sigma_e \kappa A^2} \quad \text{compared to the exact solution of } \left(\frac{1}{8}\right) \frac{I_e^2 L^2}{\sigma_e \kappa A^2}$$

Outline

- > Review
- > Lumped-element modeling: self-heating of resistor
- > Analyzing problems in space and 1/space
 - The DC Steady State – the Poisson equation
 - » Finite-difference methods
 - » Eigenfunction methods
 - Transient Response
 - » Finite-difference methods
 - » Eigenfunction methods
- > Thermoelectricity

Transient Modeling

> Finite-difference method

- Simply add a thermal capacitance to ground at each node of the finite-difference network. These circuits can be analyzed with SPICE or other circuit simulators.

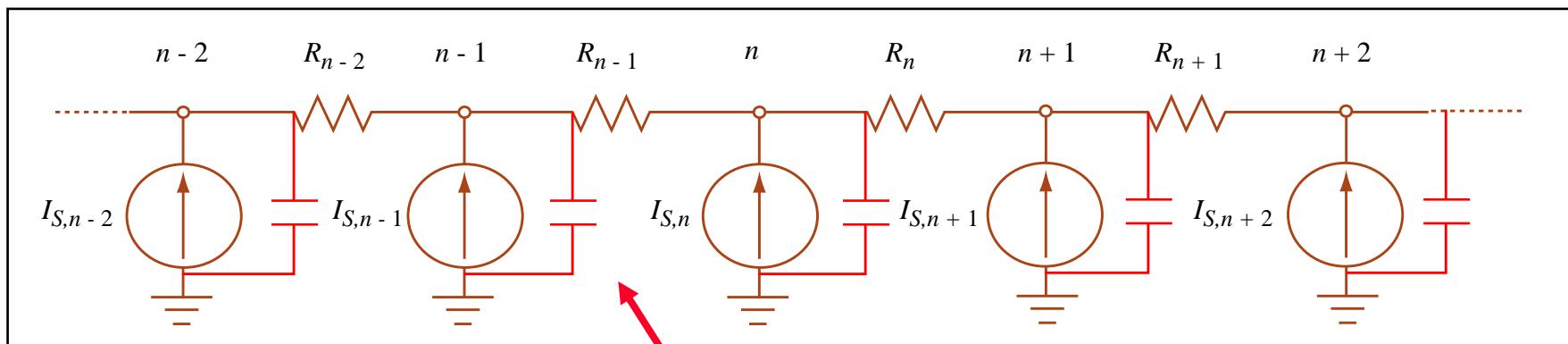


Image by MIT OpenCourseWare.

Adapted from Figure 12.1 in Senturia, Stephen D. *Microsystem Design*.
Boston, MA: Kluwer Academic Publishers, 2001, p. 302.
ISBN: 9780792372462.

$$C = hA\rho_m \tilde{C}_m$$




Node volume

Transient Modeling

> Finite-difference method

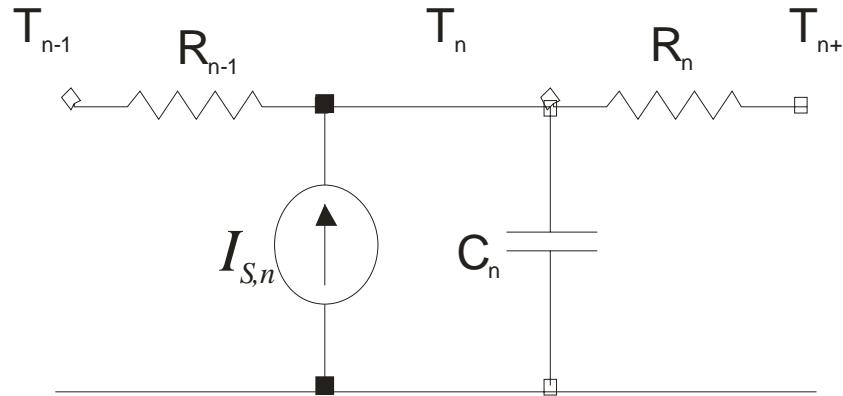- What does the matrix representation look like now?



$$I_{S,n} + G_{n-1}(T_{n-1} - T_n) + G_n(T_{n+1} - T_n) - C_n \dot{T}_n = 0$$

$$-G_{n-1}(T_{n-1} - T_n) - G_n(T_{n+1} - T_n) + C_n \dot{T}_n = I_{S,n}$$



$$\mathbf{G}\mathbf{T} + \mathbf{C}\dot{\mathbf{T}} = \mathbf{P}$$

$$\dot{\mathbf{T}} = \mathbf{A}\mathbf{T} + \mathbf{B}\mathbf{P}$$

Transient Modeling (continued)

> Eigenfunction method:

- Spatial response same as before
- Use impulse response in time to eventually get Laplace transfer function
- Use separation of variables to separate space and time

Separate variables

$$T(x, t) = \hat{T}(x)Y(t)$$

$$\frac{dT}{dt} - D\nabla^2 T = \frac{1}{\tilde{C}} \tilde{P} \Big|_{sources}$$

$$\tilde{P}(x, t) = \tilde{Q}_0(x)\delta(t) \quad [\text{J/m}^3]$$


$$\frac{dT}{dt} - D\nabla^2 T = 0 \quad t > 0^+$$

$$\hat{T}(x) \frac{dY(t)}{dt} - DY(t) \frac{d^2\hat{T}(x)}{dx^2} = 0$$

$$D \frac{1}{\hat{T}(x)} \frac{d^2\hat{T}(x)}{dx^2} = -\alpha = \frac{1}{Y(t)} \frac{dY(t)}{dt}$$

Transient Modeling (continued)

> Eigenfunction method:

- Time response is a sum of decaying exponentials
- Time and space are linked via eigenvalues

$$D \frac{1}{\hat{T}(x)} \frac{d^2 \hat{T}(x)}{dx^2} = -\alpha = \frac{1}{Y(t)} \frac{dY(t)}{dt}$$

$$Y(t) = e^{-\alpha t}$$

$$T(x, t) = \hat{T}(x) e^{-\alpha t}$$

$$D \frac{d^2 \hat{T}}{dx^2} = -\alpha \hat{T}$$

$$\hat{T}(x) = \sum_n A_n \sqrt{\frac{2}{L}} \sin(k_n x)$$

$$k_n^2 D = \alpha \Rightarrow k_n^2 = \frac{\alpha}{D} = \left(\frac{n\pi}{L} \right)^2$$

Transient Modeling (continued)

> Eigenfunction method:

- Match I.C. at $t=0$ to get series coefficients
- $T(x,0)$ is related to instantaneous heat input and heat capacity

$$T(x,t) = \sum_n A_n \sqrt{\frac{2}{L}} \sin(k_n x) e^{-\alpha_n t}$$

$$T(x,0) = \sum_n A_n \sqrt{\frac{2}{L}} \sin(k_n x) = \frac{\tilde{Q}_0}{\tilde{C}}$$

$$A_n = \frac{\tilde{Q}_0}{\tilde{C}} \sqrt{\frac{2}{L}} \int_0^L \sin(k_n x) dx$$

$$A_{n,odd} = \frac{\tilde{Q}_0}{\tilde{C}} \sqrt{\frac{2}{L}} \frac{2}{k_n} = \frac{\tilde{Q}_0}{\tilde{C}} \sqrt{\frac{2}{L}} \frac{2L}{n\pi}$$

$$\hat{T}(x,t) = \sum_{n,odd} \frac{4}{n\pi} \frac{\tilde{Q}_0}{\tilde{C}} \sin(k_n x) e^{-\alpha_n t}$$

Example: Impulse Response

- > Uniformly heated bar, an impulse in time
- > Result is a series of decaying exponentials in time

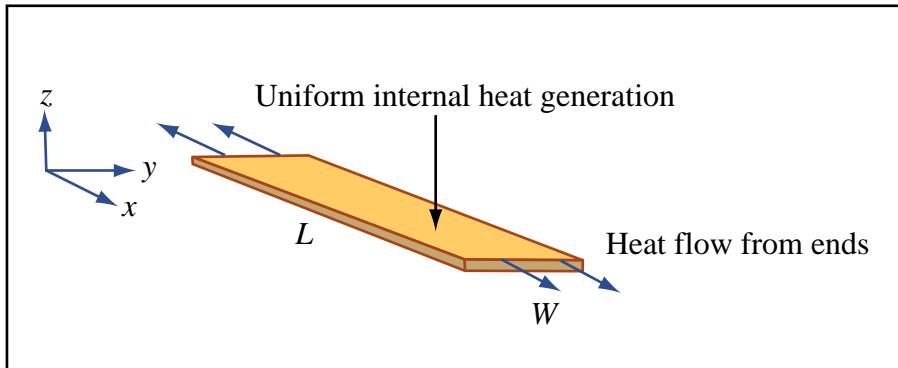


Image by MIT OpenCourseWare.

Adapted from Figure 12.3 in Senturia, Stephen D. *Microsystem Design*. Boston, MA: Kluwer Academic Publishers, 2001, p. 308. ISBN: 9780792372462.

$$T(x,t) = \frac{\tilde{Q}_0}{\tilde{C}} \sum_{n \text{ odd}} \left(\frac{4}{n\pi} \right) \sin\left(\frac{n\pi x}{L}\right) e^{-\alpha_n t}$$

where $\alpha_n = \frac{n^2\pi^2 D}{L^2}$ **lower spatial frequencies decay slower**

Using the Eigenfunction Solution

- > We can go from solution to equivalent circuit

$$I_Q = -\kappa \left(\int_0^W \int_0^H \frac{\partial T}{\partial x} \Big|_{x=0} dz dy - \int_0^W \int_0^H \frac{\partial T}{\partial x} \Big|_{x=L} dz dy \right)$$

- > First, we will lump

- Heat current conducted out as output
- Choose heat current source as input $\tilde{P} = \tilde{Q}_0 \delta(t)$

$$I_Q(t) = \left(\kappa W H \frac{8}{L} \sum_{n \text{ odd}} e^{-\alpha_n t} \right) \frac{\tilde{Q}_0}{\tilde{C}}$$

- > Then take Laplace

$$I_{Q,n}(s) = \frac{8\kappa W H}{\alpha_n L} \frac{1}{1 + s/\alpha_n} \frac{\tilde{Q}_0}{\tilde{C}}$$

$$Y(s) = \frac{1}{1 + s/\alpha_n} X(s)$$

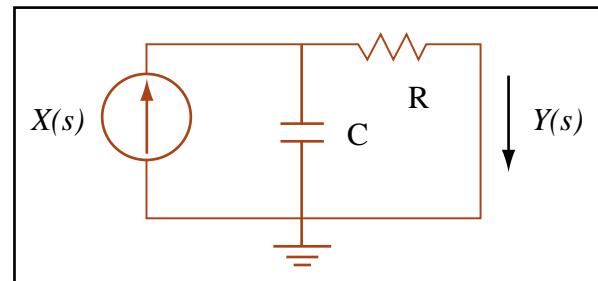


Image by MIT OpenCourseWare.

Adapted from Figure 12.4 in Senturia, Stephen D. *Microsystem Design*.
Boston, MA: Kluwer Academic Publishers, 2001, p. 310. ISBN: 9780792372462.

Using the Eigenfunction Solution

- > **Each term in the eigenfunction solution has a simple circuit representation**
- > This means that if the eigenfunction solution converges with a few terms, the lumped circuit is very simple

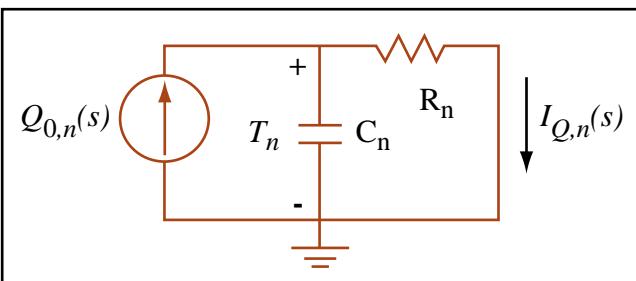


Image by MIT OpenCourseWare.

Adapted from Figure 12.4 in Senturia, Stephen D. *Microsystem Design*.
Boston, MA: Kluwer Academic Publishers, 2001, p. 310. ISBN: 9780792372462.

$$C_n = (\text{mode shape})(\text{volume})\tilde{C}$$

$$C_n = \tilde{C} \int_0^H \int_0^W \int_0^L \sin\left(\frac{n\pi x}{L}\right) dx dy dz = \frac{2}{n\pi} LHW \tilde{C}$$

$$\frac{1}{R_n C_n} = \alpha_n = \frac{n^2 \pi^2 D}{L^2}$$

↓

$$R_n = \left(\frac{1}{n\pi} \right) \frac{L/2}{\kappa WH}$$


$$Q_{0,n}(s) = \frac{8\kappa WH}{\alpha_n L} \frac{\tilde{Q}_0}{\tilde{C}} = \frac{8\kappa WHL}{n^2 \pi^2 D} \frac{\tilde{Q}_0}{\tilde{C}}$$

$$Q_{0,n}(s) = \left(\frac{8}{n^2 \pi^2} \right) (WHL) \tilde{Q}_0$$


$$Q_{0,n}(t) = \left(\frac{8}{n^2 \pi^2} \right) (WHL) \tilde{Q}_0 \delta(t)$$

A Three-Mode Equivalent Circuit
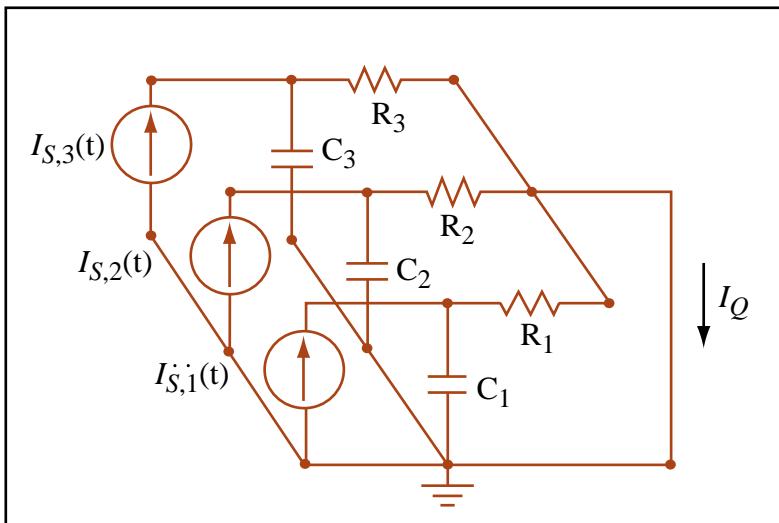
> For the first three terms in the eigenfunction expansion, we combine the three single-term circuits appropriately



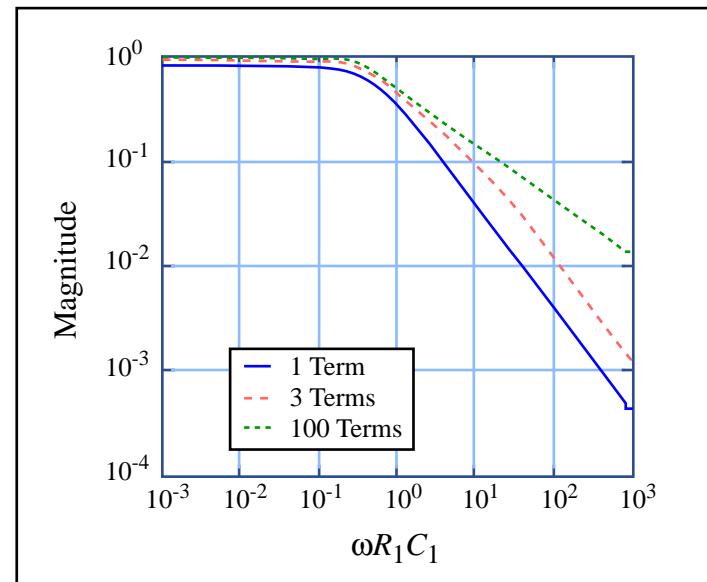Adapted from Figure 12.5 in Senturia, Stephen D. *Microsystem Design*.
Boston, MA: Kluwer Academic Publishers, 2001, p. 312. ISBN: 9780792372462.



Adapted from Figure 12.6 in Senturia, Stephen D. *Microsystem Design*.
Boston, MA: Kluwer Academic Publishers, 2001, p. 313. ISBN: 9780792372462.

Outline

- > Review
- > Lumped-element modeling: self-heating of resistor
- > The DC Steady State – the Poisson equation
 - Finite-difference methods
 - Eigenfunction methods
- > Transient Response
 - Finite-difference methods
 - Eigenfunction methods
- > Thermoelectricity

Microscale temperature measurement/control

- > We have seen that a resistor can be used as a temperature sensor and hotplate
- > There are other techniques to measure or control temperature at microscale
 - Couple temperature to material properties
- > Sensors
 - TCR: temperature → resistance change
 - Thermal bimorph: temperature → deflection
 - Thermoelectrics: temperature → induced voltage

Coupled Flows

- > In an ideal world, one driving force creates one flux

$$J_Q = -\kappa \nabla T$$

- > In our world, multiple forces create multiple fluxes

- Drift-diffusion in semiconductors or electrolytes

$$J_e = -\sigma_e \nabla \phi$$

- > In general, all the different fluxes are coupled

$$J_e = -z_n q_e D_n \nabla n - q_e n \mu_n \nabla \phi$$

- > If you set it up right, the L_{ij} matrix is reciprocal

- The Onsager Relations


$$J_i = \sum_{j=1}^n L_{ij} F_j$$

Quantities in the Onsager Relations

- > To explain thermoelectrics, we must look at coupling between heat flow and electric field
- > This is written in a standard form

$$J_e = -L_{11}\nabla\varphi - L_{12}\nabla T$$
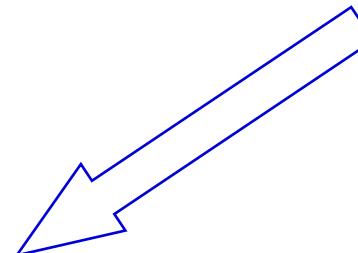
$$\frac{J_Q}{T} = -L_{21}\nabla\varphi - L_{22}\nabla T$$



Resistivity **Seebeck coefficient**

$$-\nabla\varphi = \rho_e J_e + \alpha_s \nabla T$$

$$J_Q = \Pi J_e - \kappa \nabla T$$

Peltier coefficient **Thermal conductivity**

Thermocouples

- > Analyze the potential gradient around a closed loop under the assumption of zero current ($J_e=0$)
- > Thermocouple voltage depends on the difference in Seebeck Coefficient between the two materials, integrated from one temperature to the other
- > It is a BULK EFFECT, not a junction effect
- > It is possible to make thermocouples by accident when using different materials in MEMS devices in regions that might have temperature gradients!

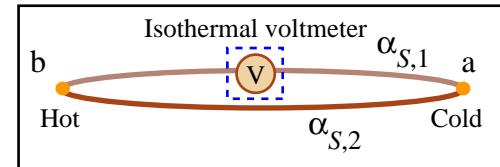


Image by MIT OpenCourseWare.
Adapted from Figure 11.10 in Senturia, Stephen D. *Microsystem Design*. Boston, MA: Kluwer Academic Publishers, 2001, p. 294. ISBN: 9780792372462.

$$-\nabla \varphi = \alpha_s \nabla T$$

↓

$$V_{ab} = \int_{T_a}^{T_b} \alpha_s(T) dT$$

Go around the loop


$$V_{TC} = \int_{T_C}^{T_H} (\alpha_{S,2} - \alpha_{S,1}) dT$$

$$V_{TC} = (\alpha_{S,2} - \alpha_{S,1}) \Delta T$$

For small temp rises

MEMS Thermocouples

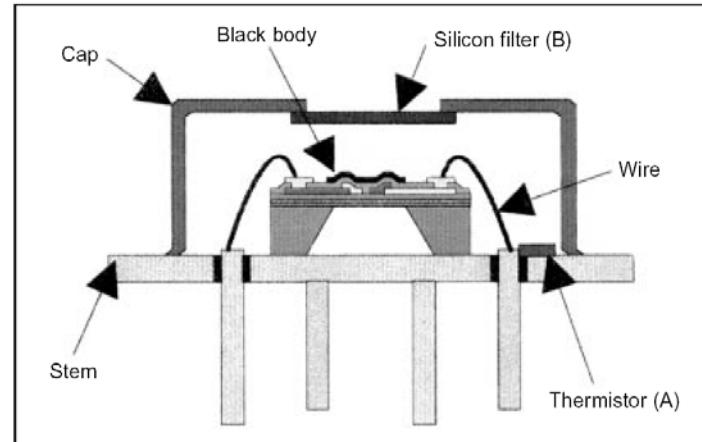- > Many thermocouples in series create higher sensitivity (V/K)
- > These are known as thermopiles
- > In MEMS thermopiles, often use Al/Si or Al/polySi
- > Able to get good thermal isolation of sensing element
- > Number of thermocouples is limited by leg width
 - Increasing leg width decreases thermal resistance and thus temperature response



Courtesy of Thermometrics Corporation. Used with permission.

Thermometrics commercial Si thermopile

Image removed due to copyright restrictions.

Conclusions

- > The thermal domain is a great way to transfer energy around
 - Except that you have to pay the tax
- > We can model thermal problems using
 - Equivalent circuits via lumped element models *in space*
 - » “Big” and “small”
 - Equivalent circuits via lumped element models *in reciprocal space*

For Further Information

- > Introduction to Heat Transfer, Incropera and DeWitt
 - > Analysis of Transport Phenomena, William Deen
 - > Solid-State Physics, Ashcroft and Mermin
-